

UNIVERSITY OF MICHIGAN

EECS 270: Intro to Logic Design

Midterm Exam 2

Prof. Karem A Sakallah

Wednesday November 17, 2021
6:00-8:00 p.m.

A - L: 1013 DOW || M - RL: 1017 DOW || S - T: 1006 DOW || U - Z: 1018 DOW

Name: _____

UMID: _____

Honor Pledge:

"I have neither given nor received aid on this exam, nor have I concealed any violation of the Honor Code."

Signature: _____

Instructions:

- The exam is closed book except for **two** 8.5"x11" sheets of notes
No electronics of any kind may be used.
- Print your name and student ID number and sign the honor pledge.
- Make sure your answers and meaningful work are on the pages with numbers at the bottom. We will be scanning and looking at only these pages: all work on the backs of pages will **not** be checked for determining partial credit.
- The exam consists of 12 problems with the point distribution indicated here. Please keep this in mind as you work through the exam. Use your time wisely.
- There are 13 pages in this exam. Make sure that you have all 13 pages and notify an instructor if you do not.

| | | |
|--------|-------|------|
| 1. | _____ | /6 |
| 2. | _____ | /8 |
| 3. | _____ | /10 |
| 4. | _____ | /10 |
| 5. | _____ | /5 |
| 6. | _____ | /10 |
| 7. | _____ | /4 |
| 8. | _____ | /10 |
| 9. | _____ | /10 |
| 10. | _____ | /12 |
| 11. | _____ | /5 |
| 12. | _____ | /10 |
| Total: | _____ | /100 |


1 [Latch and and Flip-Flop Timing–6 points]

- a. [1 points] If the propagation delay of the NOR gates in an SR latch is 5 ns, what is the *minimum allowable pulse width* on the S and R inputs to guarantee proper operation?

Answer: $5\text{ns} + 5\text{ns} = 10\text{ns}$.

 
- b. [1 points]

Consider the back-to-back negative edge-triggered flip-flop and positive level-sensitive latch shown here as a *single flip-flop*. Let $C \uparrow$ and $C \downarrow$ denote, respectively, the rising and falling edges of the clock input C , and let S and H denote the setup and hold times. Circle the correct answers below.





S and H must be checked against:

Q changes shortly after:

 

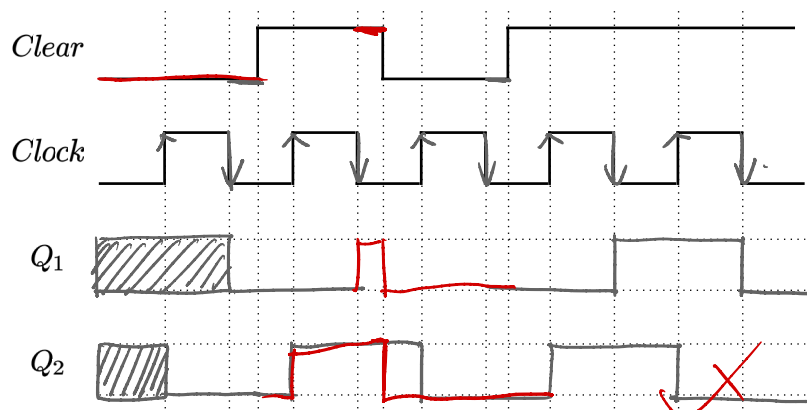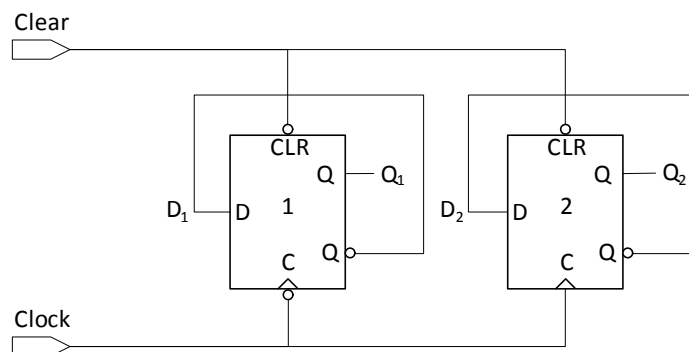- c. [4 points] The following circuit has two D flip-flops with asynchronous active-low “CLR” inputs. Complete the timing diagram for Q_1 and Q_2 assuming zero combinational delays. You do not need to show causality arrows.



2 [Weird Latch—8 points]

- a. [4 points] The XOR/NAND/INV circuit shown below is proposed as a new type of latch. Derive its transition table, indicating the function it performs (Set, Reset, Hold, Invalid). For invalid input combinations, state the reasons for their invalidity (e.g., Q and QB are not complements, Q and QB oscillate, etc.)

$Q^+ = (Q \cdot Y)' \oplus X$

Handwritten calculations for the transition table:

- $(Q)' \oplus 1$
- $Q=0 \rightarrow 0$
- $Q=1 \rightarrow 1$
- $Q^+ = (0)' \oplus 0 = 1 \oplus 0 = 1$
- $Q^+ = (Q)' \oplus 0$
- $Q=0 \rightarrow 1$
- $Q=1 \rightarrow 0$
- $(0)' \oplus 1 = 1 \oplus 1 = 0$

| X | Y | Q^+ | Function |
|---|---|-------|------------------------|
| 0 | 0 | 1 | Set |
| 0 | 1 | Q' | Oscillation (invalid). |
| 1 | 0 | 0 | Reset |
| 1 | 1 | Q | Hold |

- b. [4 points] The invalid input combination(s) in this latch can be eliminated by “merging” them with one of the valid combinations (Set, Reset, or Hold). This can be accomplished by adding a “Bad Combo Eliminator” circuit as shown below. Design a minimal 2-input/2-output gate-level circuit (using the usual gates) that accepts all possible combinations on its X^*Y^* inputs, while producing only valid combinations on its XY outputs. Write the corresponding logic expressions for X and Y in terms of X^* and Y^* .

Handwritten logic expressions for the Bad Combo Eliminator:

Truth table for X^*Y^* to XY :

| X^* | Y^* | X | Y |
|-------|-------|-----|-----|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 |

Logic expressions:

$$X = X^* + Y^*$$


$$Y = Y^*$$

Handwritten derivation of the logic expression for X :

$$X^*Y^* + X^*Y^* + X^*Y^* = X^* + Y^*$$

3 [Sequential Circuit Analysis–10 points]

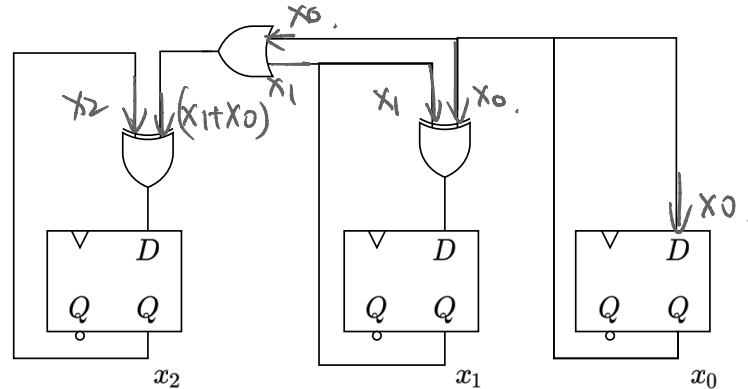Let $X = x_2x_1x_0$ denote a two's complement number that has been loaded into the 3-bit register shown below. (The logic for loading the register is not shown.)



- a. **[3 points]** Write the symbolic expressions of the next-state for each bit of X using the usual logic operators (AND, OR, XOR, etc.) You do not need to simplify the expressions.

$$x_0^+ = x_0$$

$$x_1^+ = x_1 \oplus x_0$$

$$x_2^+ = x_2 \oplus (x_1 \oplus x_0)$$

- b. **[6 points]** Write the simplest possible symbolic expressions for each bit of X after *exactly two clock ticks*. Hint: $a + b = a \oplus b \oplus (ab)$.

$$x_0^{++} = x_0$$

$$x_1^{++} = (x_1 \oplus x_0) \oplus x_0 = x_1 \oplus (x_0 \oplus x_0) = x_1$$

$$x_2^{++} = x_2^+ \oplus (x_1^+ \oplus x_0^+) = [x_2 \oplus (x_1 \oplus x_0)] \oplus [x_1 \oplus x_0 \oplus x_0] = x_2$$

-3₁₀ 1 0 1


- c. **[1 points]** Assuming the register is initialized to $X = -3_{10}$, what is its value, in decimal notation, after two clock ticks?

Answer: $X = 101_{10}$

$$\begin{aligned}
 & x_1 \oplus x_0 \oplus x_0 \\
 &= x_1 \oplus [x_0 \oplus x_0] \oplus [(x_1 \oplus x_0) \cdot x_0] \quad x_1 \oplus (x_1 \cdot x_0) \oplus x_0 \\
 &= x_1 \oplus 0 \oplus [(x_1 \oplus x_0) \cdot x_0] \quad x_2 \oplus x_1 \oplus x_0 \oplus x_1 \oplus x_0 \\
 & \quad x_1 \oplus [x_1 \cdot x_0 \oplus x_0 \cdot x_0] \\
 & \quad x_2 \\
 & x_1 \oplus [x_1 \cdot x_0 \oplus x_0]
 \end{aligned}$$

4 [Sequential Circuit Analysis–10 points]

 This sequential circuit sets its output Z to 1 when the appropriate secret code is entered on its input X . Assuming that the circuit is reset to state $Q_1Q_2 = 00$ before application of any input, your job is to figure out what the secret code is. *Hint: Note that Z is a Mealy output!*



- a. **[3 points]** Derive the next-state and output equations:

$$Q_1^+ = \underline{\hspace{10cm}}$$

$$Q_2^+ = \underline{\hspace{10cm}}$$

$$Z = \underline{\hspace{10cm}}$$

- b. **[4 points]** Complete the following transition/output table. Note that each table entry should be formatted as “Next State/Output”.

| $Q_1 Q_2$ | $X = 0$ | $X = 1$ |
|-----------|---------|---------|
| 0 0 | | |
| 0 1 | | |
| 1 0 | | |
| 1 1 | | |


$Q_1^+ Q_2^+ / Z$

- c. **[3 points]** What is the secret code?

Secret Code: _____

5 [Sequential Circuit Analysis–5 points]

 Consider the following synchronous sequential circuit and corresponding state assignment. Which of the following choices is its correct state table?



State Assignment*

| Q_1Q_2 | State Label |
|----------|-------------|
| 0 0 | A |
| 0 1 | B |
| 1 0 | C |
| 1 1 | D |

*Note that Q_1 is the most significant bit.

A.

| PS | $X = 0$ | $X = 1$ |
|------|---------|---------|
| A | A | B |
| B | B | C |
| C | A | D |
| D | B | C |

NS

B.

| PS | $X = 0$ | $X = 1$ |
|------|---------|---------|
| A | B | C |
| B | C | D |
| C | B | A |
| D | C | D |

NS

C.

| PS | $X = 0$ | $X = 1$ |
|------|---------|---------|
| A | C | D |
| B | D | A |
| C | C | B |
| D | D | A |

NS

D.

| PS | $X = 0$ | $X = 1$ |
|------|---------|---------|
| A | D | A |
| B | A | B |
| C | D | C |
| D | A | B |

NS


E.

| PS | $X = 0$ | $X = 1$ |
|------|---------|---------|
| A | C | B |
| B | B | A |
| C | C | D |
| D | B | A |

NS


7 [Sequential Circuit Design—4 points]

A partially-completed state diagram for a sequence recognizer with input x and output z is shown below. The output should be 1 whenever the pattern 1101, including overlaps, appears on the input; otherwise it should be 0. Each arrow in the diagram is labeled with the value of x and corresponding value of z for that transition (e.g., the transition from A to B occurs when $x = 1$ and sets z to 0). Assume that A is the initial state.

 


Identify the two missing transitions in this diagram.

First missing transition:

 

Second missing transition:

 

8 [Two-Level Minimization—10 points]

Consider the following K-Map for the 4-variable function $f(w, x, y, z)$:

| | | yz | | | |
|----|----|----|----|----|----|
| | | 00 | 01 | 11 | 10 |
| wx | 00 | 1 | 0 | 1 | 1 |
| | 01 | d | d | d | 0 |
| | 11 | 0 | d | d | 0 |
| | 10 | d | 1 | 0 | 1 |

For each of the product terms in the following table, indicate if the product term is an implicant of f , and whether it is prime and/or essential. Indicate your answer by writing “Yes”, “No”, or “N/A” (for not applicable). N/A means that the product term a) is not an implicant of f , b) is an implicant that is not prime, or c) is a prime implicant that is not essential.


*Hint: It helps if you first find **all** the prime implicants before filling the table!*

| Product Term | $w'x$ | xz | $x'z'$ | $x'y'z'$ | $w'yz$ | $wx'y'$ | $wx'y'z$ | $w'xyz$ | $w'y'z'$ | $w'x'y$ |
|------------------|-------|------|--------|----------|--------|---------|----------|---------|----------|---------|
| Implicant? | | | | | | | | | | |
| Prime Implicant? | | | | | | | | | | |
| Essential PI? | | | | | | | | | | |

9 [Sequential Blocks–10 points]

 a. [3 points]


This circuit uses a binary counter that has synchronous load and clear controls. What is its modulus?



Answer: _____

 b. [3 points]

A 4-bit binary up-counter is connected to an 8-to-1 MUX. As the counter cycles through its 16 states (from 0 to 15), the output Y will be repeatedly asserted (becomes 1) at a subset of these states. Determine this subset as an increasing sequence of decimal values.



Answer: _____

c. [4 points]

An 8-bit Johnson counter is constructed from a left-shift register $Q_7Q_6 \cdots Q_0$. The next-state equations for each of the register's 8 flip-flops are:

$$Q_0^+ = \underline{\hspace{2cm}} \quad Q_4^+ = \underline{\hspace{2cm}}$$

$$Q_1^+ = \underline{\hspace{2cm}} \quad Q_5^+ = \underline{\hspace{2cm}}$$

$$Q_2^+ = \underline{\hspace{2cm}} \quad Q_6^+ = \underline{\hspace{2cm}}$$

$$Q_3^+ = \underline{\hspace{2cm}} \quad Q_7^+ = \underline{\hspace{2cm}}$$

10 [Sequential Timing Analysis–12 points]

The following tables show the minimum and maximum combinational delays, as well as the timing parameters of the flip-flops, in a sequential circuit with three positive edge-triggered D flip-flops. All delays and timing parameters are in nanoseconds.

| Minimum Delays | | | | Maximum Delays | | | | FF Timing Parameters | |
|----------------|----------|-------|----------|----------------|-----------|-------|-----------|----------------------|---|
| δ_{ij} | D_0 | D_1 | D_2 | Δ_{ij} | D_0 | D_1 | D_2 | | |
| Q_0 | 1 | 2 | 3 | Q_0 | 5 | 3 | 7 | Clock to Q delay: | 2 |
| Q_1 | 2 | 1 | ∞ | Q_1 | 3 | 4 | $-\infty$ | Setup time: | 2 |
| Q_2 | ∞ | 0 | 2 | Q_2 | $-\infty$ | 4 | 5 | Hold time: | 1 |

The timing specification for this circuit requires it to operate at a frequency of 100MHz.

- a. **[6 points]** Compute the early and late arrival times for the three flip-flops.

$$a_0 = \underline{\hspace{2cm}} \quad A_0 = \underline{\hspace{2cm}}$$

$$a_1 = \underline{\hspace{2cm}} \quad A_1 = \underline{\hspace{2cm}}$$

$$a_2 = \underline{\hspace{2cm}} \quad A_2 = \underline{\hspace{2cm}}$$

- b. **[3 points]** Determine if there are any setup or hold violations:

| | | |
|------------------------|------|-------|
| Hold violation at FF0 | True | False |
| Hold violation at FF1 | True | False |
| Hold violation at FF2 | True | False |
| Setup violation at FF0 | True | False |
| Setup violation at FF1 | True | False |
| Setup violation at FF2 | True | False |

- c. **[3 points]** If there are setup or hold violations that prevent the circuit from operating at 100MHz, what is the minimum clock period P_{\min} in nanoseconds and corresponding clock frequency f_{\max} in MHz that allow the circuit to function without timing errors? *Note: Truncate f_{\max} to one digit after the decimal point.*

$$P_{\min} = \underline{\hspace{2cm}}$$

$$f_{\max} = \underline{\hspace{2cm}}$$

11 [Potpourri—5 points]

A selection of multiple-choice and True/False questions on various topics!

a. [1 points]

The main difference between Moore and Mealy outputs is:

- A. Moore outputs are synchronous with the clock whereas Mealy outputs are asynchronous with the clock
- B. Moore outputs are functions of the inputs only whereas Mealy outputs are functions of both the inputs and the state variables
- C. Moore outputs are functions of the state variables only whereas Mealy outputs are functions of both the state variables and the inputs
- D. Moore outputs are functions of primary inputs and state variables whereas Mealy outputs are functions of state variables only.
- E. None of the above

b. [1 points]

An example of an asynchronous counter is:

- A. A decade counter
- B. A Johnson counter
- C. A ring counter
- D. A ripple binary counter
- E. None; All are synchronous

c. [1 points]

A minimal SOP solution for a Boolean function must include at least one essential prime implicant.

- A. TRUE
- B. FALSE

d. [1 points]

The counting sequence, in decimal, of a 2-bit Johnson counter is: $0 \rightarrow$ _____

e. [1 points]

The number of prime implicants of an n -input OR function is _____

12 [Lab Experience—10 points]

Complete the following Verilog that implements a counter that counts 0,1,2,3,2,1 and repeats.

```
module counter(input reset, clk, output reg [1:0] state);
```

```
    BLANK1 NS1, NS0;    // next state
    BLANK2 S1, S0;      // current state
    reg D;              // direction: 1 is up, 0 is down
```

```
    assign NS1 = ~D & S1 & S0 | BLANK3 | D & S1 & ~S0;
    assign NS0 = BLANK4;
```

```
    BLANK5
begin
    if( reset ) begin S1 <= 0; S0 <= 0 ; D <= 1; end
    else begin BLANK6; end
    if (BLANK7) D <= 0; else BLANK8;
end
```

```
    BLANK9
begin
    state [1] = S1;
    state [0] = S0;
end
```

```
BLANK10
```

BLANK1: _____ BLANK6 : _____

BLANK2: _____ BLANK7 : _____

BLANK3: _____ BLANK8 : _____

BLANK4: _____ BLANK9 : _____

BLANK5: _____ BLANK10 : _____