

## Introduction to Computer Organization – Fall 2023

# Lab 5

Due: @11:55 PM, Wed October 4th

The following assignment is intended to be completed during your assigned lab period. One member of your group must submit the assignment to Gradescope by the posted deadline and indicate your group members when submitting the assignment. **Each group member must be present during the scheduled lab period in order to receive credit.**

Group names and unqiqlnames

Pod Member Name	Uniqname
Yuzhen chen	yuzhech
Therron Montgomery	therronm
Yuhan Zhang	zyuhan


For each of the following problems, one person should act as the "scribe" and log the discussions of the group. You should rotate who is the scribe for each problem and indicate in the given space.

**Problem 1: Circuit Delay [15 Points]**

Topics: Timing Diagrams, Propagation Delay

Scribe: [Scribe's name here]

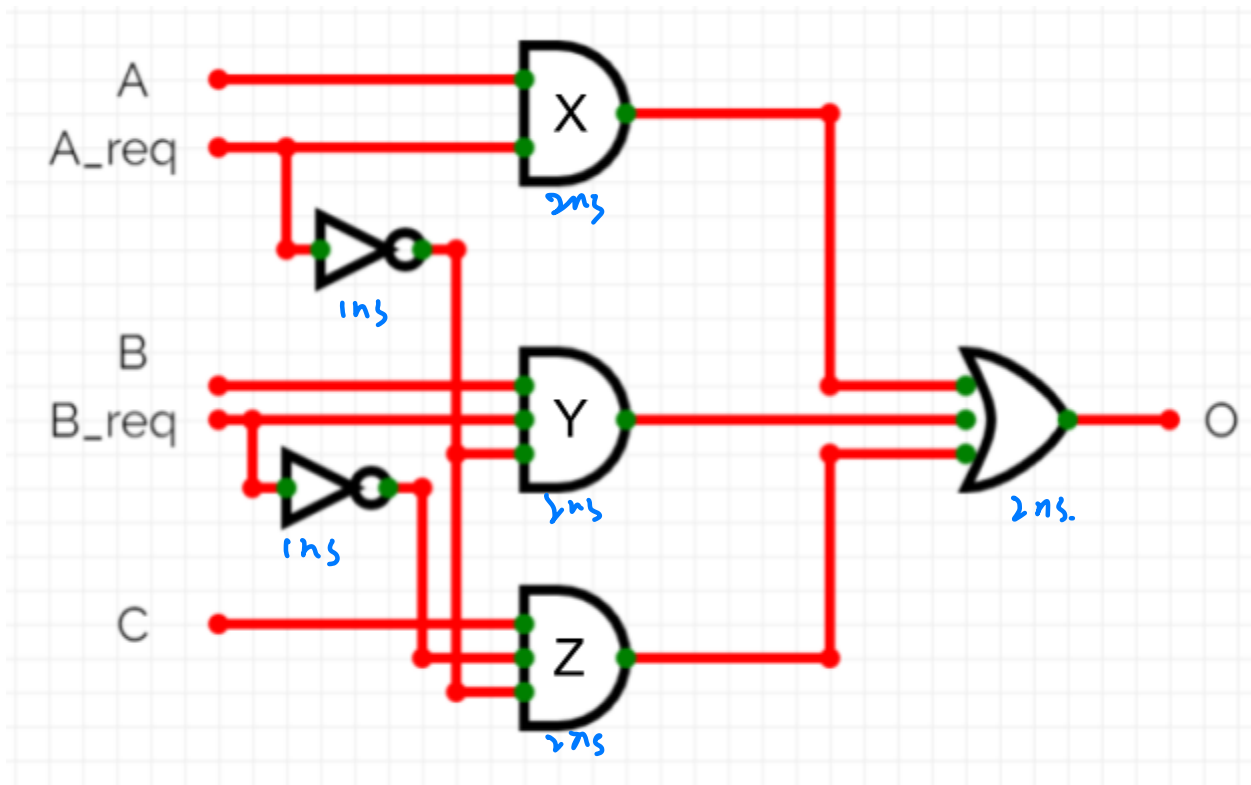Consider the following naive implementation of a priority selector. This priority selector takes 3 data inputs, “A,” “B,” and “C” and one data output, “O.” It has 2 requester inputs, “A\_req,” “B\_req.” If A\_req is asserted, O outputs the value of A. If A\_req is not asserted but B\_req is, O outputs the value of B. If no requesters are asserted, C is outputted.



Assume that NOT gates have a 1ns delay, and that OR and AND gates have a 2ns delay regardless of the number of input wires. Assume no wire delay.

Say that for an infinite amount of time before we start measuring, all input signals are “1.”

- At 1ns, B\_req goes to “0”
- At 2ns, A\_req goes to “0”
- At 6ns, C goes to “0”.
- At 8ns, A goes to “0”.
- At 9ns, A\_req and B\_req go to “1”.


$$X = A \cdot A\_req$$

$$Z = C \cdot B\_req' \cdot A\_req'$$

$$Y = B \cdot B\_req \cdot A\_req' \quad O = X + Y + Z$$

 - a. Draw a timing diagram from  $t=0\text{ns}$  to  $t=16\text{ns}$  showing the input signals (A, B, C), requester signals (A\_req, B\_req), the output signal (O), and all intermediate gates (!A\_req, !B\_req, X, Y, Z). The inputs, requesters, and 1 intermediate gate have been done for you. Also include a line "L" (for Logic) depicting what the output signal would be with no delay. [10 points]


For drawings, you may draw by hand and insert a photo of your work, or merge PDFs before submission, or just digitally modify the drawing below.



 - b. Draw a circuit using only two 2-input Muxes that implements the circuit. [5 points]

The definition of the 3-input priority selector is repeated:

- If A\_req is asserted, O outputs the value of A.
- If A\_req is not asserted but B\_req is, O outputs the value of B.
- If no requesters are asserted, C is outputted.




A_req	B_req	A	B	C
0	0	0	0	1
0	1	0	1	0
1	0	1	0	0
1	1	1	0	0

**Problem 2: Finely Stated [15 Points]**

Topics: FSM, Flip Flops, Decoders

Scribe: [Scribe's name here]

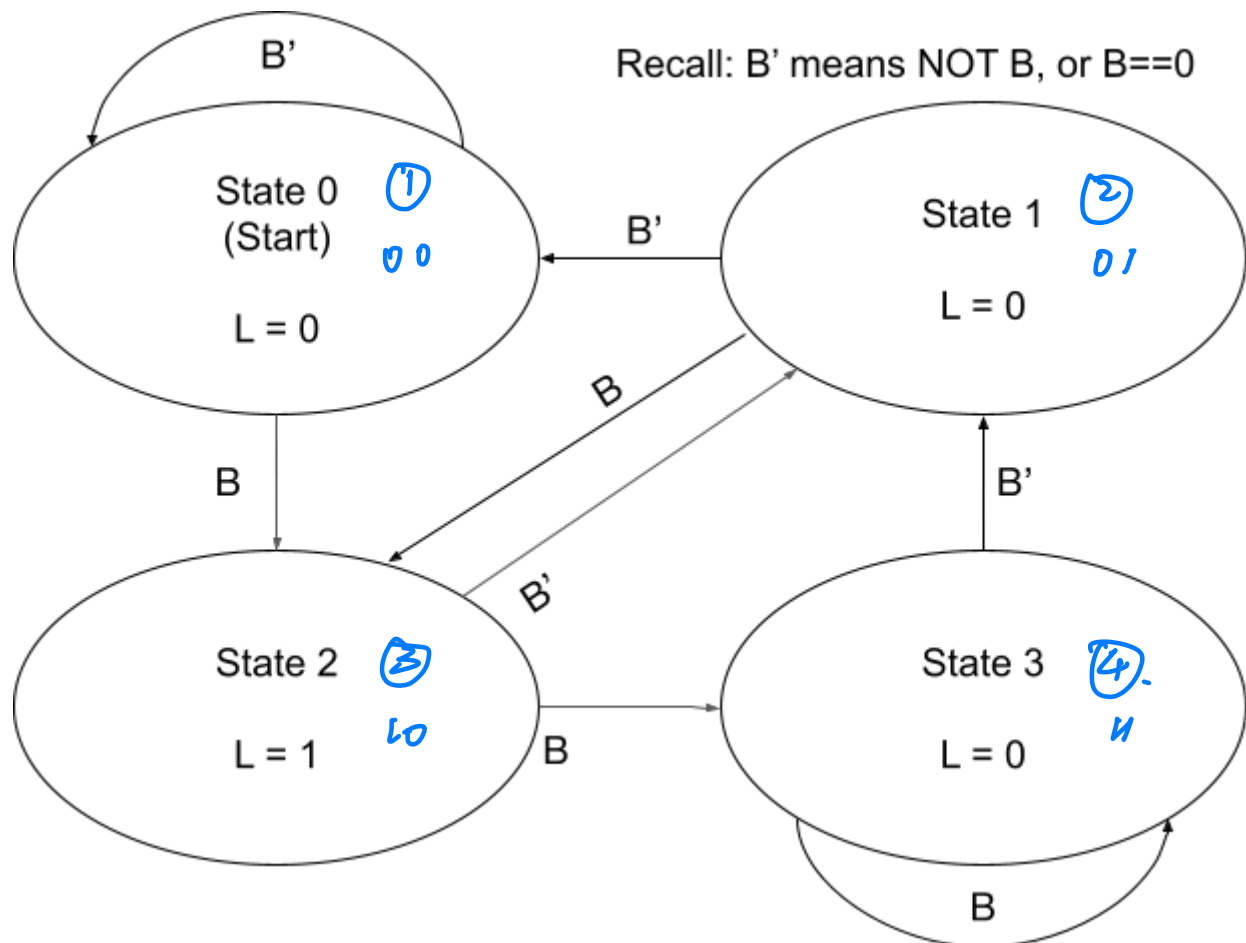Consider the finite state machine diagram below. This FSM tracks the last 2 values of the input B, sets an output L to 1 if a code is received.



On the next page, convert the Finite State Machine into a circuit. Fill in the provided bubbles in the control ROM to determine the next state [7.5 points]. Inside the dotted box, add wires and logic gates to complete the rest of the logic for the output L [7.5 points].

- Assume the clock is connected but not shown.
- Assume the flip flops have a starting value of 0.
- Do not add outputs to the control ROM, and do not modify anything outside the ROM bubbles and the dotted box.
- The decoder inputs are  $\{\text{State}_1, \text{State}_0, B\}$
- Filling in one of the control ROM bubbles means there is a connection, so current flows and we get a 1. Otherwise, the wires are disconnected and we get a 0.
  - For example, state 0 is done for you in the first 2 rows. When the FSM is in state 0 and  $B=0$ , the next state is 0, so both Next State bits are 0 and not filled in. But when the FSM is in state 0 and  $B=1$ , the next state is 2 (binary 10), so the bubble for the Next State<sub>1</sub> bit is filled in while the bubble for Next State<sub>0</sub> is not.

Q <sub>0</sub> Q <sub>1</sub>	B	B'	Z
00	10	00	0
01	10	00	0
10	11	01	1
11	11	01	0

The circuit diagram shows two D flip-flops, State<sub>1</sub> and State<sub>0</sub>, and a 3-to-8 decoder. The inputs are Clk and B. The outputs are Q<sub>1</sub>, Q<sub>0</sub>, and L.

**Handwritten Annotations:**

- Equation:**  $Q_1^+ = D_1$
- Truth Table:**

Q <sub>1</sub>	Q <sub>0</sub>	B	Q <sub>1</sub>
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1
- 3-to-8 Decoder Truth Table:**

Q <sub>1</sub>	Q <sub>0</sub>	B	Q <sub>1</sub>
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1
- Logic Expression:**  $Q_1 Q_0' B' + Q Q_0 B' + Q_1 Q_0' B + Q Q_0 B$
- Decoder Output Mapping:**
  - 000 → 4
  - 110 → 6
  - 101 → 5
  - 111 → 7

$Q_1, Q_0, B$	$Q_0$
0 0 0	0
0 1 0	0
1 0 0	1 $\leftarrow$
1 1 0	1 $\leftarrow$
0 0 1	0
0 1 1	0
1 0 1	1 $\leftarrow$
1 1 1	1 $\leftarrow$

$$Q_1 Q_0' B' + Q_1 Q_0 B' + Q_1 Q_0' B + Q_1 Q_0 B$$

$Q_1 Q_0 B$	$Q_1$
0 0 0	0
0 1 0	0
1 0 0	0
1 1 0	0
0 0 1	1
0 1 1	1
1 0 1	1
1 1 1	1

B.

001  $\rightarrow$  1

011 → }

$$101 \rightarrow 5$$

$$111 \rightarrow 7$$

**Problem 3: LC2K ABI [20 Points]**

Topics (Review from Lab 4): ABI, Functions, Loops

Scribe: [Scribe's name here]

Convert this function to LC2K using the following ABI:

- r0: always 0
- r1 - r2: function arguments, caller-save
- r3 - r4, r6: caller-save
- r5: stack pointer
- r7: return address (caller-save)

Assume the stack grows "up". If you want to store a new variable on the stack, you should write it to an address offset by r5, and then increment r5 by the appropriate amount. Make sure you decrement it back to the original value before returning from the function so that the calling function can access its own local variables.

Please submit typed LC2K code (which won't be autograded) - no handwritten code.

```
void start() {
    int a = -1, b = 2, c = 3;
    for (int i = 3; i != 0; --i) {
        mystery(i, a);
        c = i + b;
    }
}
```

```
Start lw 0 2 neg1 //a
      lw 0 3 one //inc
      add 3 3 4 //b
      add 3 4 6 //c
      add 0 6 1 //i
```

for beg 3 0 done //check.

sw 5 7 stack // store return address of caller

add 3 5 5 // sp++

sw 5 1 stack // store reg 1 (i) in to stack

add 3 5 5 // sp++.

sw 5 4 stack // store reg 4 (b) into stack.

add 3 5 5 // sp++.

lw 0 3 fcall

jr 3 7

don halt

reg 2 = -1 ← a.

reg 3 = 1 ← increment

✓ reg 4 = 2 ← b

reg 6 = 3 ← c.

✓ reg 1 = 3 ← i

Stack →

fcall .fill mystery.

one .fill 1

neg1 .fill -1

```

void Start() {
    int a = 1;
    a += mystery(a);
}

```

保 reg1 reg7

reg 1 → a = 1    reg 6 = one    每次 update stack 的  
最新位置。

start    lw 0 1    one    用 reg5 来记录目前位置和 stack  
          lw 0 6    one    相差多少。

          sw 5 7    stack  
          add 5 6    5  
          sw 5 1    stack  
          add 5 6    5    -

---

          lw 0 6    fcall  
          jor 6 7    reg5 ↑

---

          lw 0 6    negal  
          add 5 6    5    --  
          lw 5 1    stack  
          add 5 6    5    --  
          lw 5 7    stack

          jaln    7 6

Stack → reg7  
one . fill 1  
fcall . fill mystery  
negal . fill -1