



# UM EECS 270 F22

## Introduction to Logic Design

### 10. Analysis of Sequential Circuits


# Sequential Circuits




- Modeled as **Finite** State Machines
- Timing behavior:
  - Synchronous (clocked)
  - Asynchronous

Our Focus: **Synchronous** Sequential Circuits

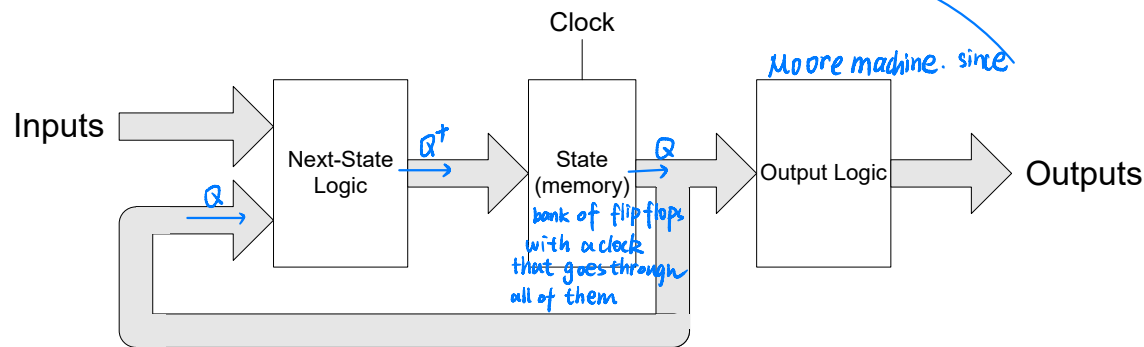- Sequential Circuit Components:
  - Next state logic (combinational):** next state =  $f(\text{current state, inputs})$
  - Memory (sequential):** stores state in terms of state variables
  - Output logic (combinational):**
    - Moore Output:** output =  $g(\text{current state})$  <sup>only  $z$</sup>




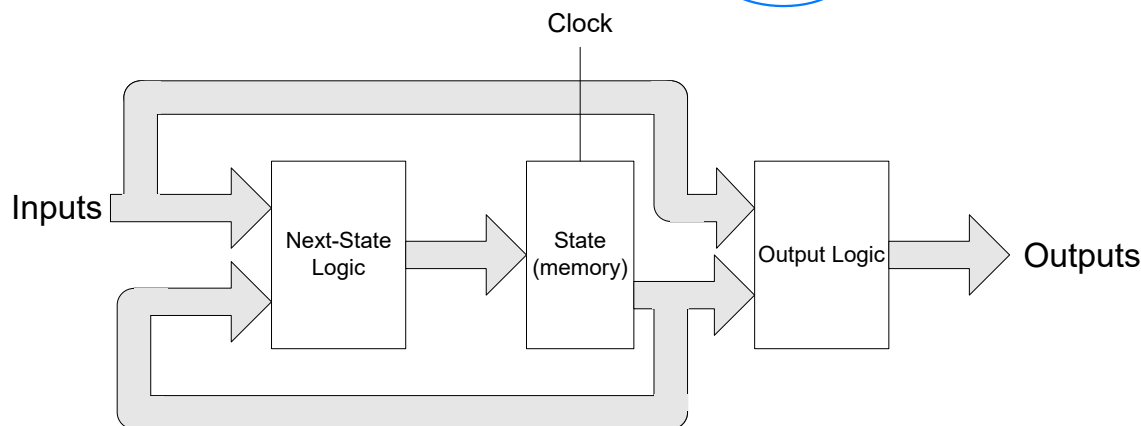- Mealy Output:** output =  $g(\text{current state, inputs})$  <sup>also</sup>



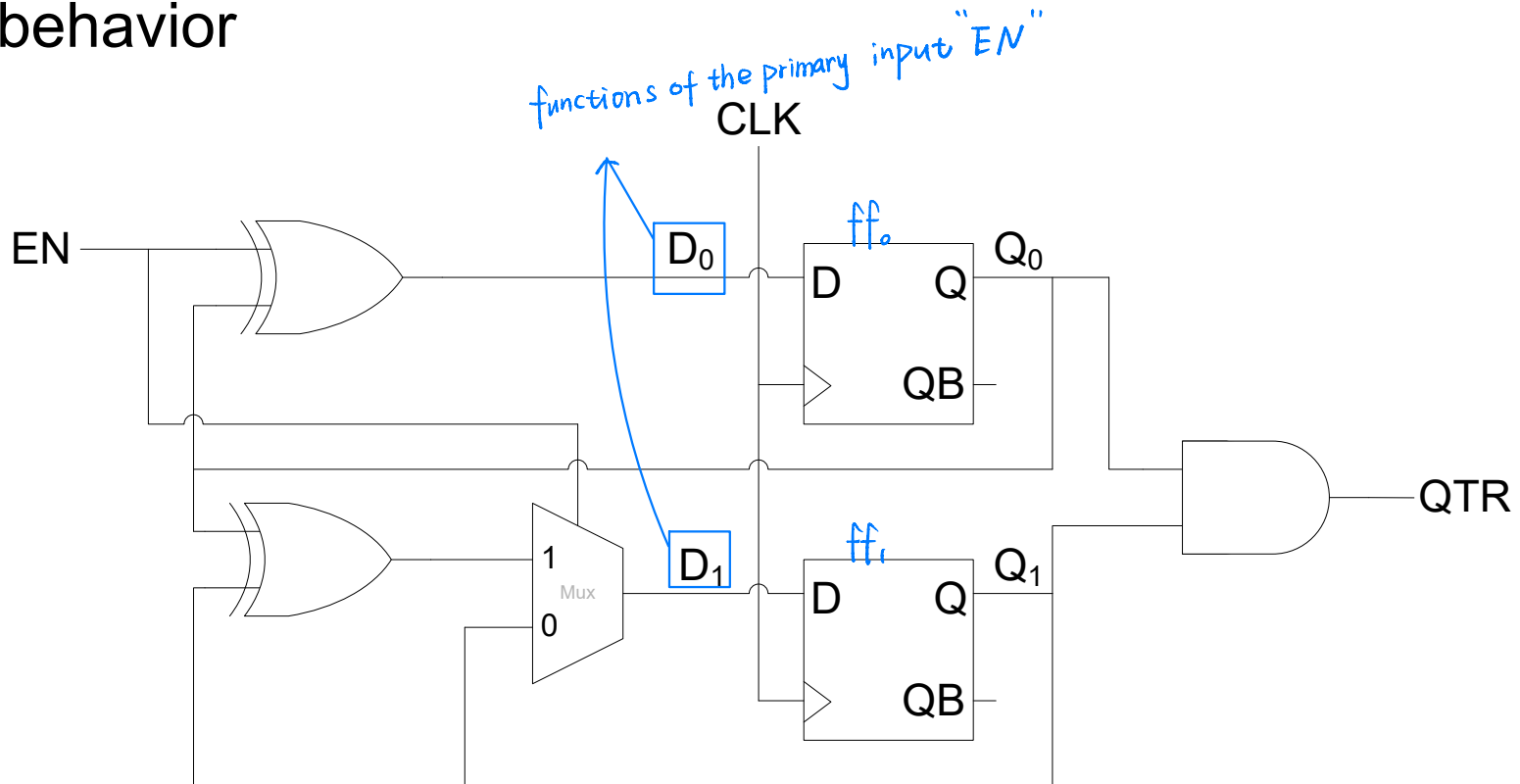
# Sequential Circuit Analysis

- Goal: Given a sequential circuit, describe the circuit's behavior



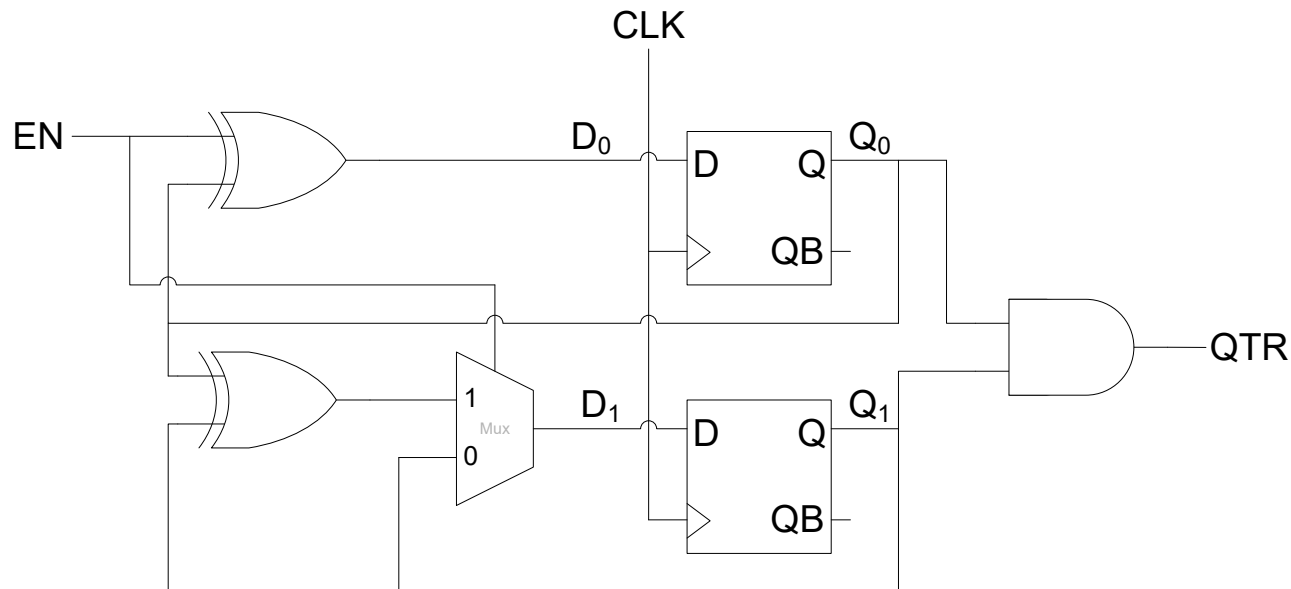- **Excitation equations** describe memory (FF or latch) input signals as a function of inputs and current state (i.e., state variables)




*Excitation Equations:*

$$D_0 = EN \oplus Q_0$$

$$D_1 = EN \cdot (Q_0 \oplus Q_1) + \overline{EN} \cdot Q_1$$

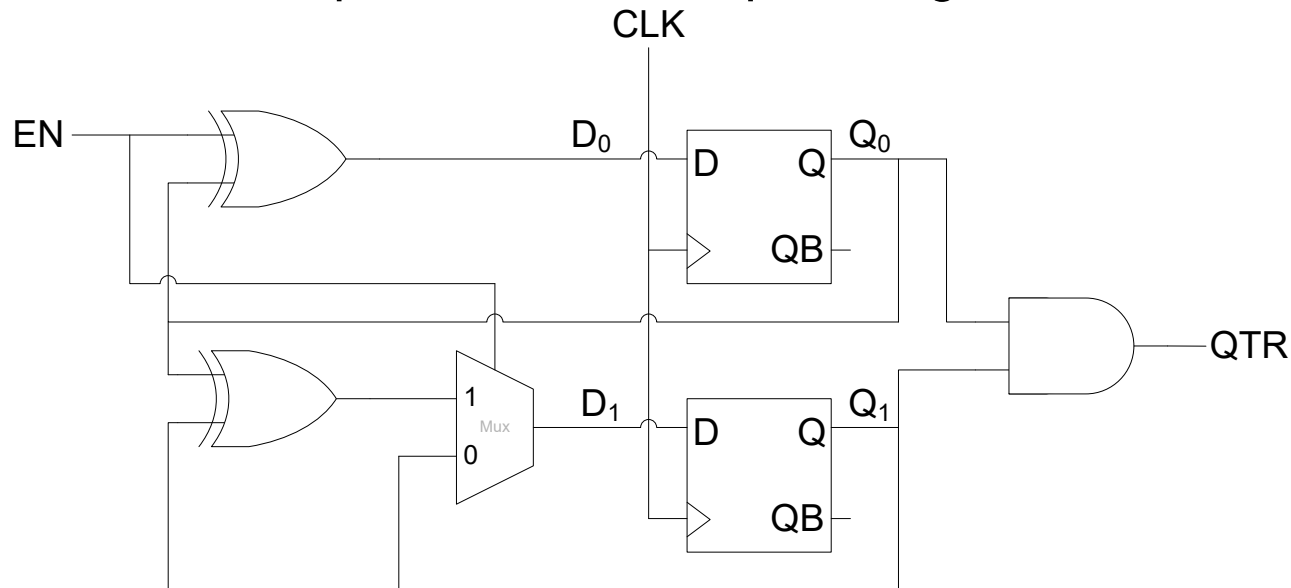- **Transition equations** describe the next state as a function of inputs and current state
  - Generated by substituting the excitation equations into the characteristic equation for the sequential gates



*D FF Characteristic Eqn:*

$$Q^+ = D$$


*Transition Equations:*

$$Q_0^+ = D_0 = EN \oplus Q_0$$

$$Q_1^+ = D_1 = EN \cdot (Q_0 \oplus Q_1) + \overline{EN} \cdot Q_1$$

*This step is trivial when using D FFs!*

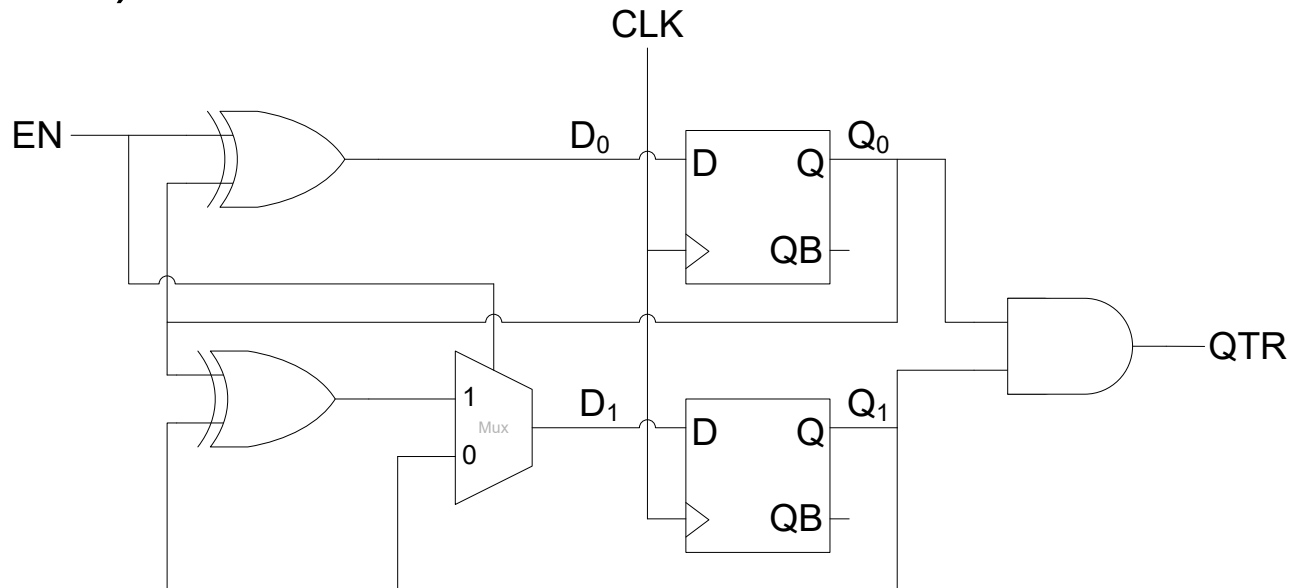
- **Output equations** describe the output signals as a function of the current state (for a Moore machine) or as a function of the current state and inputs (for a Mealy machine)



*Output Equation:*

$$QTR = Q_0 \cdot Q_1$$

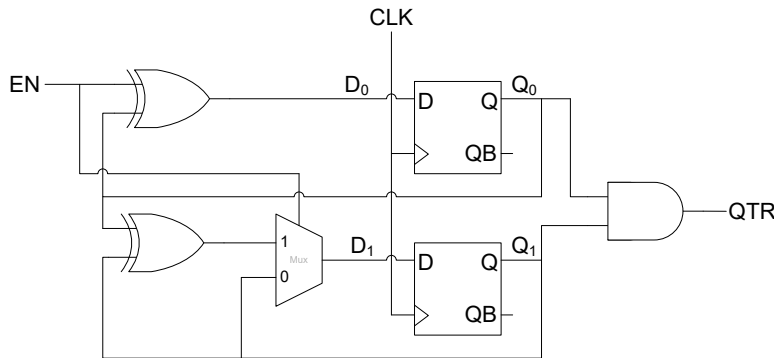- The **transition/output table** shows the next state and output for every current state/input combination
  - Entries of the table are obtained from the transition equations and the output equations



*Transition Equations:*

$$Q_0^+ = D_0 = EN \oplus Q_0$$

$$Q_1^+ = D_1 = EN \cdot (Q_0 \oplus Q_1) + \overline{EN} \cdot Q_1$$

*Output Equation:*

$$QTR = Q_0 \cdot Q_1$$

*Transition/Output Table:*

<i>current state</i>		<i>input</i>		<i>output</i>
		EN		
Q <sub>1</sub>	Q <sub>0</sub>	0	1	QTR
0	0	00	01	0
0	1	01	10	0
1	0	10	11	0
1	1	11	00	1
		$\overline{Q_1^+} \quad Q_0^+$		
		<i>next state</i>		




- **State labels** are a one-to-one mapping from state encodings to state names

Q <sub>1</sub>	Q <sub>0</sub>	State name
0	0	A
0	1	B
1	0	C
1	1	D

- The **state/output table** has the same format as the transition table, but state names are substituted in for state encodings

*Transition/Output Table:*

Q <sub>1</sub>	Q <sub>0</sub>	EN		QTR
		0	1	
0	0	00	01	0
0	1	01	10	0
1	0	10	11	0
1	1	11	00	1
		$Q_1^+ Q_0^+$		

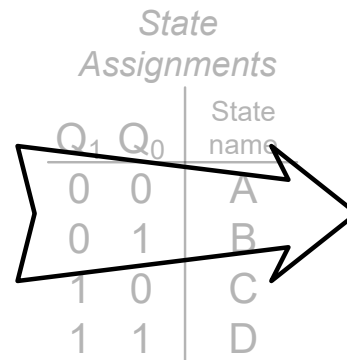

*State/Output Table:*


S	EN		QTR
	0	1	
A	A	B	0
B	B	C	0
C	C	D	0
D	D	A	1
			$S^+$

- A **state diagram** is a graphical representation of the information in the state/output table
- **Nodes** (or vertices) represent states
  - Moore machines: output values are written in state node
- **Arcs** (or edges) represent state transitions
  - Labeled with a **transition expression**
    - when an arc's transition expression evaluates to 1 for a given input combination, that arc is followed to the next state
  - Mealy machines: output values (or expressions) are written on arcs

*State/Output Table:*

S	EN		QTR
	0	1	
A	A	B	0
B	B	C	0
C	C	D	0
D	D	A	1
$S^+$			

*State Diagram:*

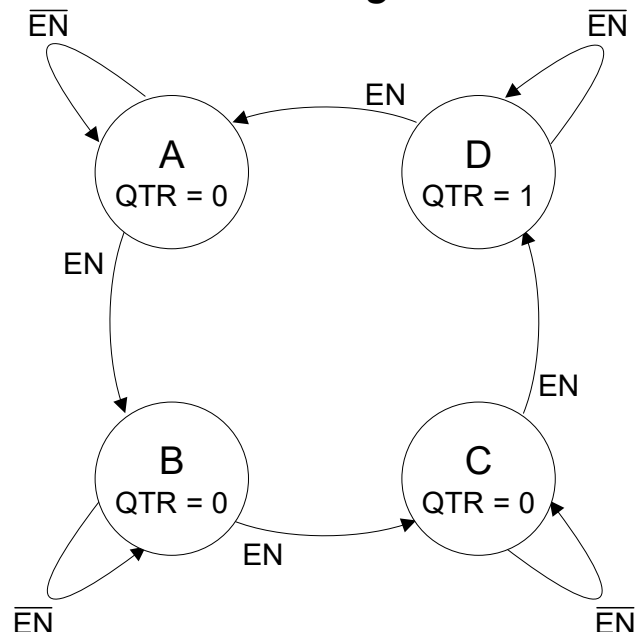



# Sequential Circuit Analysis Recap

- 1) Find the circuit's **excitation equations**
- 2) Using the excitation and characteristic equations, write the circuit's **transition equations**
- 3) Write the circuit's **output equations**
- 4) From the transition and output equations, create the circuit's **transition/output table**
- 5) Create **state labels**
- 6) Using the transition table and state labels, create the **state table**
- 7) (optional) Draw the circuit's **state diagram**