



UM EECS 270 F22

Introduction to Logic Design

7. Binary Arithmetic

addition of unsigned number

Binary Arithmetic



- Representation of positive numbers (old news)
- Binary addition
- Representation of negative numbers
- Binary subtraction
- (Basic) Binary multiplication

Binary Addition



- How do we add two binary numbers?

Just like elementary school!

Decimal:

$$\begin{array}{r} 1 & 1 \\ 4 & 2 & 5 & 9 \\ + & 1 & 8 & 3 & 7 \\ \hline 6 & 0 & 9 & 6 \end{array}$$


This is the *carry out* of the first column, which becomes the *carry in* to the second column

the only difference between adding decimal number and binary number is we only have 2 digits instead of 10.

Binary:

$$\begin{array}{r} 1 & 1 \\ 1 & 0 & 0 & 1 \\ + & 0 & 0 & 1 & 1 \\ \hline 1 & 1 & 0 & 0 \end{array}$$

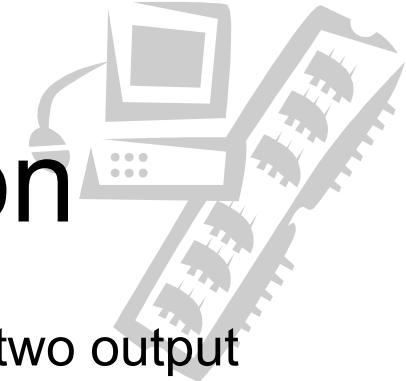- If we have a fixed number of bits (which is usually the case), a carry out of the most significant column indicates that there's not enough bits to hold the sum value. This case is referred to as **overflow**.



C
A
B
S

Addition Implementation

模拟每一位的计算.

- Addition of two 1-bit binary numbers, A and B – requires two output bits, which we'll call S (sum) and C (carry).

A	B	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

two bit answer

$$C = AB$$

只有两个都是1的时候才进位.

$$S = \overline{A}\overline{B} + \overline{AB} = A \oplus B$$

XOR


当A和B相同时不管同0还是同1
Sum都是0. 所以 Sum只有在A,B不同时才为1"

XOR Operation

$$X \oplus Y \equiv X\bar{Y} + \bar{X}Y$$



Implementation:

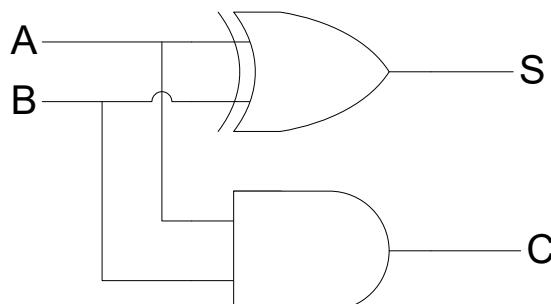


This circuit is called a
Half Adder (HA)

- What if we want to add larger numbers?

- What's missing from HA? 将 HA 的结论向外推导.


相比 HA, 我们少了一个 Carry in.

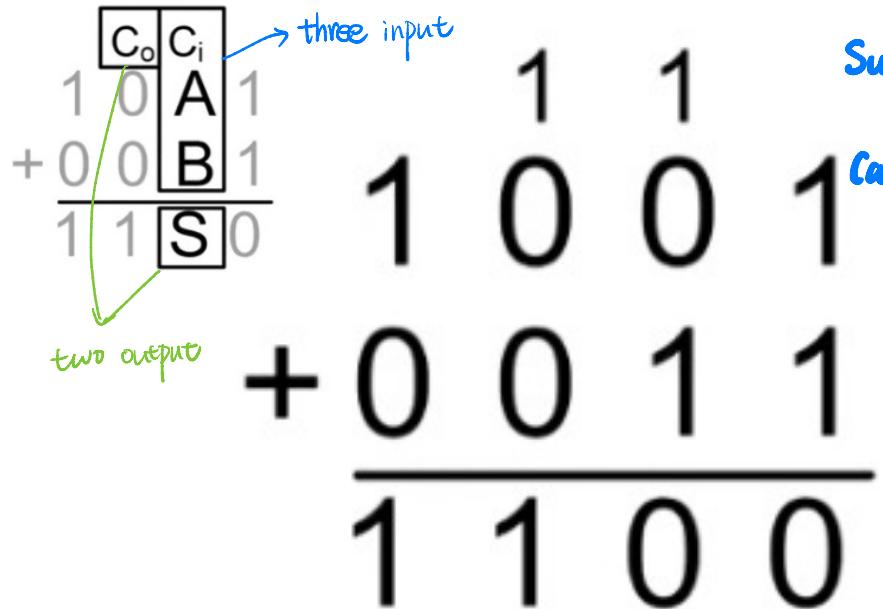

Need to add carry-in (C_i) input!

$$S = \sum_{A,B,C_i} (1,2,4,7)$$

$$C_o = \sum_{A,B,C_i} (3,5,6,7)$$

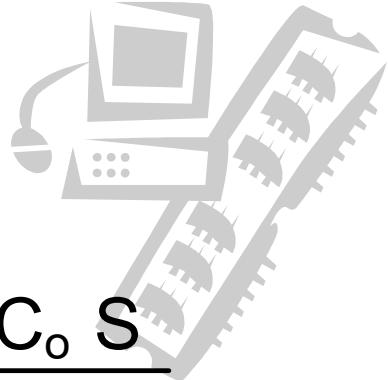

- Sum output:

$$S = \sum_{A,B,C_i} (1, 2, 4, 7)$$



$$S = A'B'C_i + A'BC'_i + AB'C'_i + ABC_i$$

$$S = C_i \left(\underbrace{A'B' + AB}_{\text{xNor}} \right) + C'_i \left(\underbrace{A'B + AB'}_{\text{xor}} \right)$$

$$S = C_i \left(A \oplus B \right)' + C'_i \left(A \oplus B \right)$$

$$S = A \oplus B \oplus C_i$$

- Carry-out output:

$$C_o = \sum_{A,B,C_i} (3,5,6,7)$$



$$C_o = A'BC_i + AB'C_i + ABC'_i + ABC_i$$

$$C_o = A'BC_i + AB'C_i + ABC'_i + ABC_i + ABC_i + ABC_i$$

BC_i AC_i AB

$$C_o = AB + AC_i + BC_i$$

This requires 3 (2-input) AND gates
and 1 (3-input) OR gate.

Can we do any better?

- Carry-out output: A bit of cleverness ...



PFD: $A+B = (A \oplus B) + AB$

$$\begin{aligned}
 & AB + AC_i + BC_i \\
 & = AB + C_i(A + B) \\
 & = AB + C_i((A \oplus B) + AB) \\
 & = AB + C_i(A \oplus B) + ABC_i \\
 & = C_i(A \oplus B) + AB(1 + C_i) \\
 & = AB + (A \oplus B)C_i
 \end{aligned}$$

First, we observe that:

$$\begin{aligned}
 A + B &= (A \oplus B) + AB \\
 C_o &= AB + AC_i + BC_i \\
 &= AB + C_i(A + B) \\
 &= AB + C_i((A \oplus B) + AB) \\
 &= AB + (A \oplus B)C_i + \underline{ABC_i} \quad \text{if } AB = 0 \text{ then } ABC_i = 0 \\
 &= AB + (A \oplus B)C_i
 \end{aligned}$$

↑ and ↑ or ↑ xor ↑ and
new gate we need



$AB + ABC_i = AB(1 + C_i) = AB$

This requires 2 2-input AND gates, a 2-input OR gate, and a 2-input XOR, *but we've already implemented $A \oplus B$ for the Sum output!* So we only require 3 additional gates..


- Final Circuit:

$$S = A \oplus B \oplus C_i$$

$$C_o = AB + (A \oplus B)C_i$$

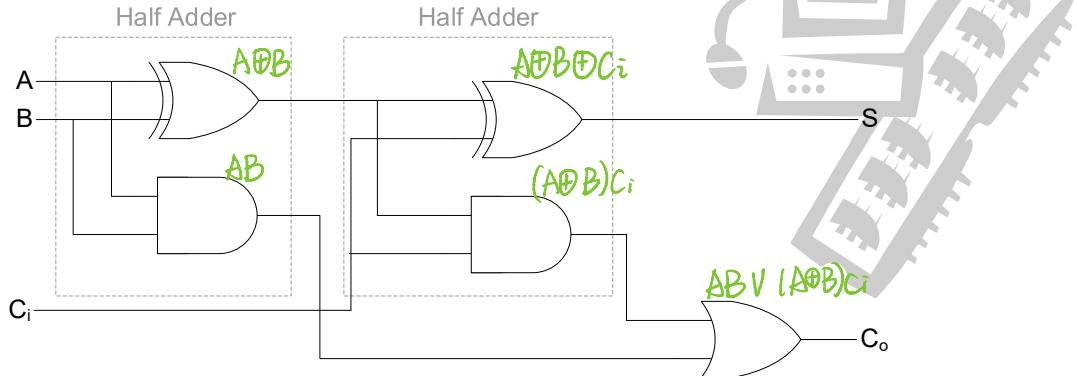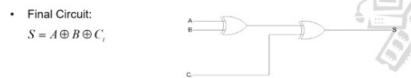

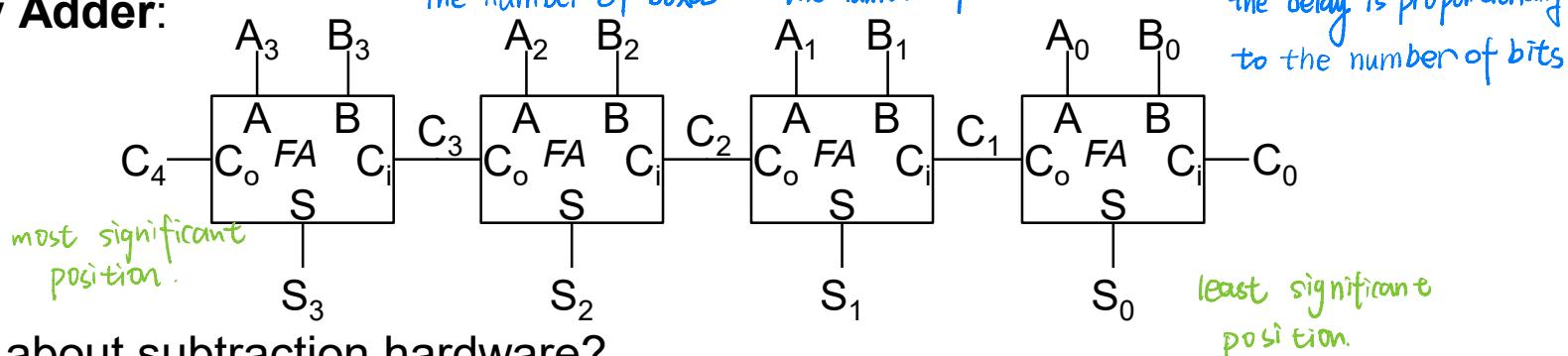- This circuit is called a **Full Adder (FA)**
- After all that design work, we really just have 2 HAs with an OR gate
- To make an n-bit adder, simply cascade Full Adders to make a **Ripple Carry Adder**:



- What about subtraction hardware?

- Could design subtractor hardware using process similar to adder design
- Simpler way: re-use our addition hardware! $A - B = A + (-B)$

$(-B)???$ How do we represent **negative numbers**?

① Half Adder

$$\begin{array}{c|cc} C & \\ \hline A & S : A \oplus B \\ + B & C : AB \\ \hline S & \end{array}$$

② Full Adder

$$\begin{array}{c|cc} C_i & \\ \hline A & S : A \oplus B \oplus C_i \\ + B & C : AB + (A \oplus B)C_i \\ \hline S & \end{array}$$

由两个 Half Adder 和一个 or gate 组成

③ Ripple carry adder

n bits 的数相加，通过
n 个 Full Adder.

Binary Representation of Negative Numbers

- Signed Magnitude:** Numbers consist of a magnitude and a symbol indicating whether the number is positive or negative

– We're used to this:
(-10: “-”: sign, “10”: magnitude)

- In binary, reserve MSB to represent the sign: 0 indicates a positive number, 1 indicates a negative number 1 说明 true, 说明有负号.

- Sign bit position has no weight

- What is the range of numbers that can be represented with 4-bit binary signed-magnitude representation

$$[-7 : 7]$$




- What is the range of numbers that can be represented with n -bit binary signed-magnitude representation?

$$[-(2^{n-1}-1) : 2^{n-1}-1]$$

$n-1$ 是因为若有 n 个 bits, $2^n - 1$ 是因为 MSB 表示符号不
则 MSB 是 $n-1$ position, 表示数位, 所以后面 $n-1$ 个 bit
可以表达比 $1 \dots 2^{n-1}$ 小的数位
Fixed weight 2^{n-1}

Different interpretation of 4 bits

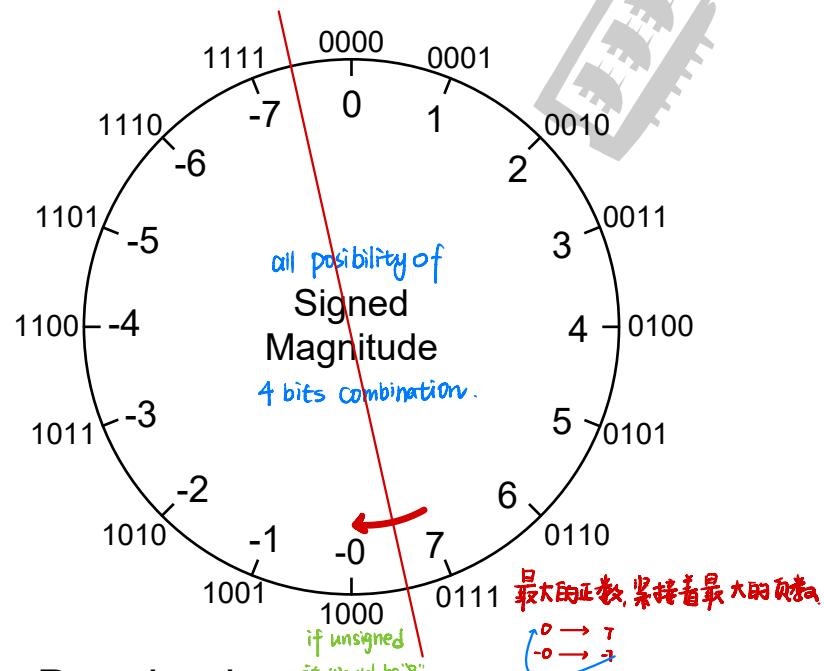

- Drawbacks


- Two representations of 0
- Signed magnitude arithmetic 对于“+”和“-”需要不同的运算方式 and hardware.

need to figure out, subtract a negative from a positive
or
subtract a negative from a positive

Can we do it without checking the sign?

Complement Representations

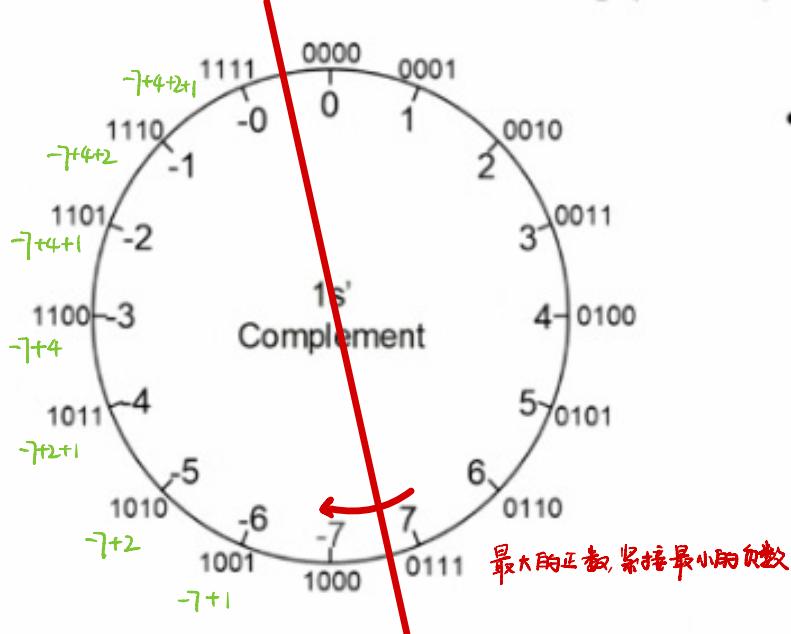- **1s' Complement Representation:** MSB has weight of $-(2^{n-1}-1)$
- To get the representation of a negative number, write the positive representation and complement all bits
- MSB is 0 if number is positive, 1 if number is negative
- What is the range of numbers that can be represented with n -bit 1s' complement representation?




$$[-(2^{n-1}-1) : 2^{n-1}-1]$$

范围取决于最大值和最小值。
最大值: $\underbrace{1 \ 1 \ 1 \dots 1}_{n-1} 2^{n-1}-1$ } 和 sign magnitude 时
最大值: $\underbrace{1 \ 0 \ 0 \dots 0}_{n-1} -2^{n-1}-1$ } 范围完全相同
 \uparrow 这个 MSB 的 weight 不再是 2^{n-1} , 而是 $-(2^{n-1}-1)$.



- Drawbacks
 - Two representations of 0
 - “Messy” arithmetic – must add carry-out of MSB to sum (**end-around carry**)

Complement Representations

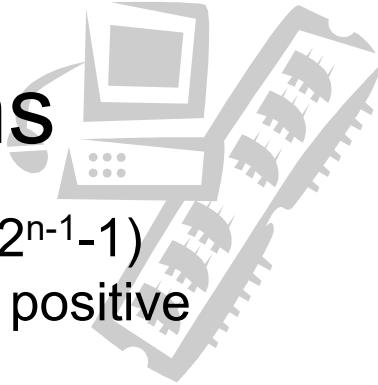

- **1s' Complement Representation:** MSB has weight of $-(2^{n-1}-1)$
- To get the representation of a negative number, write the positive representation and complement all bits

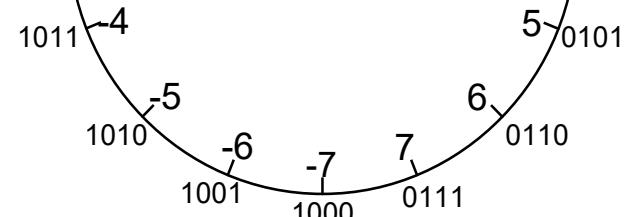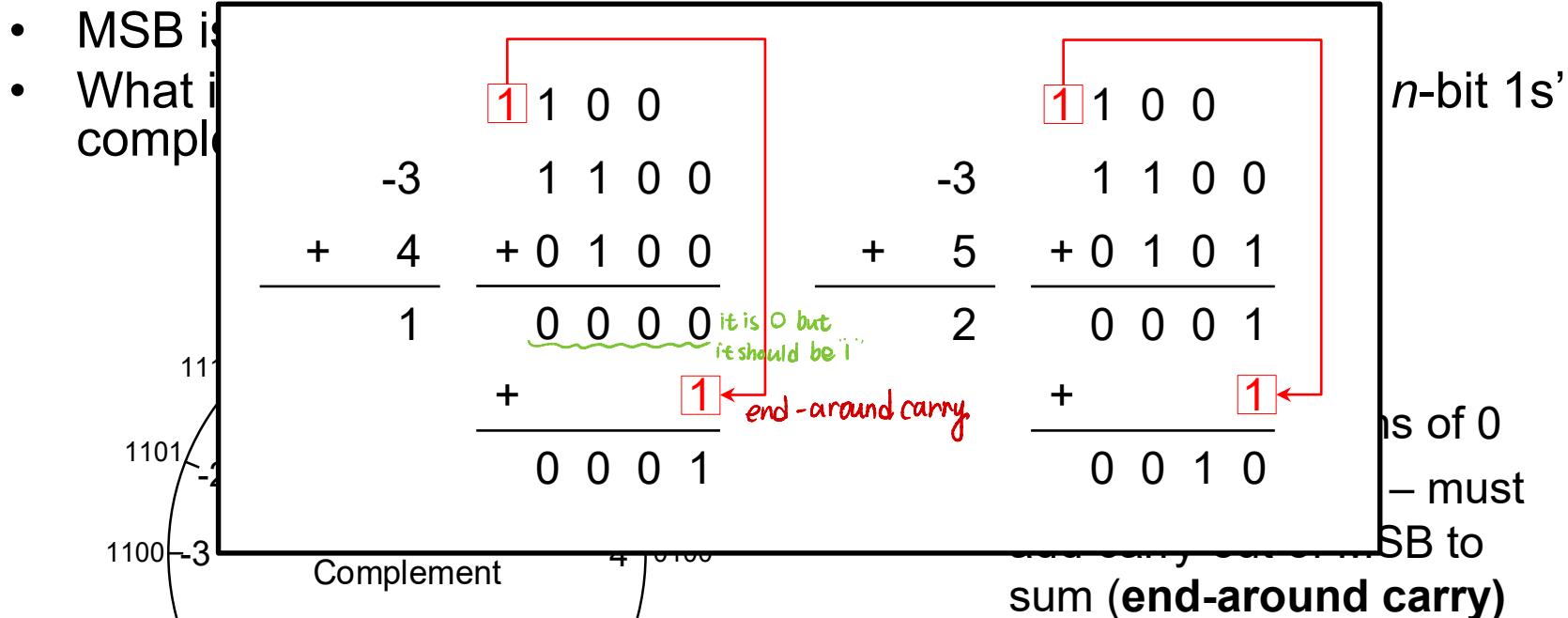Example: $-3: 3 = 0011, -3 = 1100 = 1*(-7) + 1*4 + 0*2 + 0*1$



Abandoned in the 60s in favor of 2's complement....

1's MSB weight is $(-2^{n-1}-1)$

- **2's Complement Representation:** MSB has weight of -2^{n-1}
- To get the negative representation of a number, write the positive representation, complement all bits, and add 1
(ignoring any carry-out of the most significant column)

Example: -4: 4 = 0100

$$\begin{aligned}1011 + 1 &= 1100 \\&= -8 \cdot 1 + 4 \cdot 1 + 0 \cdot 2 + 0 \cdot 1 = -4\end{aligned}$$

the trick over here is we get around the end-around carry by doing the addition when we're doing the implement


- MSB is 0 if number is positive, 1 if number is negative
- What is the range of numbers that can be represented with n -bit 2's complement representation?

我们解决了有两个零的问题.

但新的状态是 range is not symmetric (one more negative)

$$[-(2^{n-1}) : 2^{n-1}-1]$$

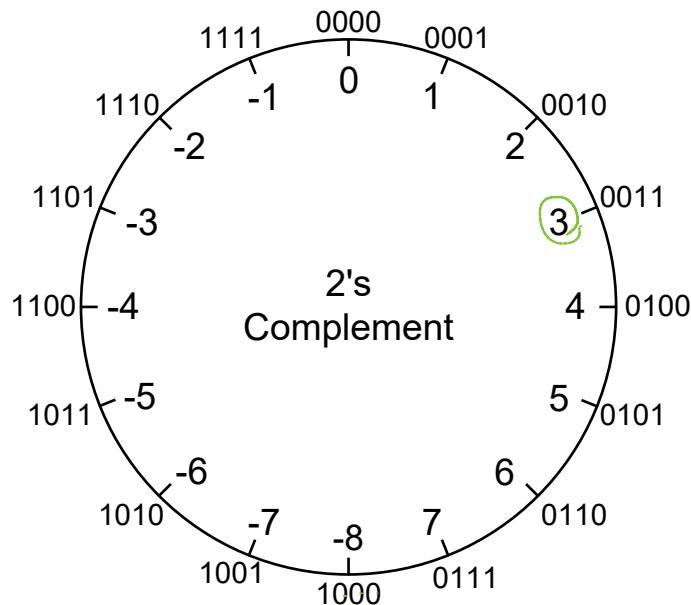但因为如果有 n bits, 就有 2^n 种组合且 negative number 在零左侧. positive number 在零右侧, 则若只有 1 个零, 则正数数量一定不相同. 因为负数比正数多一个



Complement of -8 (1000):

$$0111 + 1 = \underline{\underline{1000}}$$


这是一个错误. 我们想要的是 8:
但这里并没有 -8 的 expression 方法.
但这并不是一个严重的问题, 因为
-8 在 very end of the number range,
并不时常发生.

Complement of 0 (0000):

$$1111 + 1 = \underline{\underline{0000}} \checkmark$$

使用要求

2's Complement Arithmetic

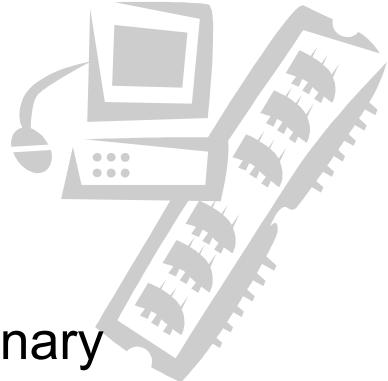

- To add two numbers (positive or negative), use normal binary addition and ignore carry out of most significant column
- Addends and sum should always have the same number of bits

3: 0 0 11

$$-3 : (0011)' + 1 = 1100 + 1 = 1101 = -8 + 4 + 1 = -3$$

$$(-3) + 4$$

$$\begin{array}{r} 1 \ 1 \\ 1 \ 1 \ 0 \ 1 \\ + 0 \ 1 \ 0 \ 0 \\ \hline 0 \ 0 \ 0 \ 1 \end{array}$$

$$5 + (-7)$$

$$\begin{array}{r} 1 \\ 0 \ 1 \ 0 \ 1 \\ + 1 \ 0 \ 0 \ 1 \\ \hline 1 \ 1 \ 1 \ 0 \end{array}$$

$$(-2) + (-3)$$

$$\begin{array}{r} 1 \ 1 \\ 1 \ 1 \ 1 \ 0 \\ + 1 \ 1 \ 0 \ 1 \\ \hline 1 \ 0 \ 1 \ 1 \end{array}$$

- To subtract, take complement of subtrahend and add to minuend:

$$A - B = A + (-B)$$

- Step 1: Generate $(-B)$ – how?
- Step 2: Add - use ripple-carry adder!

Subtraction Using RCA



- Step 1: Generate (-B)
 - Complement bits of B
 - Add 1
- Step 2: Add A to (-B) with RCA - use carry-in of LSB!

Subtract 2 from 6 (6-2):

$$\begin{array}{r}
 +2: 0010 \\
 \begin{array}{c} 1 & 1 & 1 \\ 0 & 1 & 1 \\ + & 1 & 1 \end{array} \xrightarrow{\text{complement}}
 \end{array}
 \begin{array}{r}
 0100 \\
 \hline
 0100
 \end{array}$$

Subtract (-3) from 4 (4 - (-3)):



$$\begin{array}{r}
 -3: 1101 \\
 \begin{array}{c} 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \end{array} \xrightarrow{\text{complement}}
 \end{array}
 \begin{array}{r}
 0111 \\
 \hline
 0111
 \end{array}$$

- 对之前的 ripple-carry adder 的改进, 以适应减法运算.**
- What modifications must be made to a ripple-carry adder to make a ripple-carry adder/subtractor?

- Need a signal to determine whether we're adding or subtracting!
- Complement bits of B (conditionally) → XOR
- Add 1 to B (conditionally) → use carry-in to LSB

A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0


Ripple-carry Adder/Subtractor

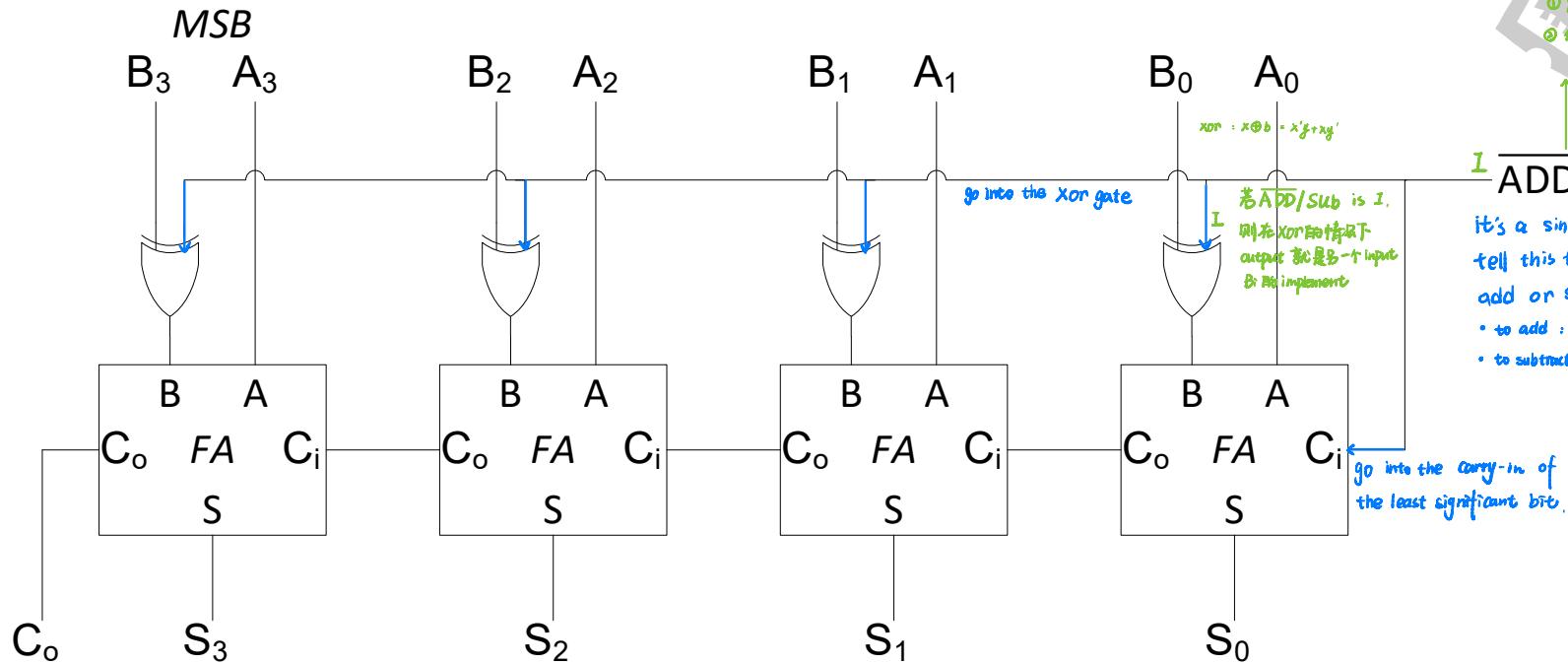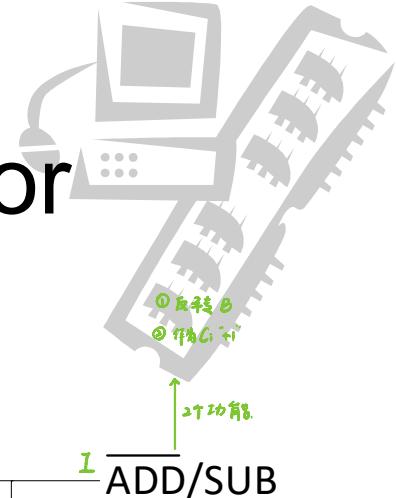

$$\overline{\text{ADD/SUB}} = 0 \rightarrow S = A + B$$

$$\overline{\text{ADD/SUB}} = 1 \rightarrow S = A - B$$

Ripple-carry Adder/Subtractor

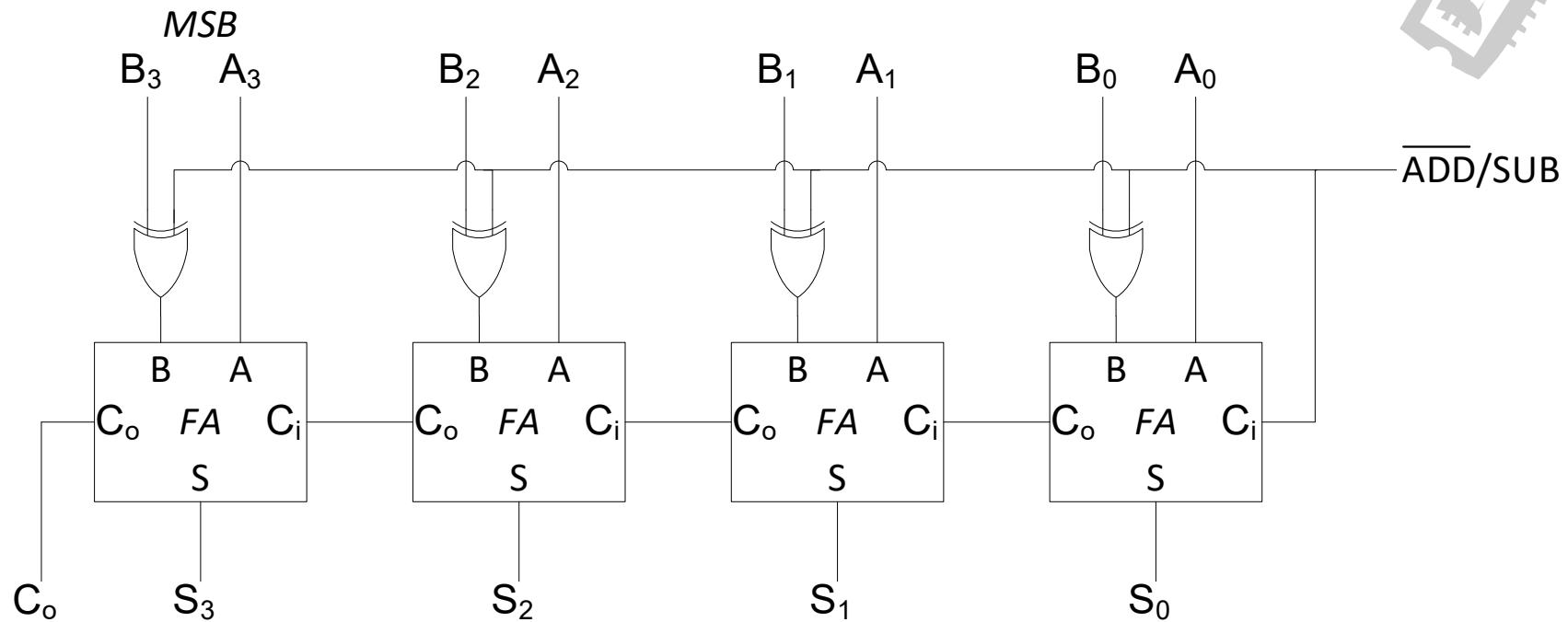

$$\overline{\text{ADD/SUB}} = 0 \rightarrow S = A + B$$

$$\overline{\text{ADD/SUB}} = 1 \rightarrow S = A - B$$



Overflow

- If result of operation is too large for the current number of bits, must notify user that result is invalid

$$\begin{array}{r} 5 + 6 \\ \boxed{0} \ 1 \text{ different} \\ 0 \ 1 \ 0 \ 1 \\ + 0 \ 1 \ 1 \ 0 \\ \hline 1 \ 0 \ 1 \ 1 = -5 \end{array}$$

sign bit


$$\begin{array}{r} (-3) + (-6) \\ \boxed{1} \ 0 \text{ different} \\ 1 \ 1 \ 0 \ 1 \\ + 1 \ 0 \ 1 \ 0 \\ \hline 0 \ 1 \ 1 \ 1 = 7 \end{array}$$

- Addition of two numbers **with different signs** can *never* overflow
- If **sign bits** of addends are the same and *different* from the sign bit of the result, then overflow has occurred
- Equivalently, if the **carry-in** to the **most-significant column** is different from the **carry-out** of the **most-significant column**, overflow has occurred
 - Easily to implement with an XOR gate

Overflow Detection




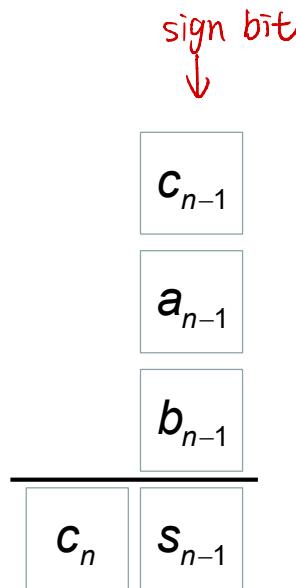ovf = sign bits of addends are the same and *different* from the sign bit of sum



$$s_{n-1} = a_{n-1} \oplus b_{n-1} \oplus c_{n-1}$$
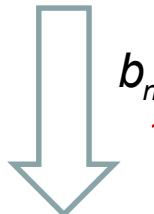
$$c_n = a_{n-1}b_{n-1} + c_{n-1}(a_{n-1} \oplus b_{n-1})$$



$$b_{n-1} = a_{n-1}$$

相加的兩數
sign 相同

$$\begin{aligned} 'y + oy' &= y \\ xy + xy' & \end{aligned}$$

$$s_{n-1} = a_{n-1} \oplus a_{n-1} \oplus c_{n-1} = 0 \oplus c_{n-1} = c_{n-1}$$


$$c_n = a_{n-1}a_{n-1} + c_{n-1}(a_{n-1} \oplus a_{n-1}) = a_{n-1} + c_{n-1} \cdot 0 = a_{n-1}$$

↑
this is what we
ignored before
(现在要看)

$$ovf = a_{n-1} \oplus s_{n-1}$$

$$= \underbrace{c_n}_{\text{the carry out}} \oplus \underbrace{c_{n-1}}_{\text{the carry in the MSB}}$$

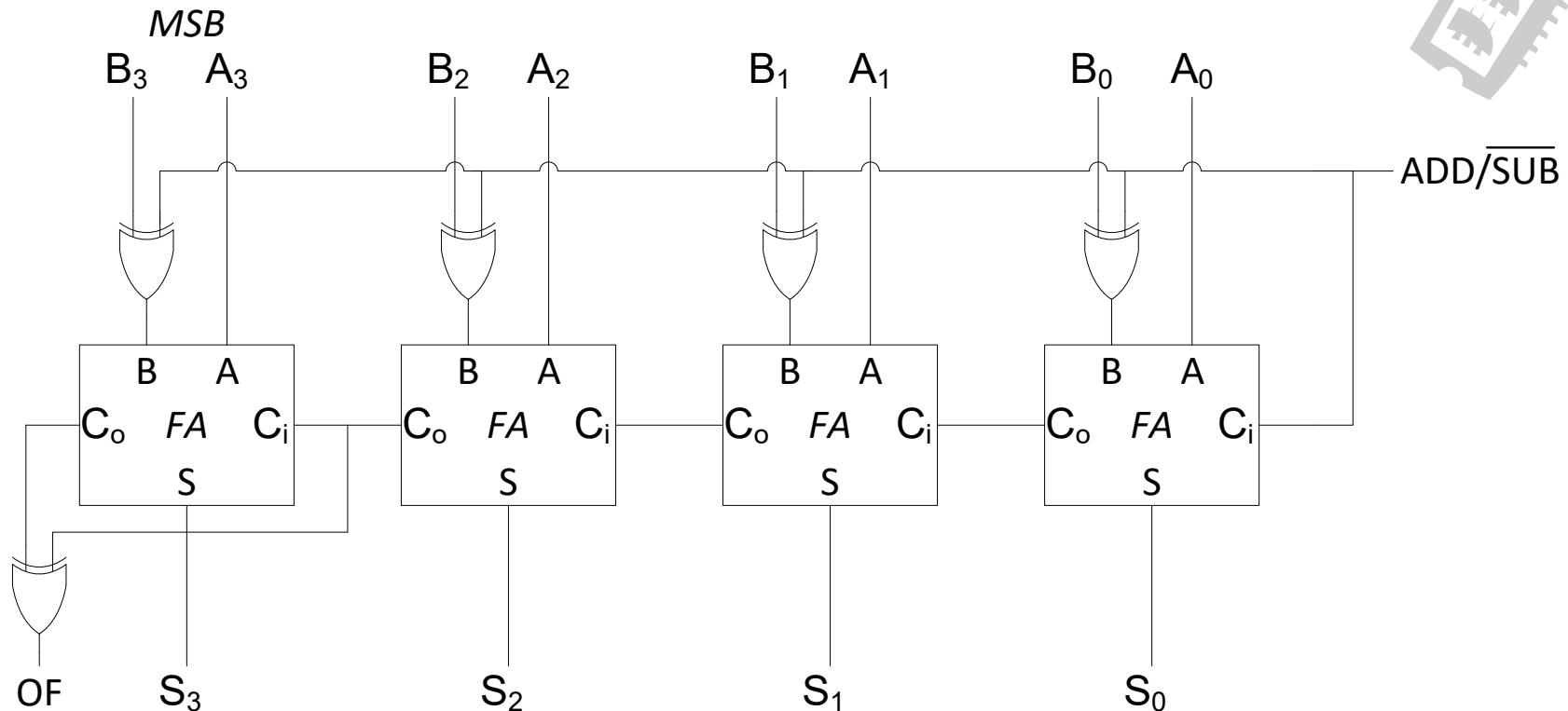Ripple-carry Adder/Subtractor with Overflow Detection



$$\overline{ADD}/\overline{SUB} = 0 \rightarrow S = A + B$$

$$\overline{ADD}/\overline{SUB} = 1 \rightarrow S = A - B$$

$$OF = 1 \rightarrow \text{Overflow}$$

Ones' v. Two's Complement

$$X_{1C} = x_3 x_2 x_1 x_0$$

$$-X_{1C} = x'_3 x'_2 x'_1 x'_0$$

x	$1 - x = x'$
0	$1 - 0 = 1$
1	$1 - 1 = 0$

$$X_{2C} = x_3 x_2 x_1 x_0$$

$$-X_{2C} = x'_3 x'_2 x'_1 x'_0 + 0001$$

$$\begin{array}{r}
 \begin{array}{|c|c|c|c|} \hline
 1 & 1 & 1 & 1 \\ \hline
 \end{array} \\
 - \begin{array}{|c|c|c|c|} \hline
 x_3 & x_2 & x_1 & x_0 \\ \hline
 \end{array} \\
 \hline
 \begin{array}{|c|c|c|c|} \hline
 x'_3 & x'_2 & x'_1 & x'_0 \\ \hline
 \end{array}
 \end{array}$$

$$-X_{1C} = \boxed{x'_3 \quad x'_2 \quad x'_1 \quad x'_0}$$

$$\begin{array}{r}
 \begin{array}{|c|c|c|c|c|} \hline
 1 & 0 & 0 & 0 & 0 \\ \hline
 \end{array} \\
 - \begin{array}{|c|c|c|c|} \hline
 x_3 & x_2 & x_1 & x_0 \\ \hline
 \end{array} \\
 \hline
 \begin{array}{|c|c|c|c|} \hline
 x'_3 & x'_2 & x'_1 & x'_0 \\ \hline
 \end{array}
 \end{array}$$


$$-X_{2C} = \boxed{x'_3 \quad x'_2 \quad x'_1 \quad x'_0} + 0001$$

$$-X_{1C} = 15 - X_{1C}$$


$$-X_{2C} = 16 - X_{2C}$$

$$-X_{1C} = (2^n - 1) - X_{1C}$$

$$-X_{2C} = 2^n - X_{2C}$$

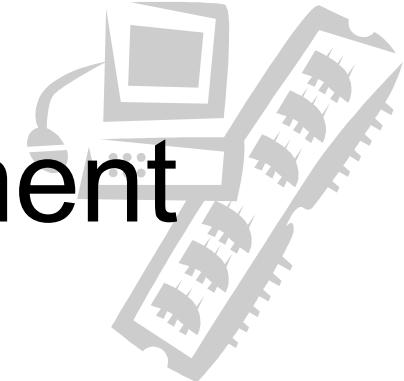

2's Complement Overflow

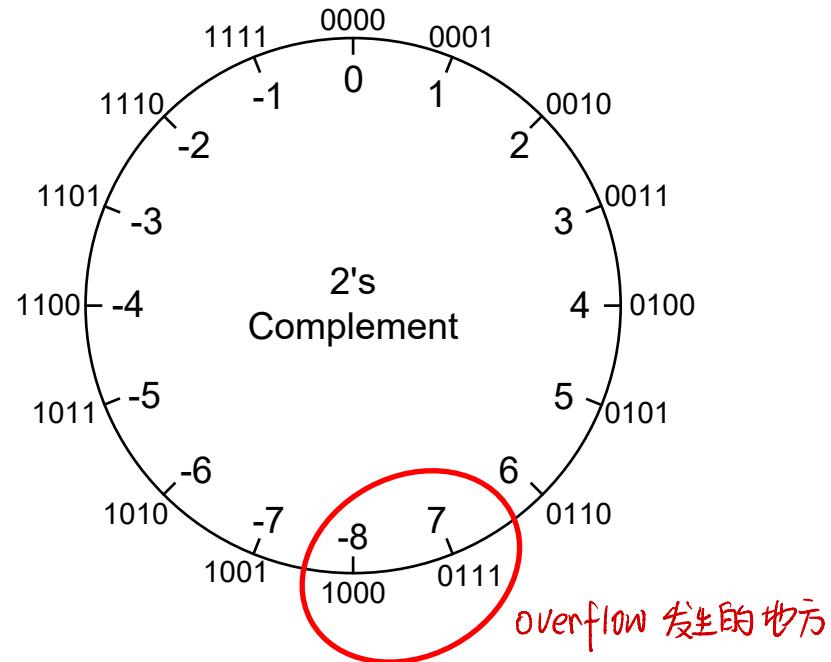

No Overflow: $A \geq 0, B < 0, A + B \in [-8, 7]$


Positive Overflow: $A, B \geq 0, A + B > 7$

Negative Overflow: $A, B < 0, A + B < -8$

2's Complement Overflow


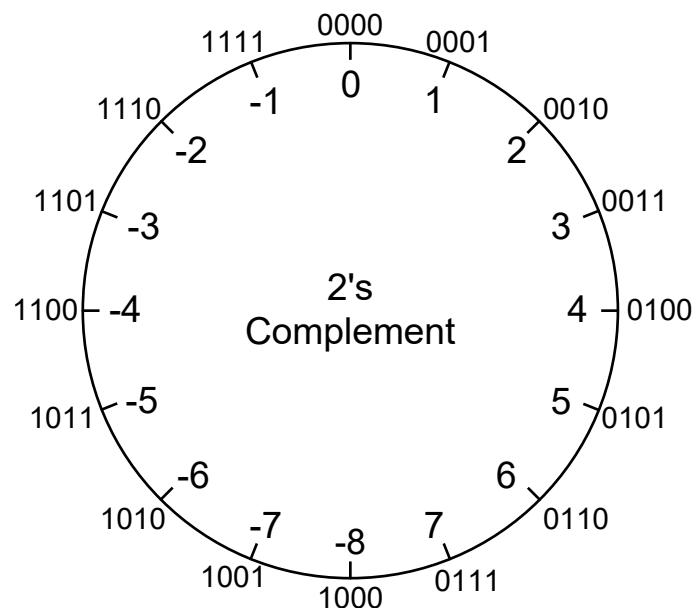
$$\begin{array}{r} -8 : 1000 \\ b : 0110 \end{array}$$



$-8 + (-6) = -14$


overflow

1	0	0	1	1
1	0	0	0	0
1	0	0	0	1

= 0 0 1 0

X incorrect answer

2's Complement Overflow

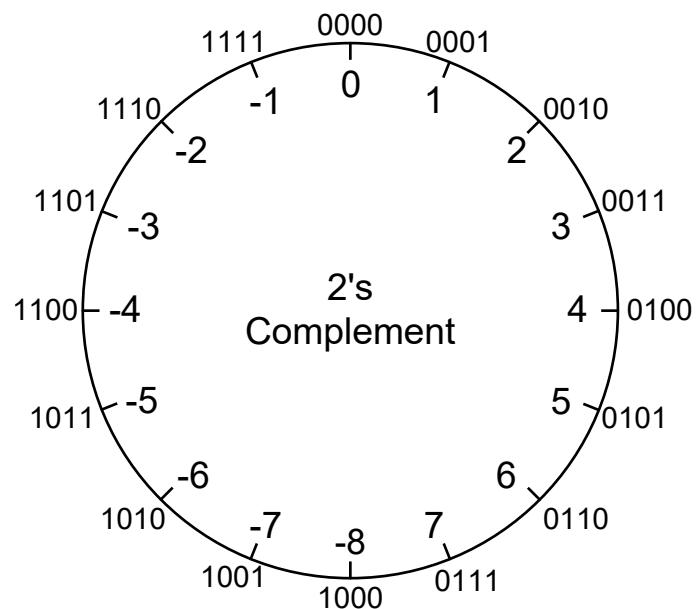

$$3 + 2 = 5$$



3: 0011

2: 0010

since we are adding



0	0	1	0	0
0	0	1	1	
+	0	0	1	0
=				
0	1	0	1	

2's Complement Overflow

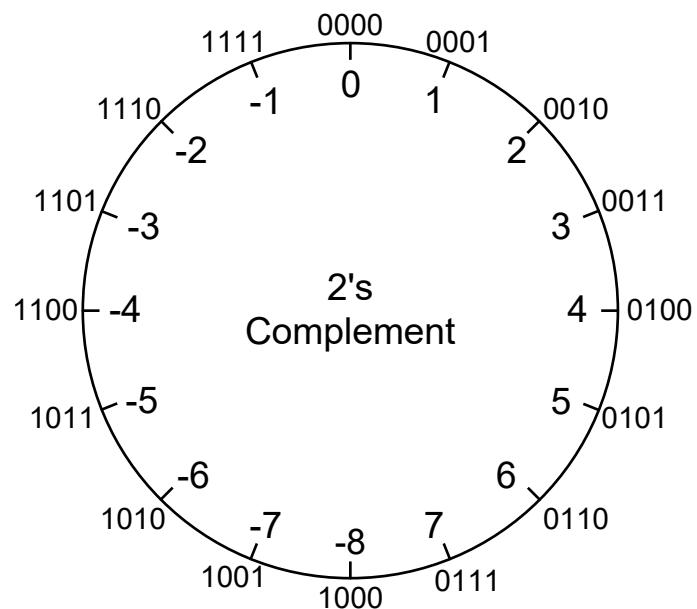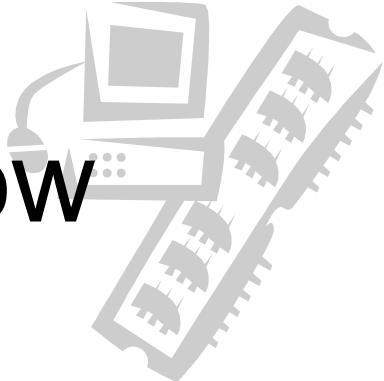

$$\begin{array}{r} \boxed{} \quad \boxed{} \quad \boxed{} \quad \boxed{} \quad \boxed{} \\ + \quad \boxed{} \quad \boxed{} \quad \boxed{} \quad \boxed{} \\ \hline = \quad \boxed{} \quad \boxed{} \quad \boxed{} \quad \boxed{} \end{array}$$

2's Complement Overflow

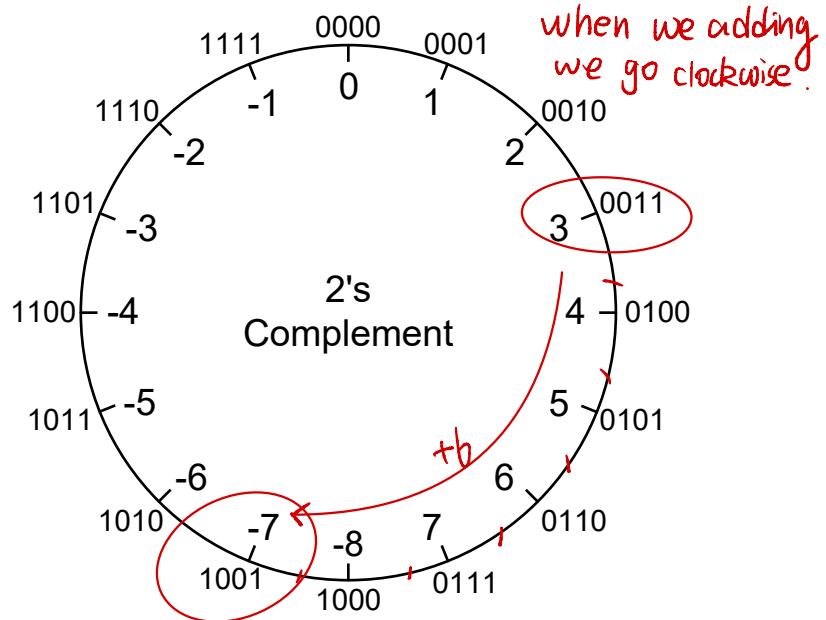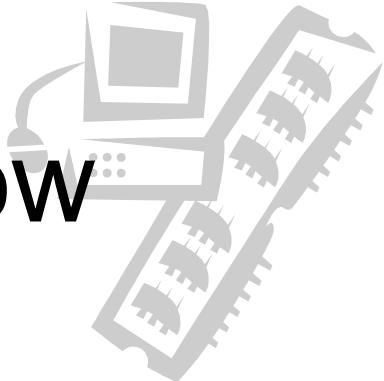

$3 + 6 = 9$
3: 0011
6: 0110

这两个不同引起 overflow

0	1	1	0	0
0	0	1	1	
0	1	1	0	
1	0	0	1	x

=

In Class Exercise



Perform the following operations in the same fashion as the ripple-carry adder/subtractor. Note whether or not overflow has occurred.

Subtract 7 from 3 ($3 - 7$)

$$\begin{array}{r} +7 \quad 0111 \\ & \text{complement} \\ & \begin{array}{r} 111 \\ 0011 \\ +1000 \\ \hline 1100 \end{array} \end{array}$$


Subtract -4 from 5 ($5 - (-4)$)

$$\begin{array}{r} -4: \quad 1100 \\ & \text{complement} \\ & \begin{array}{r} 1111 \\ 0101 \\ +0011 \\ \hline 1001 \end{array} \end{array}$$

Carry-in to most-significant column is equal to carry-out of most-significant column
→ No overflow

Carry-in to most-significant column is not equal to carry-out of most-significant column → Overflow

Derivative Arithmetic Operations

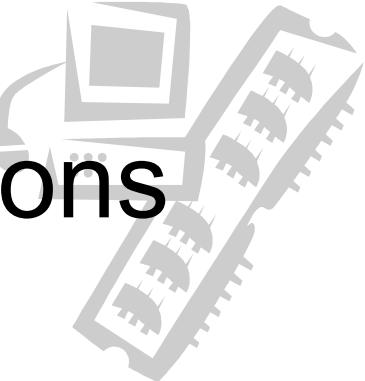

- Incrementing (+1) and decrementing (-1)
 - Start with an adder and simplify the circuit
- Multiplying an unsigned by a power of two
 - Shift to the left
- Dividing an unsigned by a power of two
 - Shift to the right
- Multiplication: $A * B$
 - Same algorithm as in decimal
 - Partial products: multiply A by digits of B
 - Add up all partial products
- Division A/B: ?