

Post-lab

1. List the inputs and outputs for the next-state logic (remember that next state is a function of sensor inputs, current state, and count). How many rows and columns would this truth table have? (5 points)

input: sensor input : E, W, NL, EL, CLK, reset each of them are 1 bits 6 bits
 current state : I have 9 state. Each of them is 4 bits 4 bits
 counter : from 0 to 2. 2bits 2 bits } 12 bits

output: output : ETL WTL NTL ELTL 4bits

$$\text{Columns} = \# \text{input} + \# \text{output} = 12 \text{ bits} + 4 \text{ bits} = 16 \text{ bits.}$$

$$\text{Lines} = 2^{\# \text{input}} = 2^{12}$$

2. List the inputs and outputs for the output logic, not including the counter.(Hex outputs are a function of current state.) How many rows and columns would this truth table have? (5 points)

inputs: current state, We have 9 states. So we need to 4 bits.

outputs : 4 7-bits HEX & Timer /HEX Board 7 segments: $4 \times 7 = 28$ bits.

$$\text{column} = \text{inputs} + \text{outputs} = 28 + 4 = 32$$

$$\text{row} = 2^{\# \text{inputs}} = 2^4$$

3. How many states are there in your FSM? How many D flip-flops are required to hold all of these states? Do you have unused states? If so, how many? (5 points).

I have 9 states in my FSM

I need 4 D flip-flops.


Yes I have unused states. $16 - 9 = 7$ 7 state unused.

4. If you had used a one-hot encoding, how many D flip-flops would you need? (5 points).

One-hot means each time only one bit is "1", the rest in "0".

So I have 9 state, means I have 9 bits which means I need 9 D flip-flops.

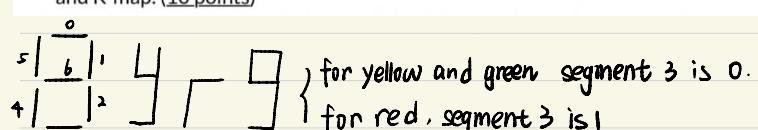5. Each segment of the 7 segment displays is the output of a logic function of the current state. Determine the logical function for segment 3 of the W, 7-segment display. Provide the minimal SOP and K-map. (10 points)



since I have 9 states. So I have S₀, S₁, S₂, S₃. (4bits).

$$f(\text{segment } 3) = S_1 + S_2 + Y_1 + Y_3 + Y_4 + Y_5$$

$$S_1: 0001 \quad S_2: 00 \quad S_3: 0001 \quad S_4: 11 \quad S_5: 10$$

$$S_6: 0010 \quad S_7: 0000 \quad S_8: 0100 \quad S_9: 1100 \quad S_{10}: 1000$$

$$Y_1: 0011 \quad Y_2: 0101 \quad Y_3: 0001 \quad Y_4: 0110 \quad Y_5: 0111$$

$$Y_6: 0101 \quad Y_7: 0111 \quad Y_8: 0011 \quad Y_9: 1011 \quad Y_{10}: 1111$$

$$Y_{11}: 0110 \quad Y_{12}: 0110 \quad Y_{13}: 1110 \quad Y_{14}: 1010 \quad Y_{15}: 1010$$

$$Y_{16}: 0111 \quad Y_{17}: 0111 \quad Y_{18}: 1110 \quad Y_{19}: 1010 \quad Y_{20}: 1010$$

$$f(\text{segment } 3) = S_2S_3' + S_0'S_2$$

