

EECS 370 - Lecture 11

Multi-Cycle Data Path



Reminder

- If you're watching lectures asynchronously...
- I have studio recordings
 - Much better quality than lecture recordings
 - I won't walk off screen, etc




Extra Lecture Section

- Professor Gokul has moved his lecture section to 10:30 am in EWRE
 - Feel free to attend those if that time works better for you


Announcements

- P2
 - P2a due Thursday
 - P2L due in a month
- HW 2
 - Posted, due next week
- Lab 5 due Wed
- Midterm Exam
 - Thu Oct 12th, 6-8 pm (next week)
 - Sample exams on website
 - You can bring 1 sheet (double sided is fine) of notes
 - We will provide LC2K encodings + ARM cheat sheet

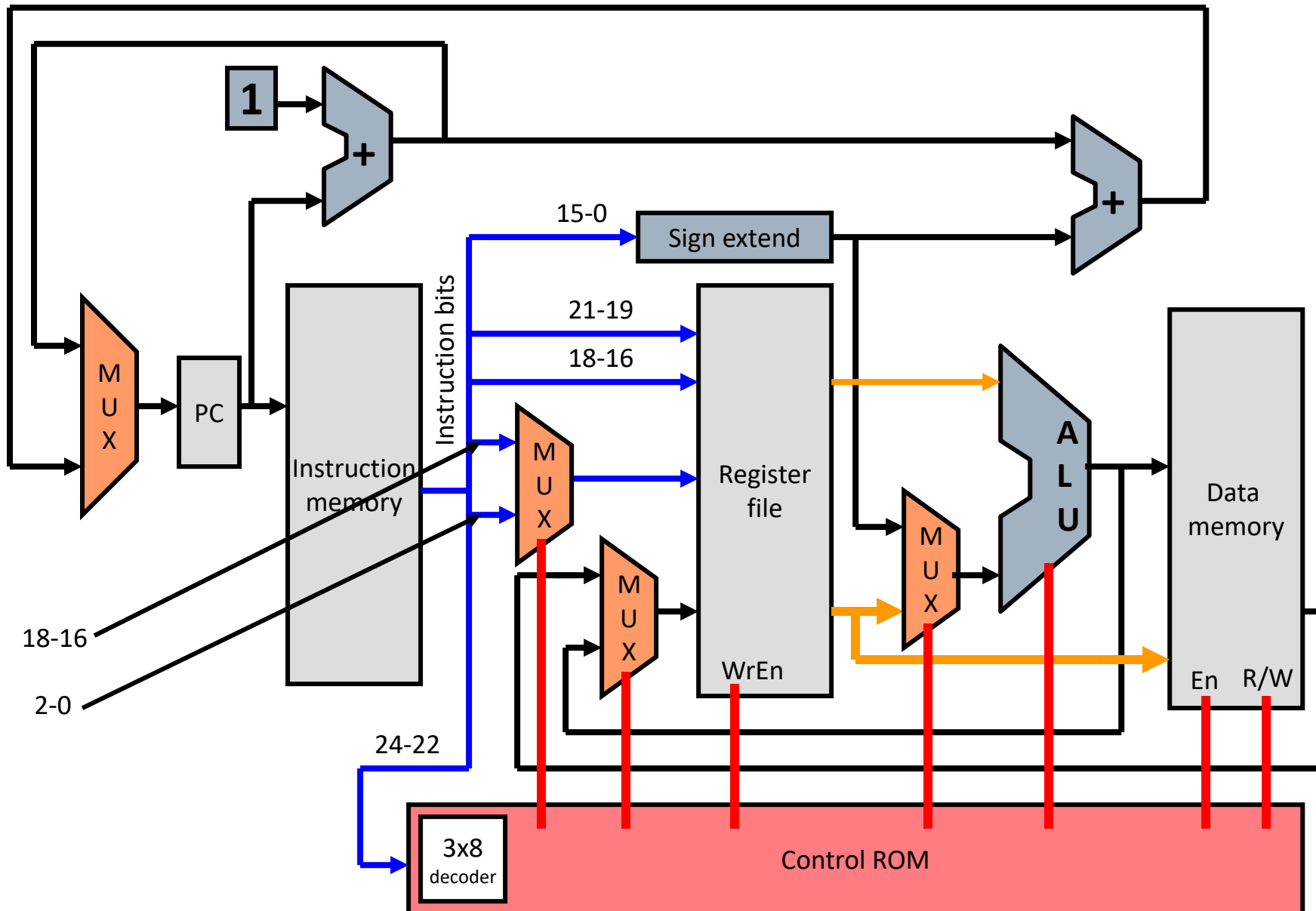
LC2K Single-Cycle Datapath Implementation



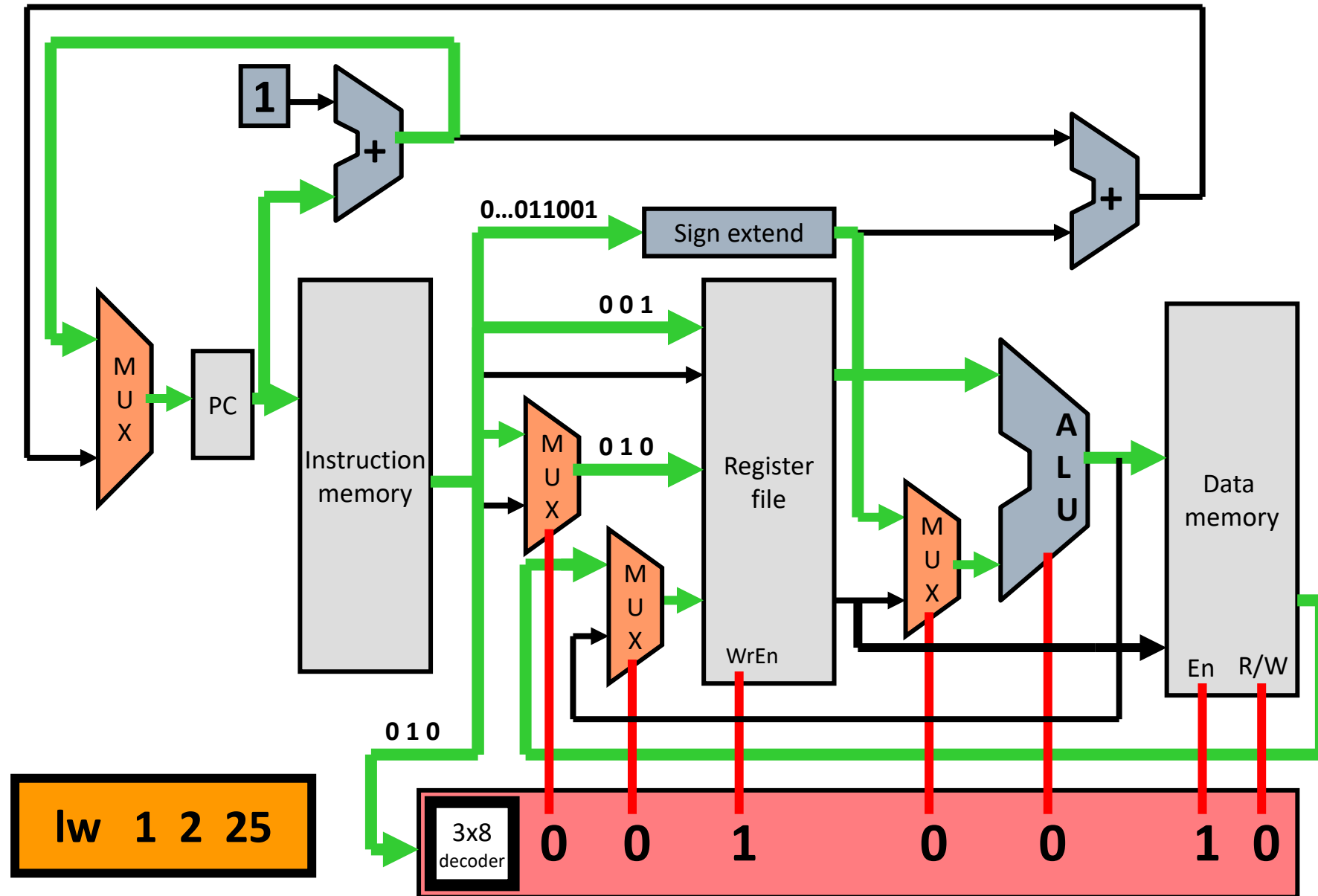
Executing a **LW** Instruction on LC2Kx Datapath



Executing a **SW** Instruction

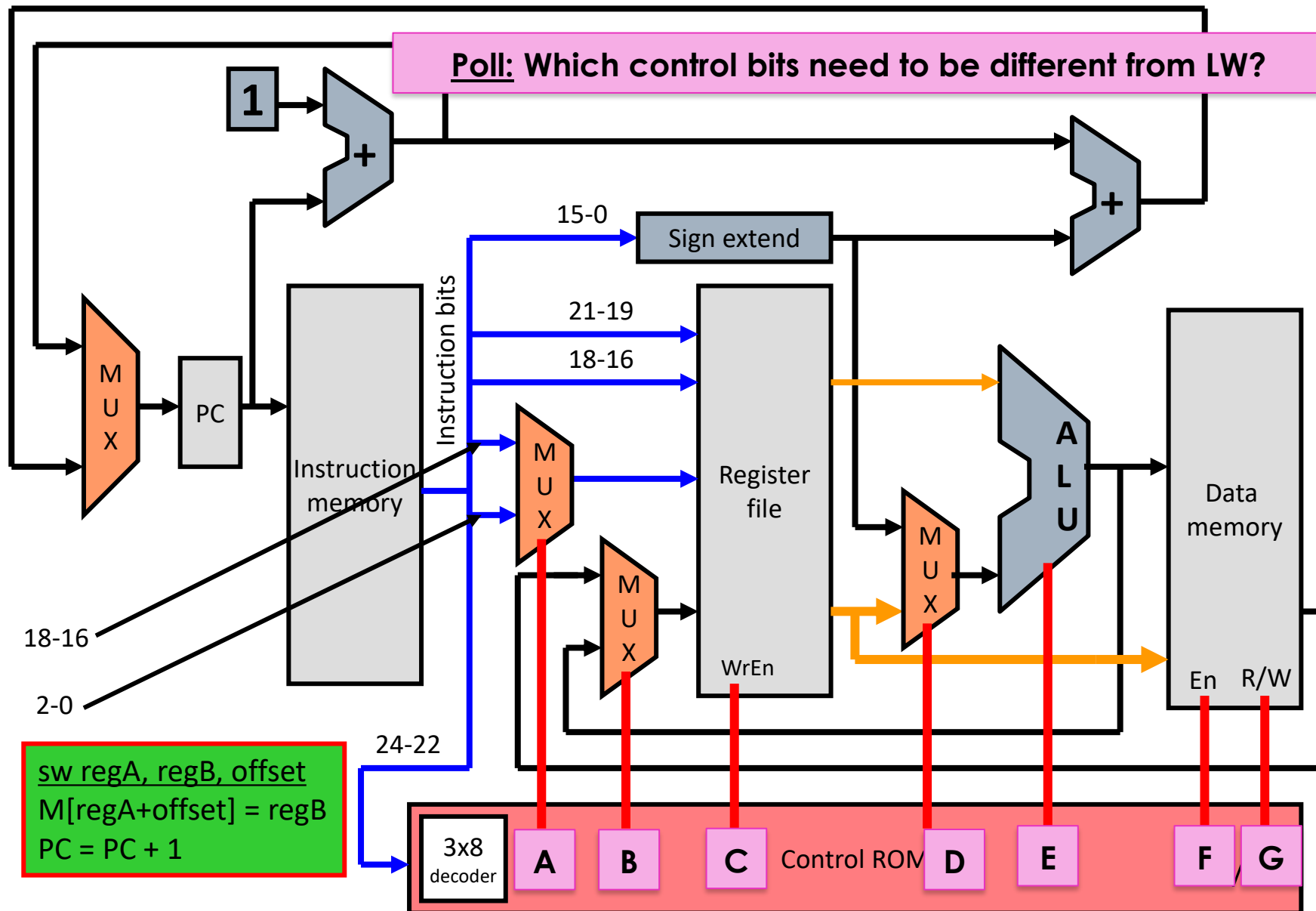


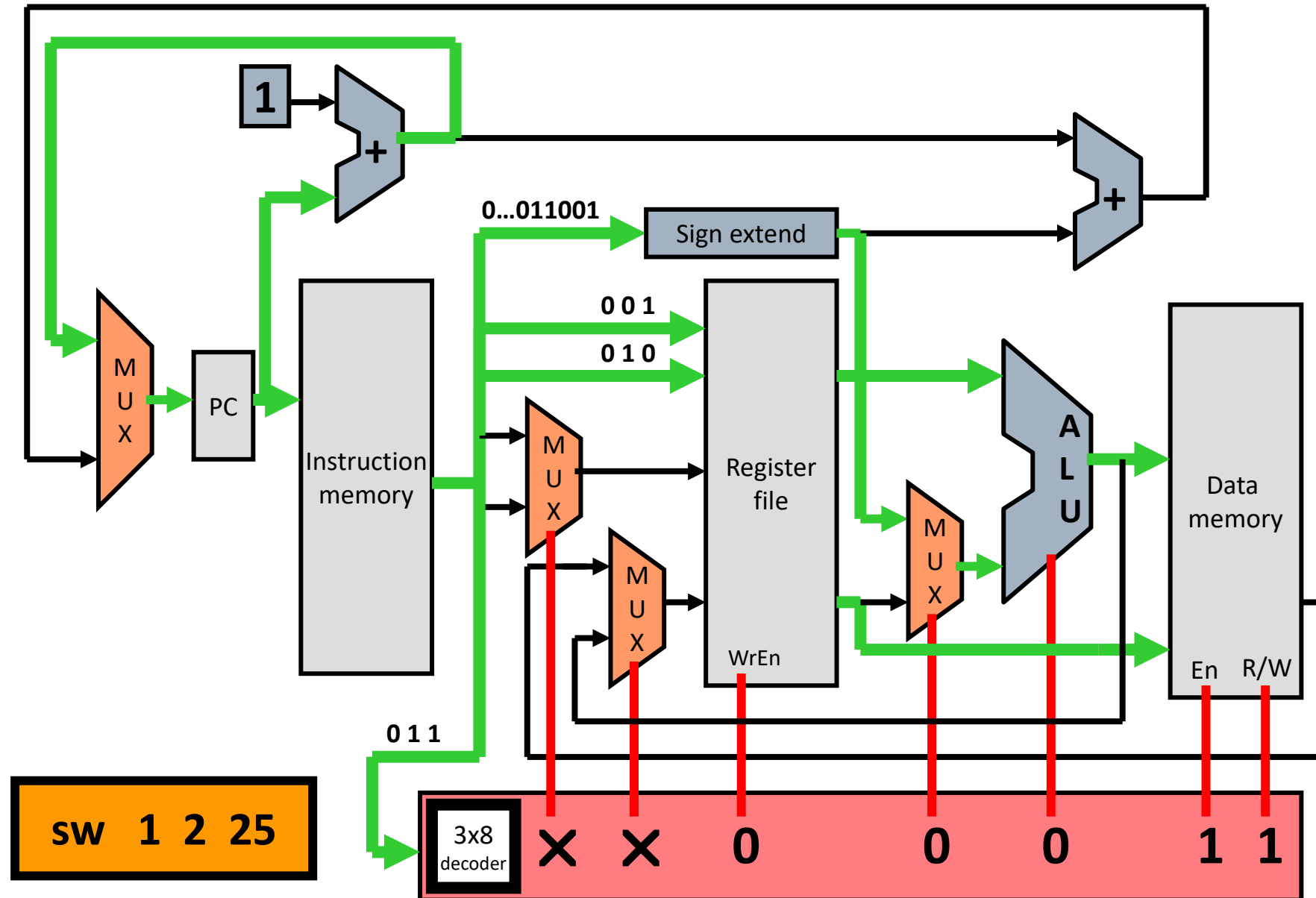Executing a **SW** Instruction on LC2Kx Datapath




Executing a **BEQ** Instruction

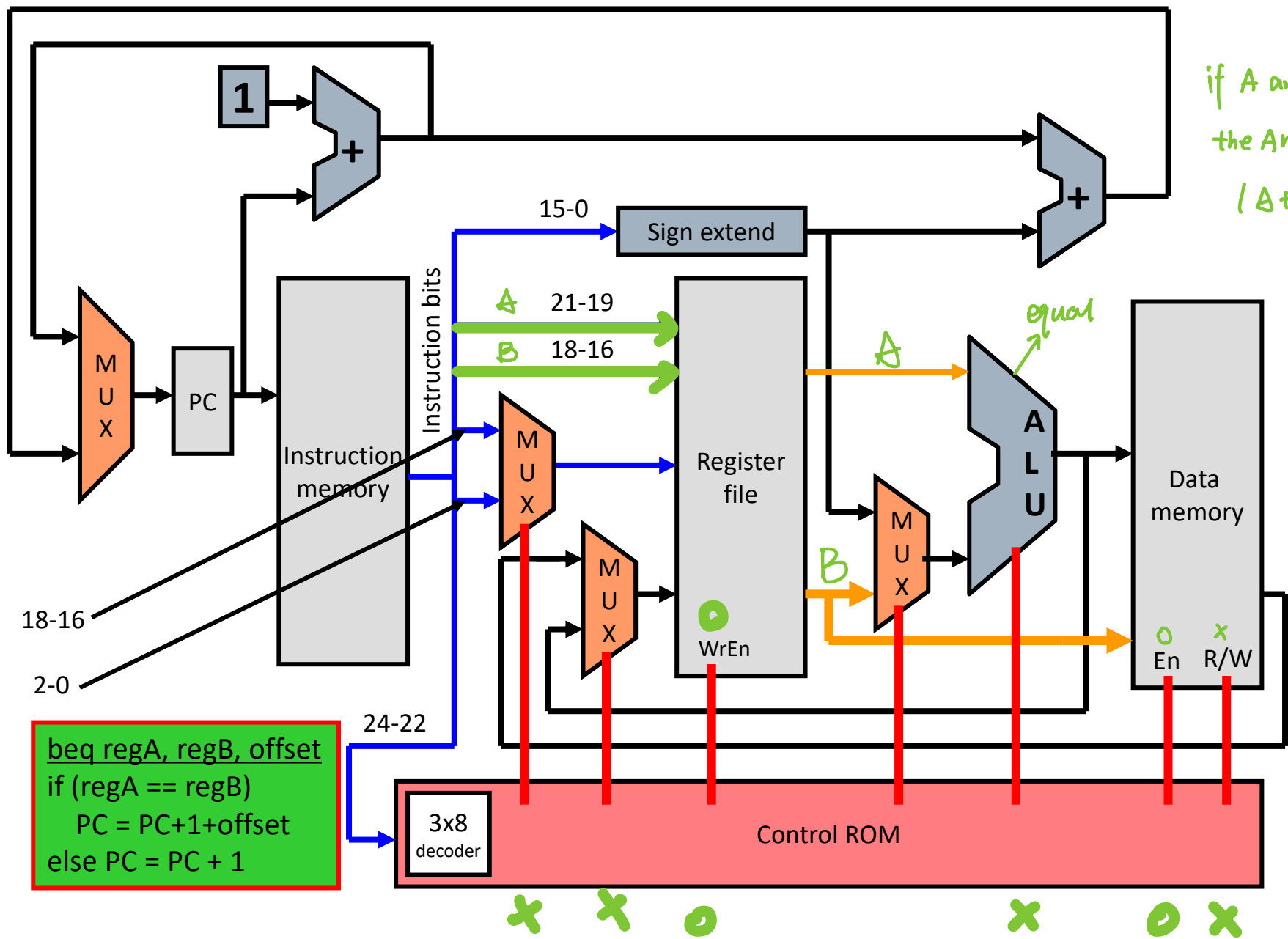if $regA = regB$. \longrightarrow Branch to $PC+1+offset$.
 if $regA \neq regB$. \longrightarrow Branch to $PC+1$.




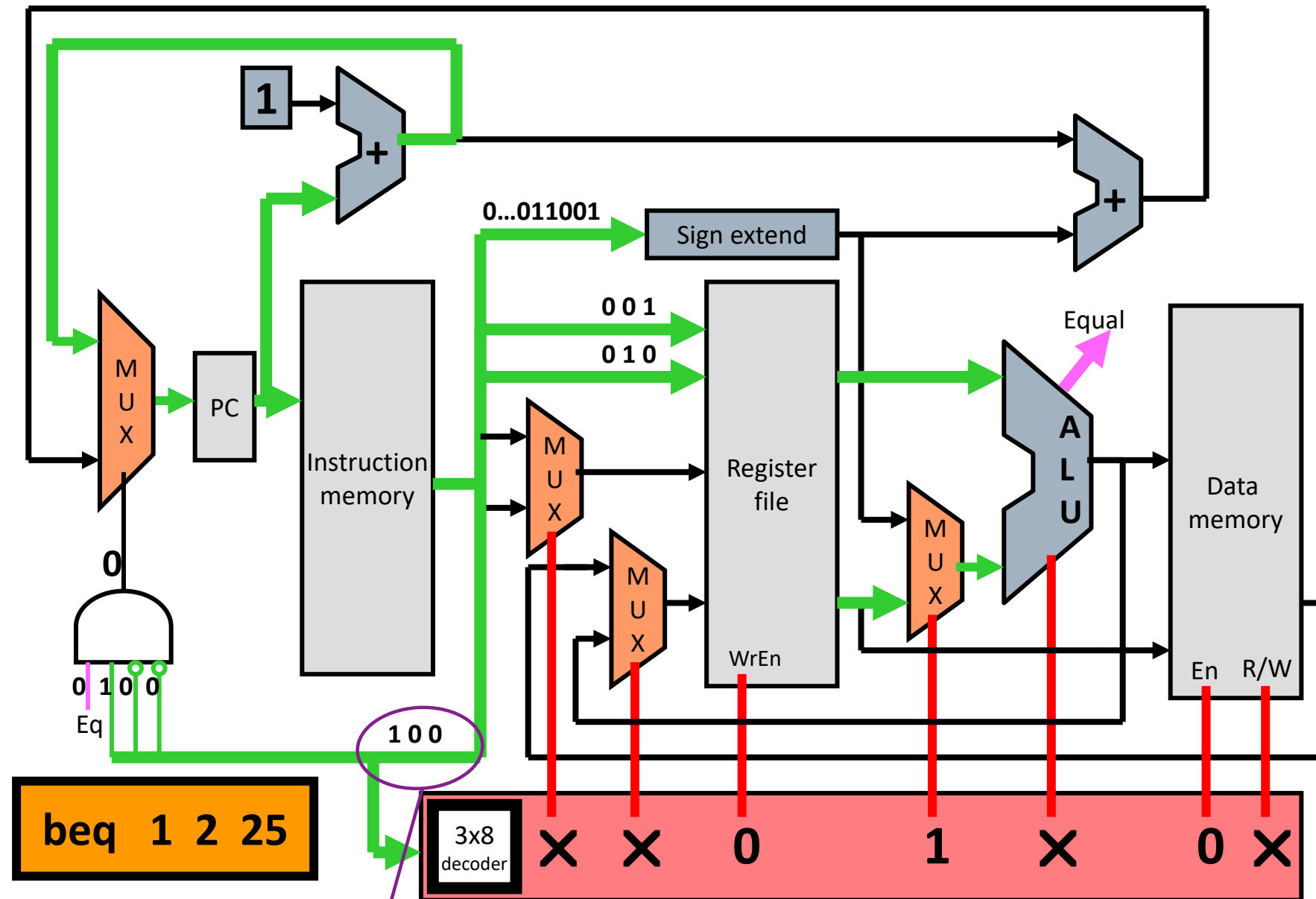Executing “not taken” **BEQ** Instruction on LC2K Datapath



opcode的信息不足以用于判断是 $PC=PC+1$ 还是 $PC=PC+1+\text{offset}$.

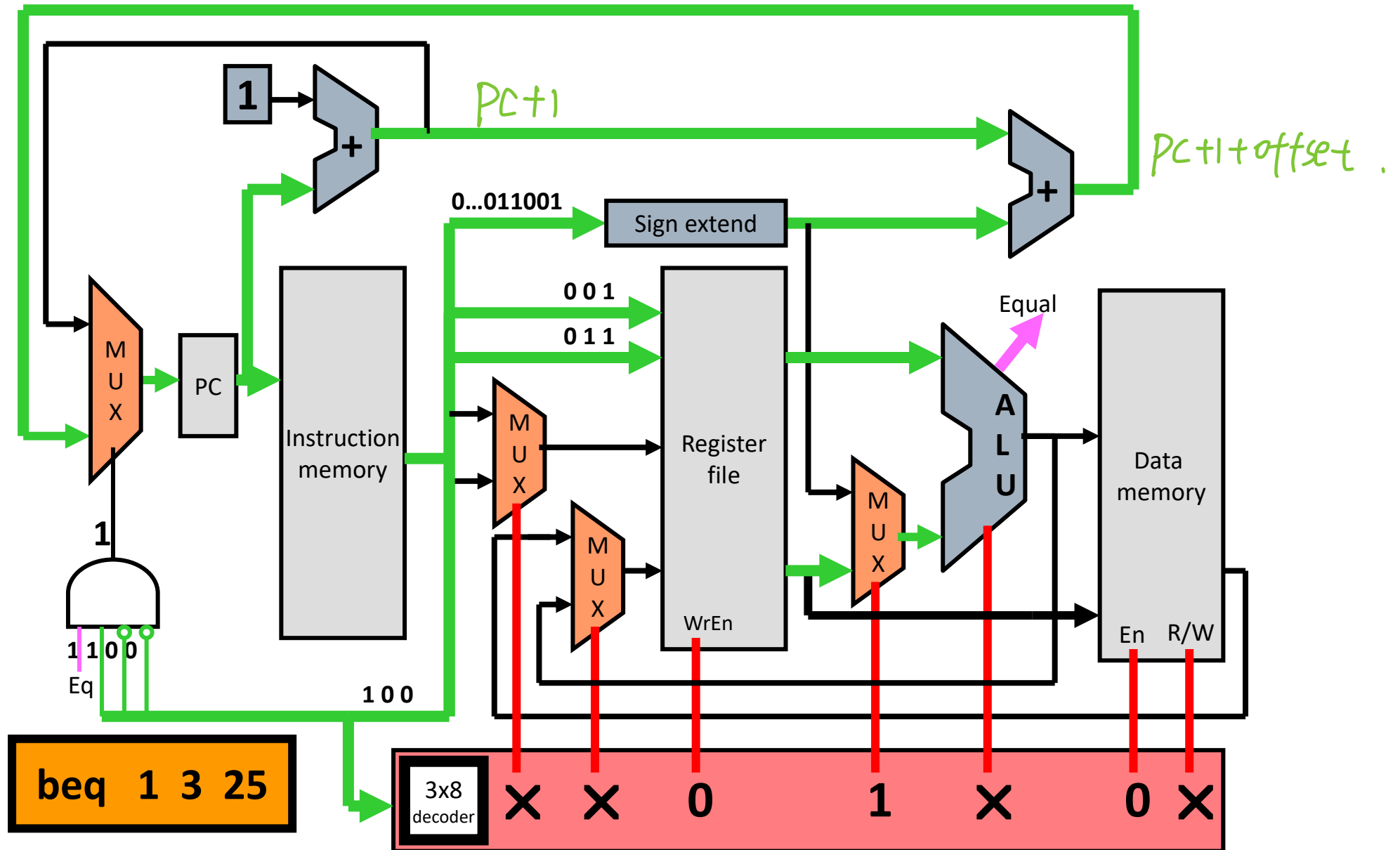Executing a “taken” **BEQ** Instruction on LC2K Datapath




So Far, So Good


- Every architecture seems to have at least one "ugly" instruction
 - Something that doesn't elegantly fit in with the hardware we've already included
- For LC2K, that ugly instruction is JALR
 - It doesn't fine into our nice clean datapath
- To implement JALR we need to:
 - Write PC+1 into regB
 - Move regA into PC
- Right now there is:
 - No path to write PC+1 into a register
 - No path to write a register to the PC




Executing a **JALR** Instruction

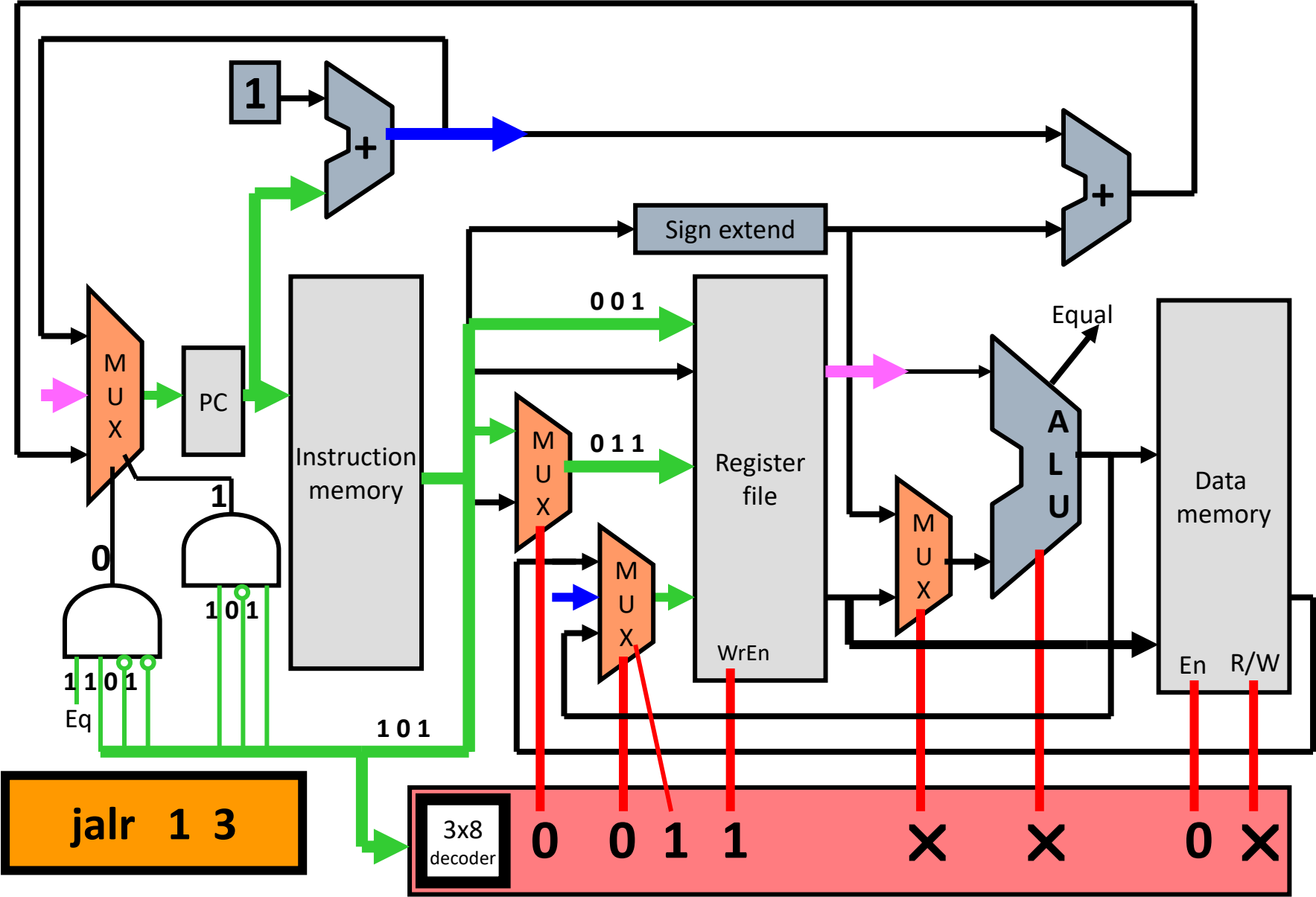

What if regA = regB for **JALR**?

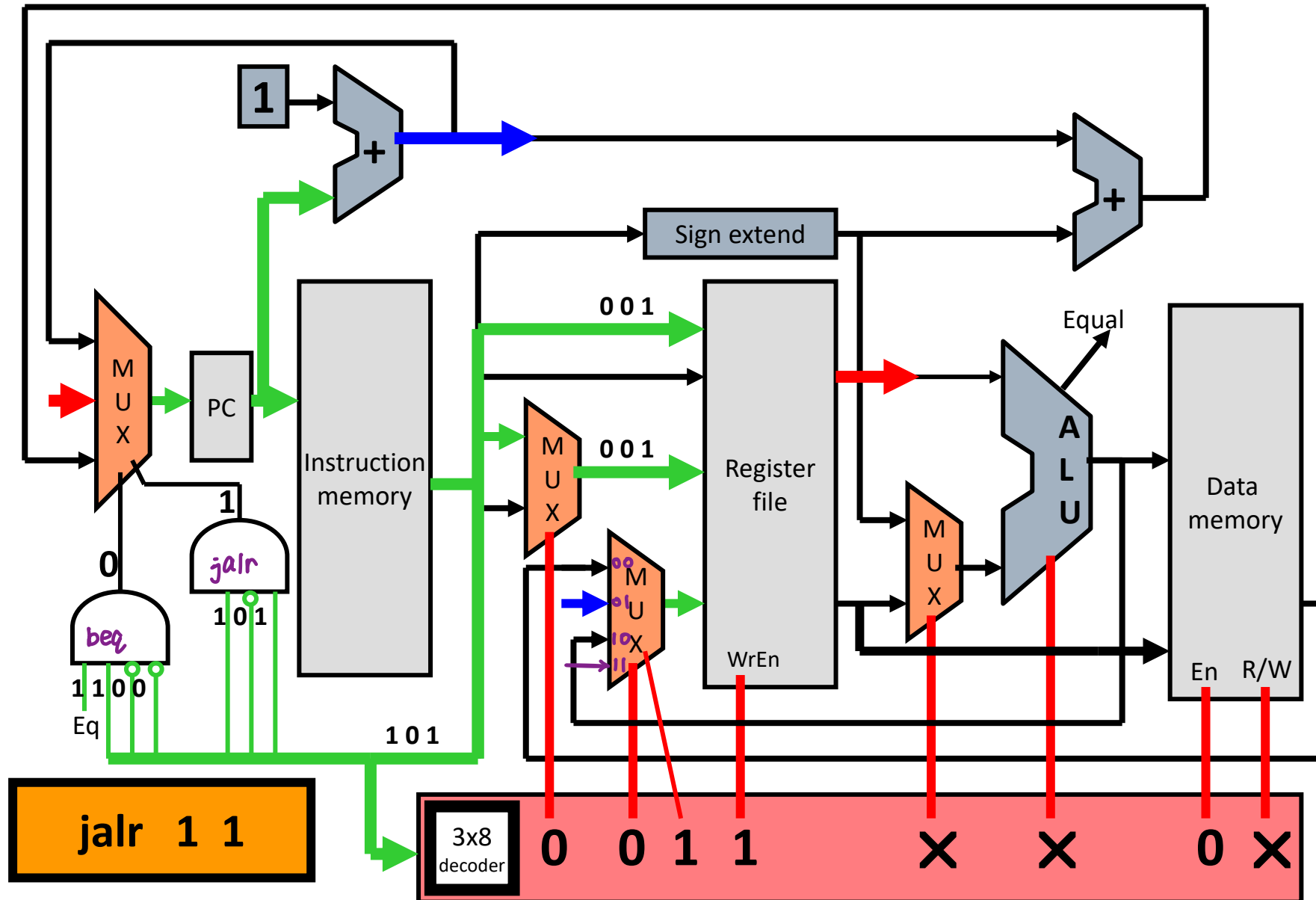

Changes for **JALR 1 1** Instruction

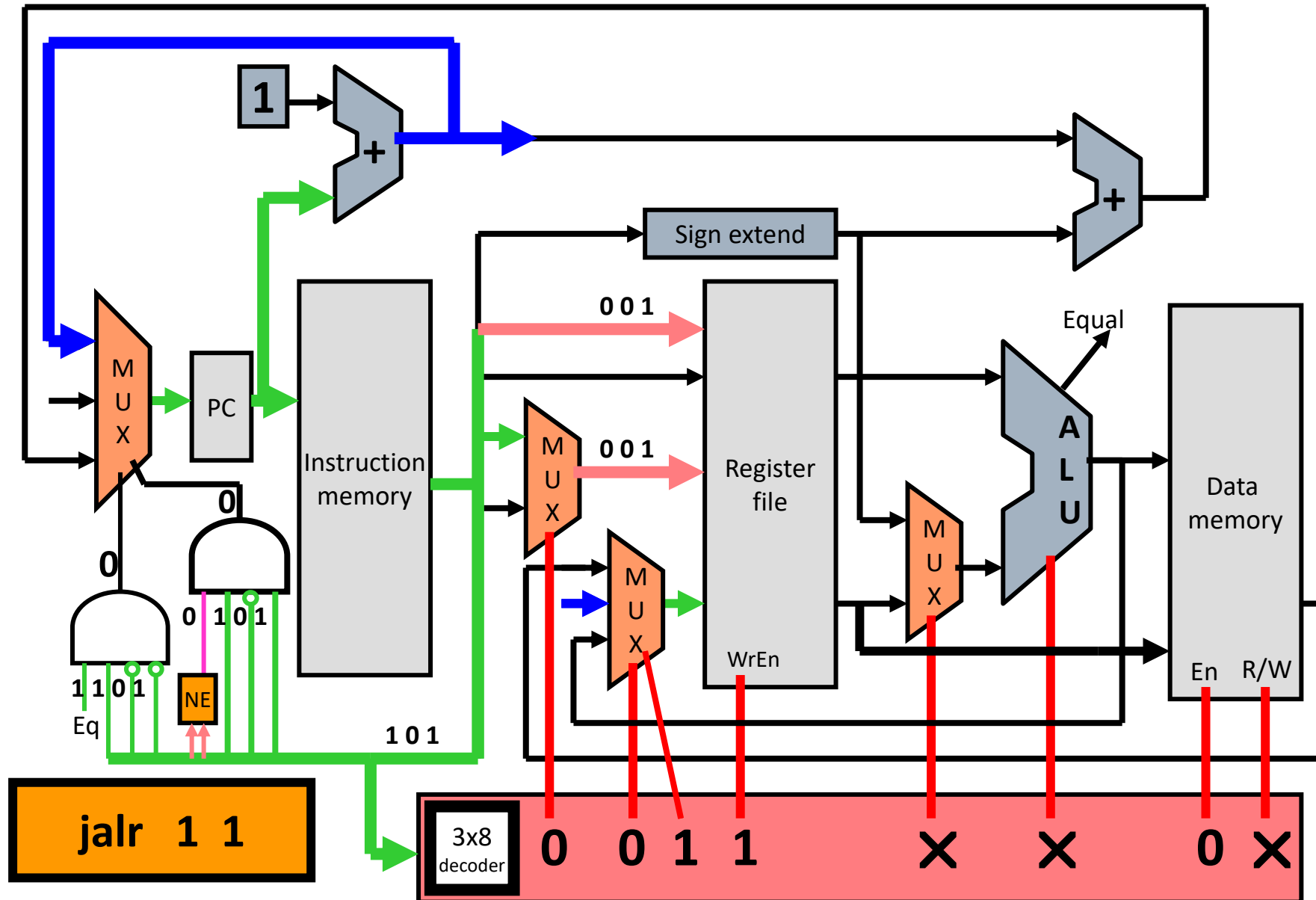

What's Wrong with Single-Cycle?

- **All instructions run at the speed of the slowest instruction.**
- Adding a **long** instruction can hurt performance
 - What if you wanted to include multiply?
- You **cannot reuse** any parts of the processor
 - We have 3 different adders to calculate $PC+1$, $PC+1+offset$ and the ALU
- No benefit in making the common case fast
 - Since every instruction runs at the slowest instruction speed
 - This is particularly important for loads as we will see later

What's Wrong with Single-Cycle?

$$1\text{ ns} = 10^{-9}\text{ s}$$

- 1 ns – Register read/write time
- 2 ns – ALU/adder
- 2 ns – memory access
- 0 ns – MUX, PC access, sign extend, ROM

Poll: What is the latency of lw?

	Get Instr	read reg	ALU oper.	mem	write reg	
• add:	2ns	+ 1ns	+ 2ns		+ 1 ns	= 6 ns
• beq:	2ns	+ 1ns	+ 2ns			= 5 ns
• sw:	2ns	+ 1ns	+ 2ns	+ 2ns		= 7 ns
• lw:	2ns	+ 1ns	+ 2ns	+ 2ns	+ 1ns	= 8 ns

The reason we don't count $PC = PC + 1$ is because we can do $PC = PC + 1$ while we load instruction from memory.

during one cycle, we need to finish on instruction. depend on the longest one.

the frequency of our clock can't change

Computing Execution Time

Assume: 100 instructions executed

25% of instructions are loads, 25 lw 8ns.
10% of instructions are stores, 10 sw 7ns.
45% of instructions are adds, and 45 add 6ns.
20% of instructions are branches. 20 beq 5ns

Single-cycle execution:

?? $100 \times 8ns = 800ns$.

Optimal execution:

?? $25 \times 8 + 10 \times 7 + 45 \times 6 + 20 \times 5$.
 $200 + 70 + 270 + 100 = 640ns$.

Poll: What is the single-cycle execution time?

How fast could this run if we weren't limited by a single-clock period?

Computing Execution Time

Assume: 100 instructions executed

25% of instructions are loads,

10% of instructions are stores,

45% of instructions are adds, and

20% of instructions are branches.

Single-cycle execution:

$$100 * 8\text{ns} = \underline{\mathbf{800}} \text{ ns}$$


Optimal execution:

$$25*8\text{ns} + 10*7\text{ns} + 45*6\text{ns} + 20*5\text{ns} = \underline{\mathbf{640}} \text{ ns}$$




Multiple-Cycle Execution


- Each instruction takes multiple cycles to execute
 - Cycle time is reduced
 - Slower instructions take more cycles
 - Faster instructions take fewer cycles
 - We can start next instruction earlier, rather than just waiting
 - Can reuse datapath elements each cycle
- What is needed to make this work?
 - Since you are re-using elements for different purposes, you need more and/or wider MUXes.
 - You may need extra registers if you need to remember an output for 1 or more cycles.
 - Control is more complicated since you need to send new signals on each cycle.

 

LC2K Datapath – cycle groups

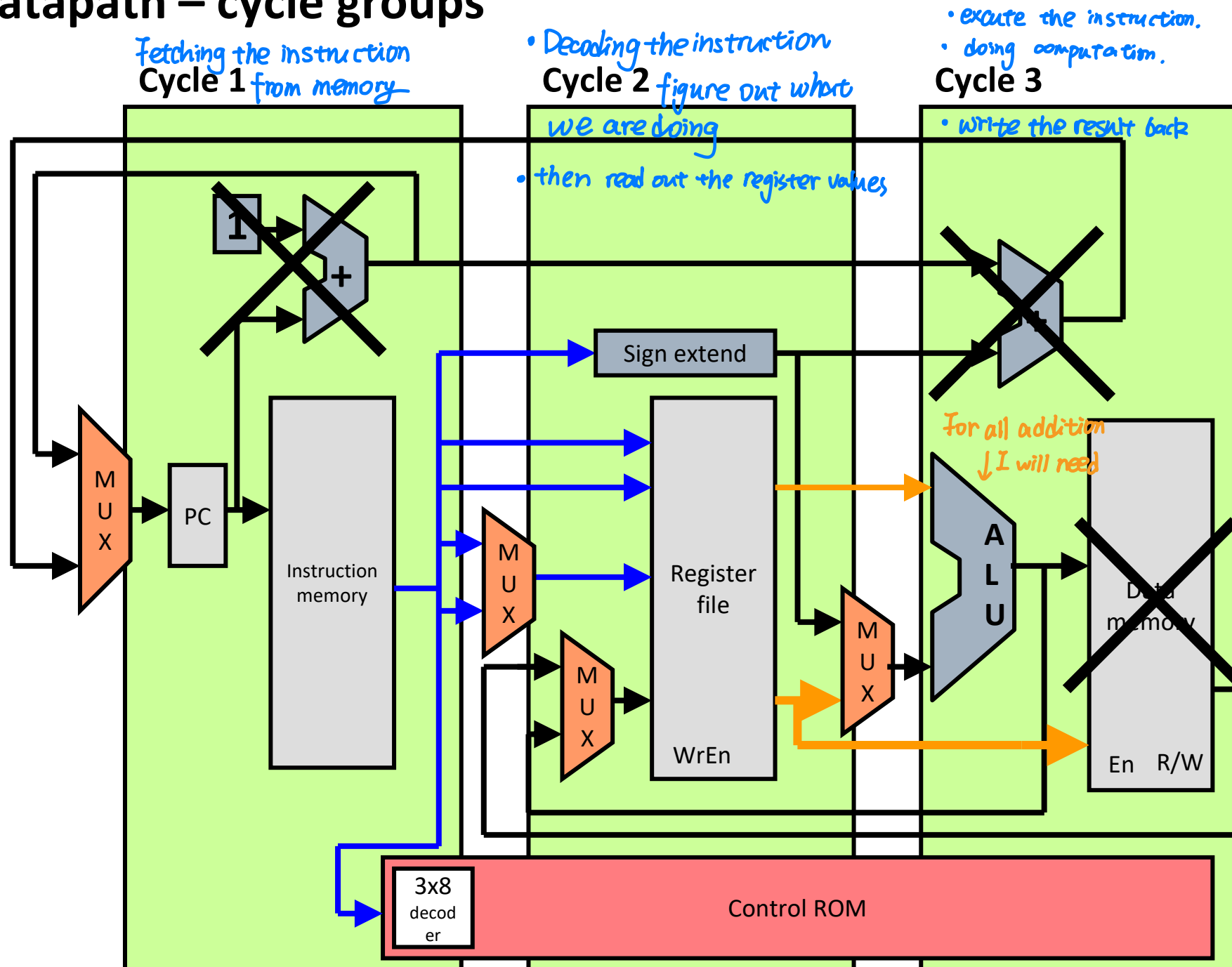


Multi-cycle LC2 Datapath

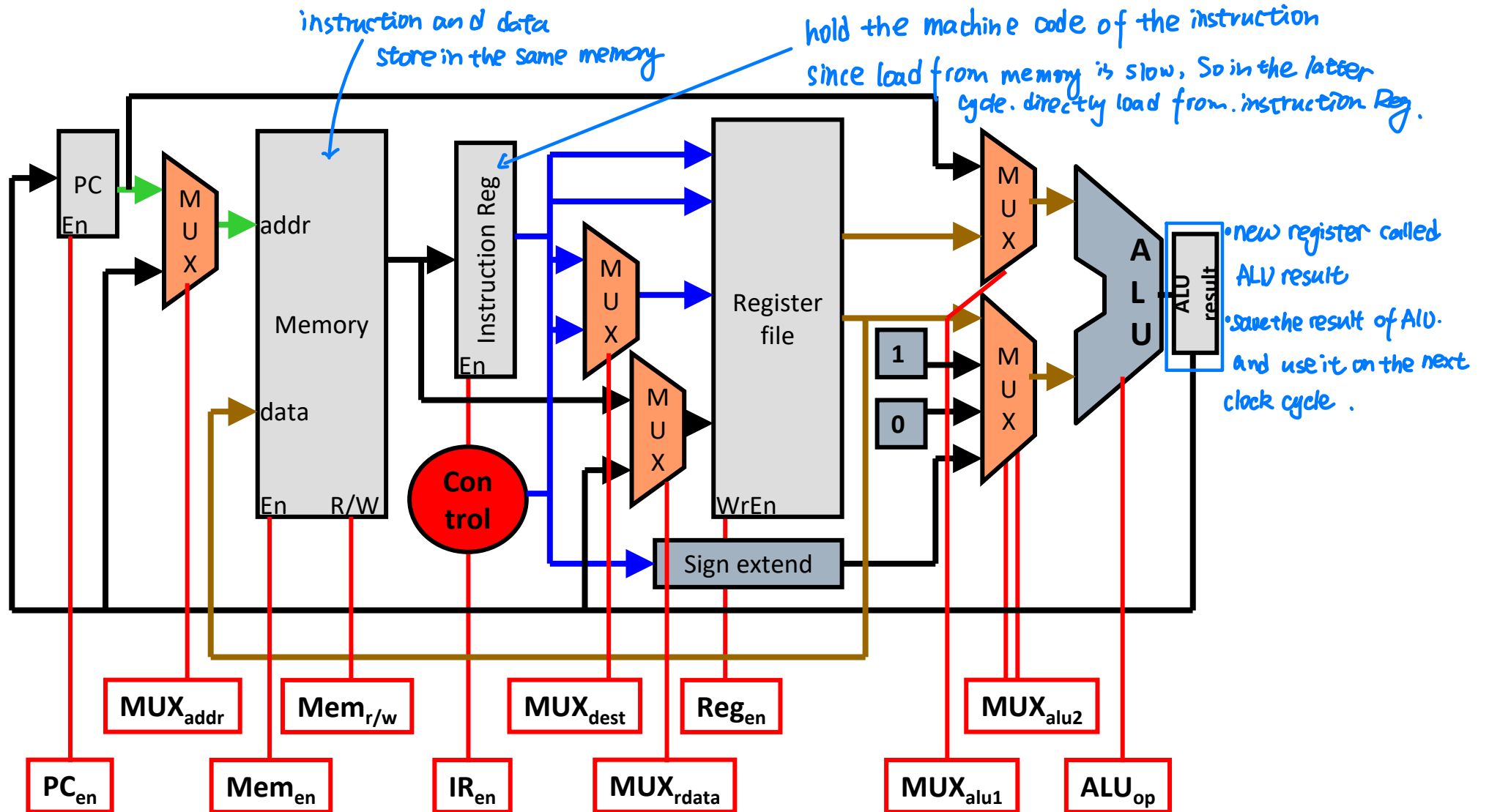

Each red signal comes from "Control" (implemented via ROM as before)

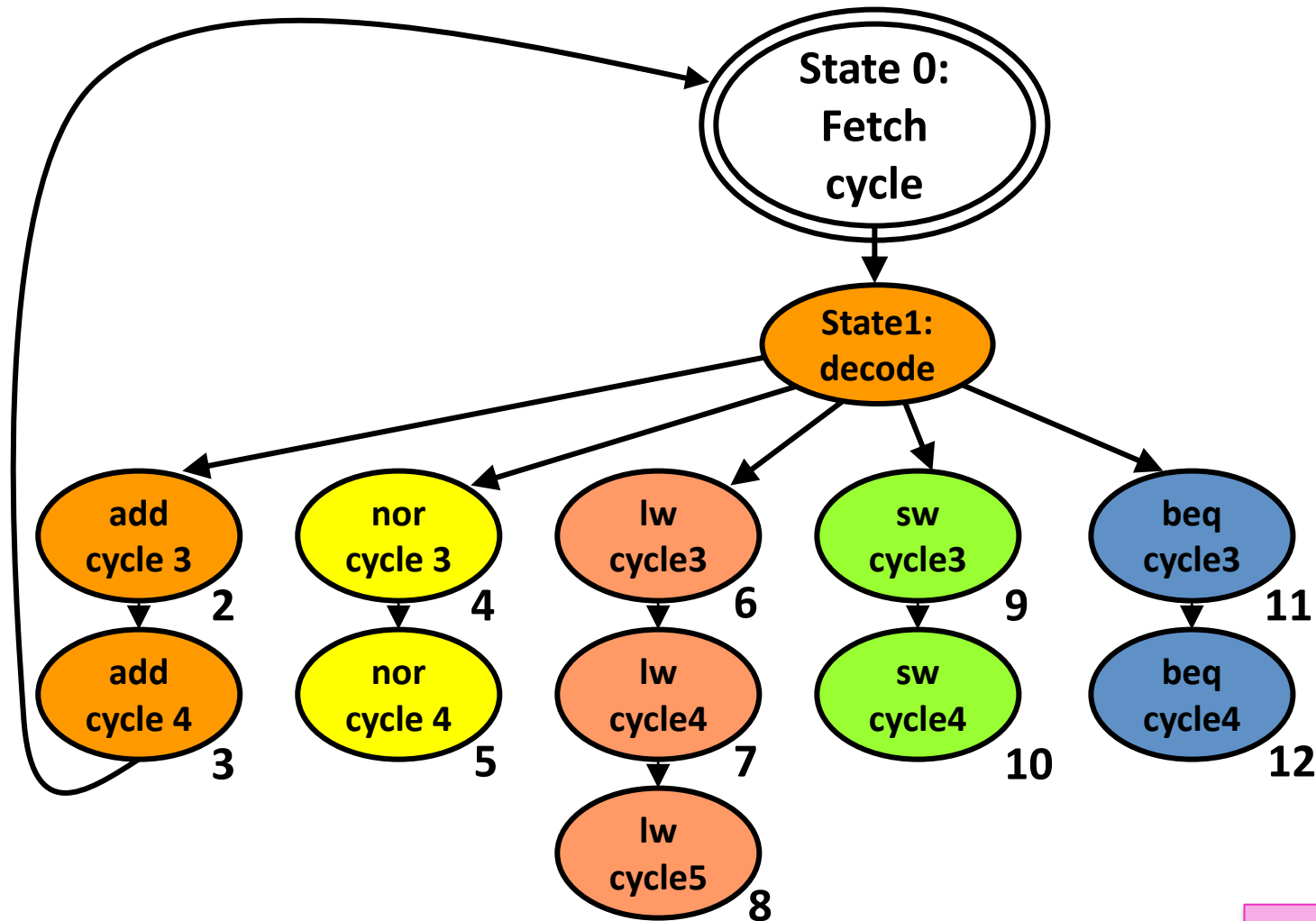State machine for multi-cycle control signals (transition functions)



Note: we aren't worrying about JALR instruction in hardware going forward


Poll: How many bits of storage are needed to store the state?

13 States


All instruction need go back to state 0.

4bits \rightarrow 4 ff.

Implementing FSM

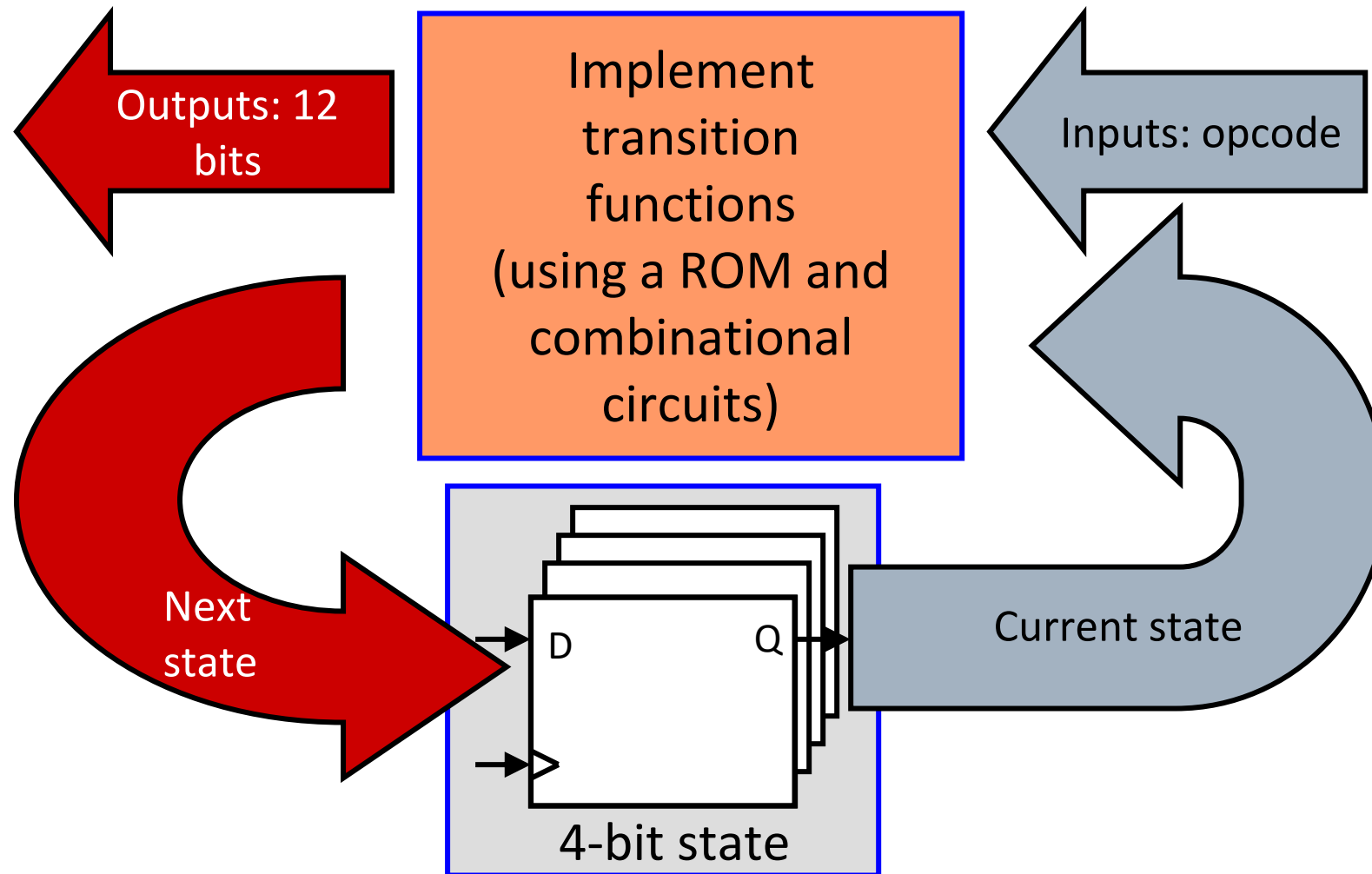

Building the Control ROM

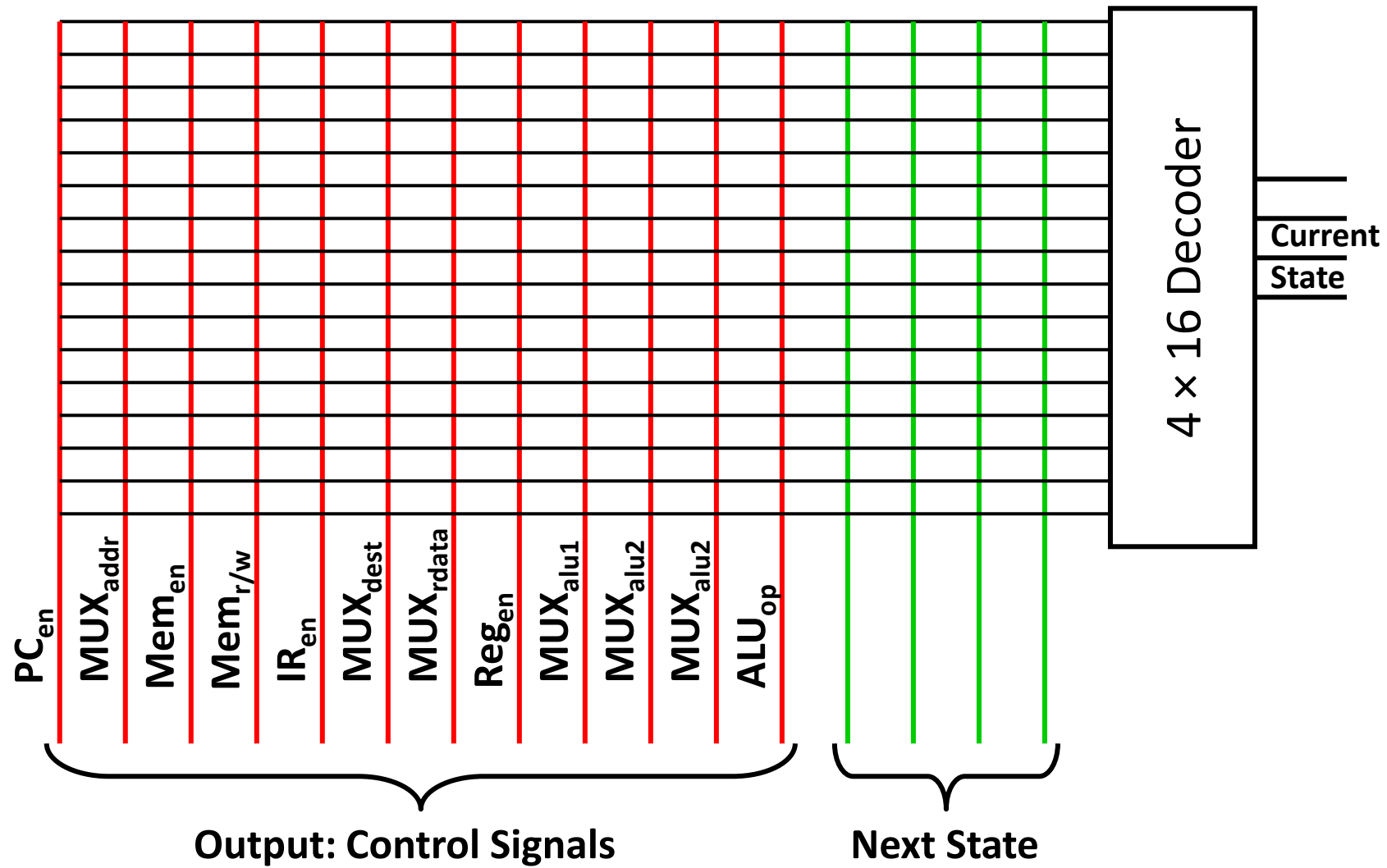


First Cycle (State 0) Fetch Instr

- What operations need to be done in the first cycle of executing any instruction?
 - Read memory[PC] and store into instruction register.
 - Must select PC in memory address MUX ($MUX_{addr} = 0$)
 - Enable memory operation ($Mem_{en} = 1$)
 - R/W should be (read) ($Mem_{r/w} = 0$)
 - Enable Instruction Register write ($IR_{en} = 1$)
 - Calculate PC + 1
 - Send PC to ALU ($MUX_{alu1} = 0$)
 - Send 1 to ALU ($MUX_{alu2} = 01$)
 - Select ALU add operation ($ALU_{op} = 0$)
 - $PC_{en} = 0$; $Reg_{en} = 0$; MUX_{dest} and $MUX_{rdata} = X$
- Next State: Decode Instruction


First Cycle (State 0) Fetch Instr

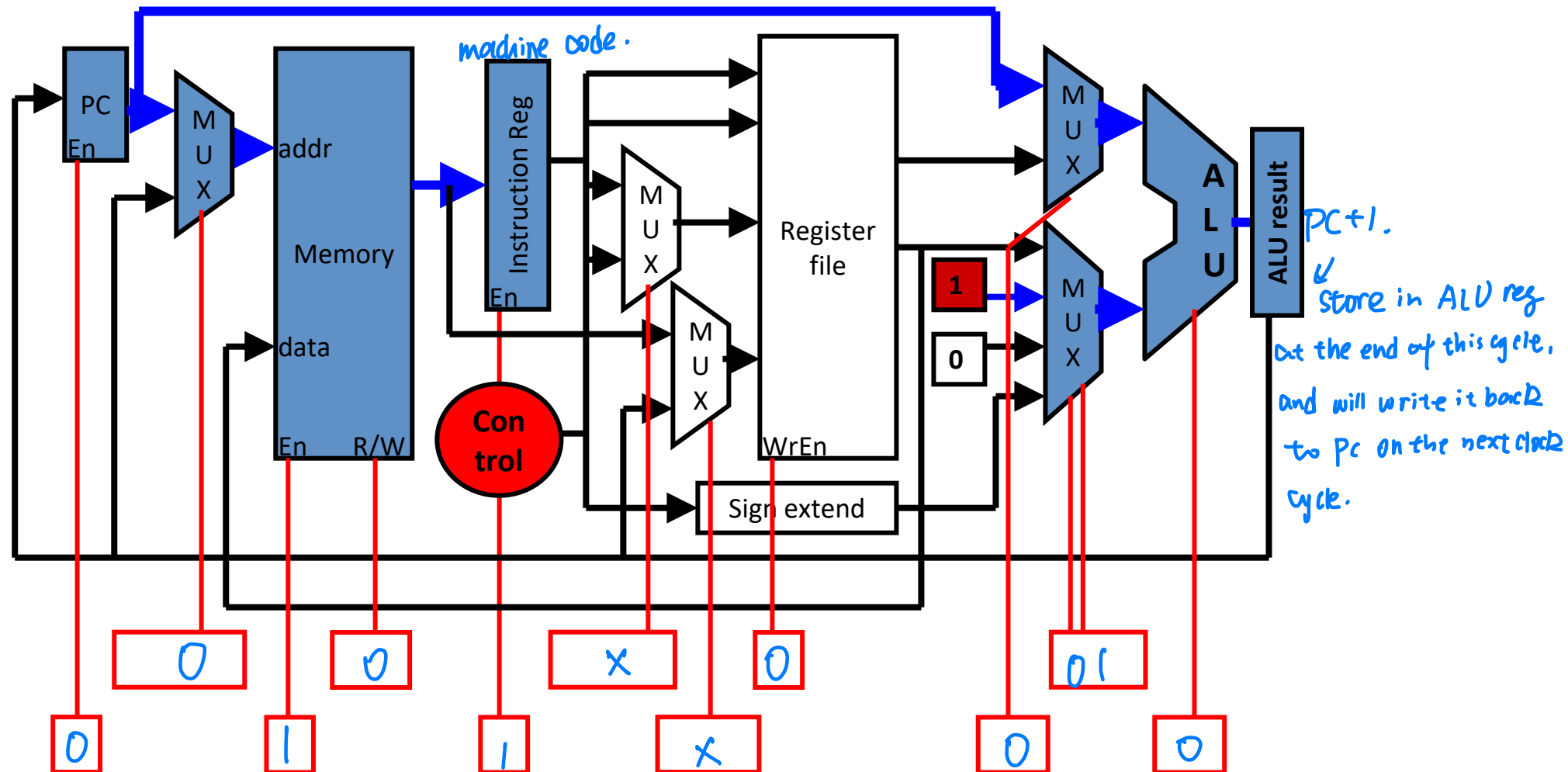This is the same for all instructions
(since we don't know the instruction yet!)




First Cycle (State 0) Fetch Instr

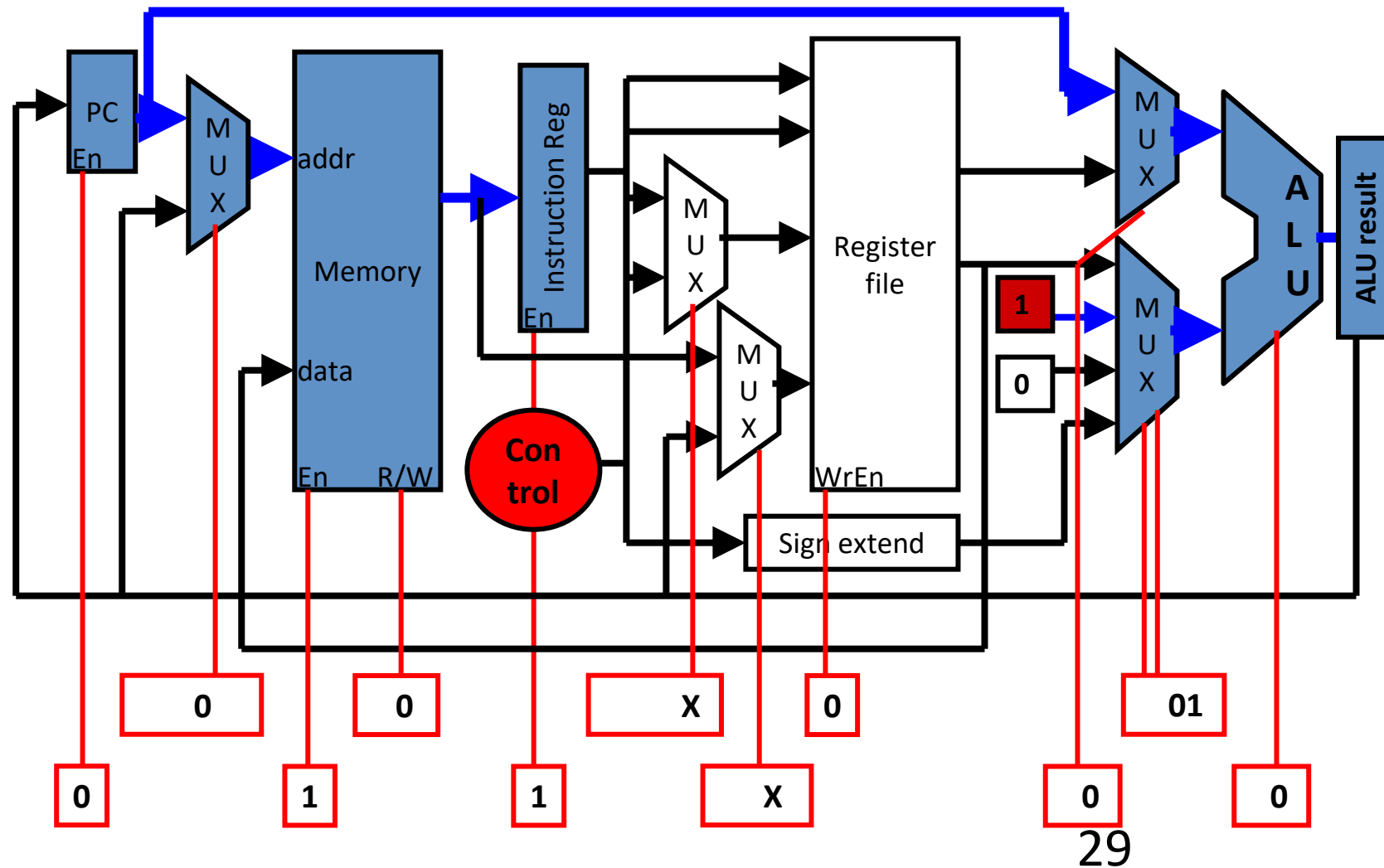
This is the same for all instructions
(since we don't know the instruction yet!)



Building the Control ROM

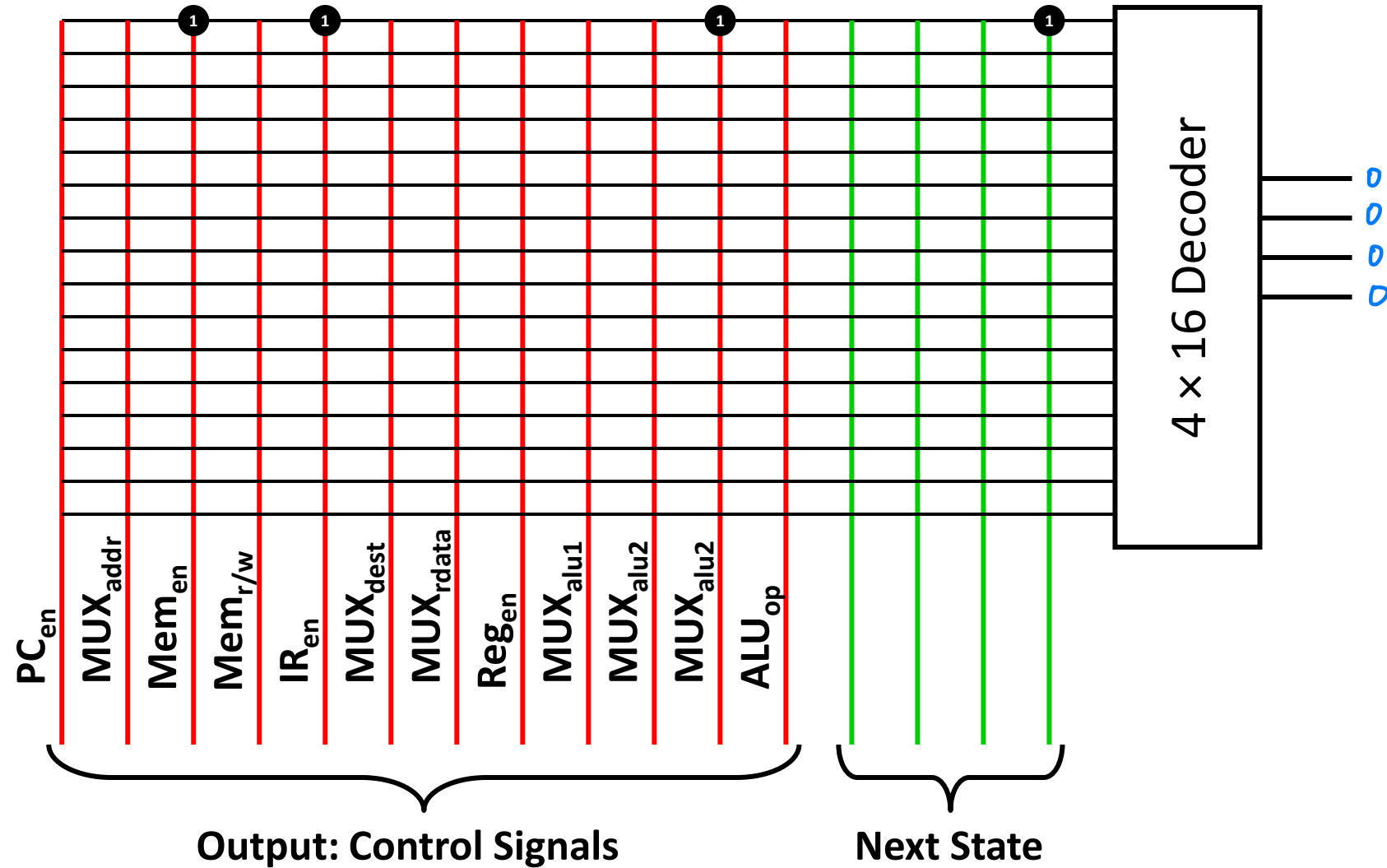

State 1: instruction decode

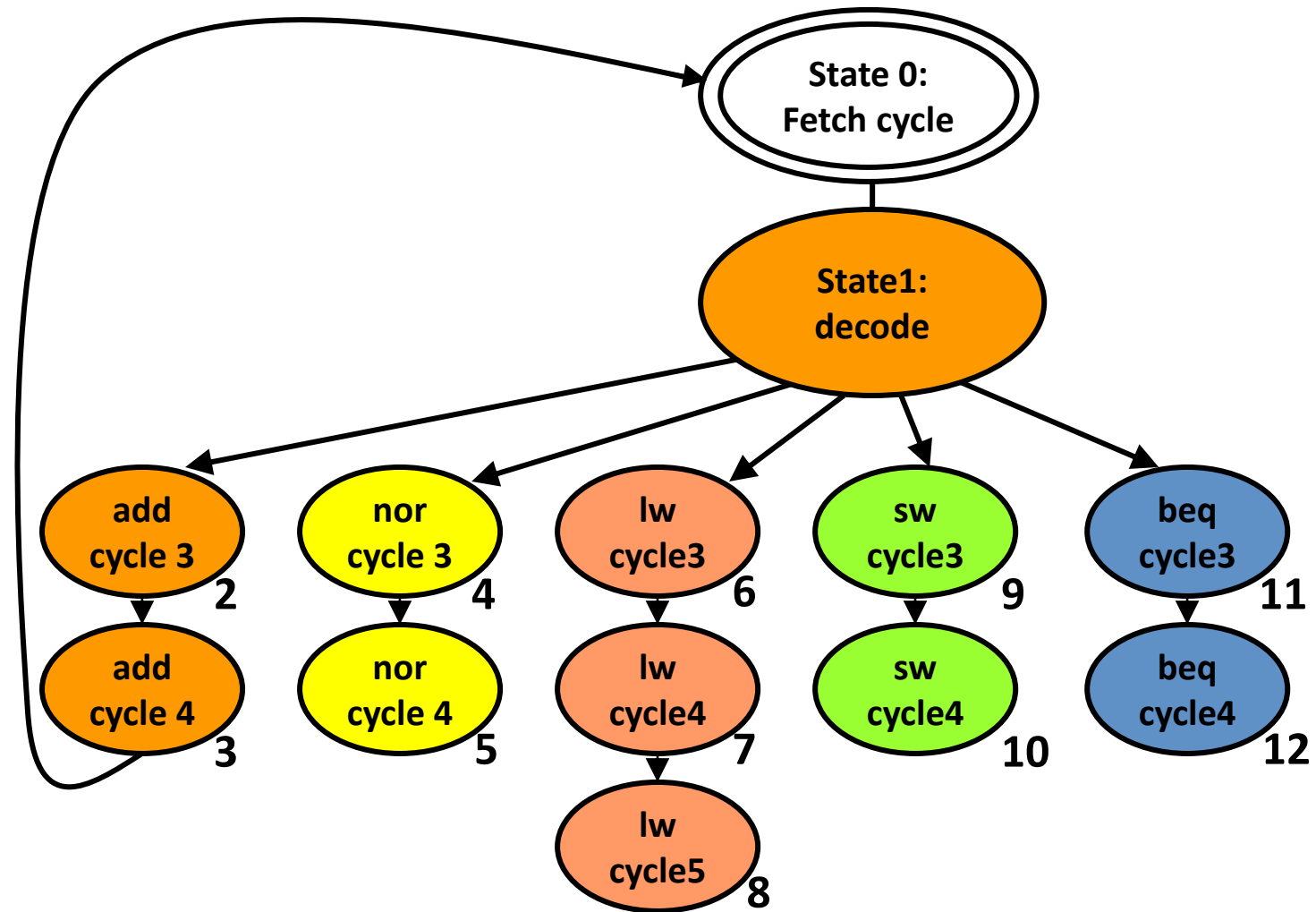


State 1: output function

Poll: What will the control bits be?


Update PC; read registers (regA and regB);
use opcode to determine next state

Note: since RF read
latency is same as
clock period, RF
data isn't available
until next cycle

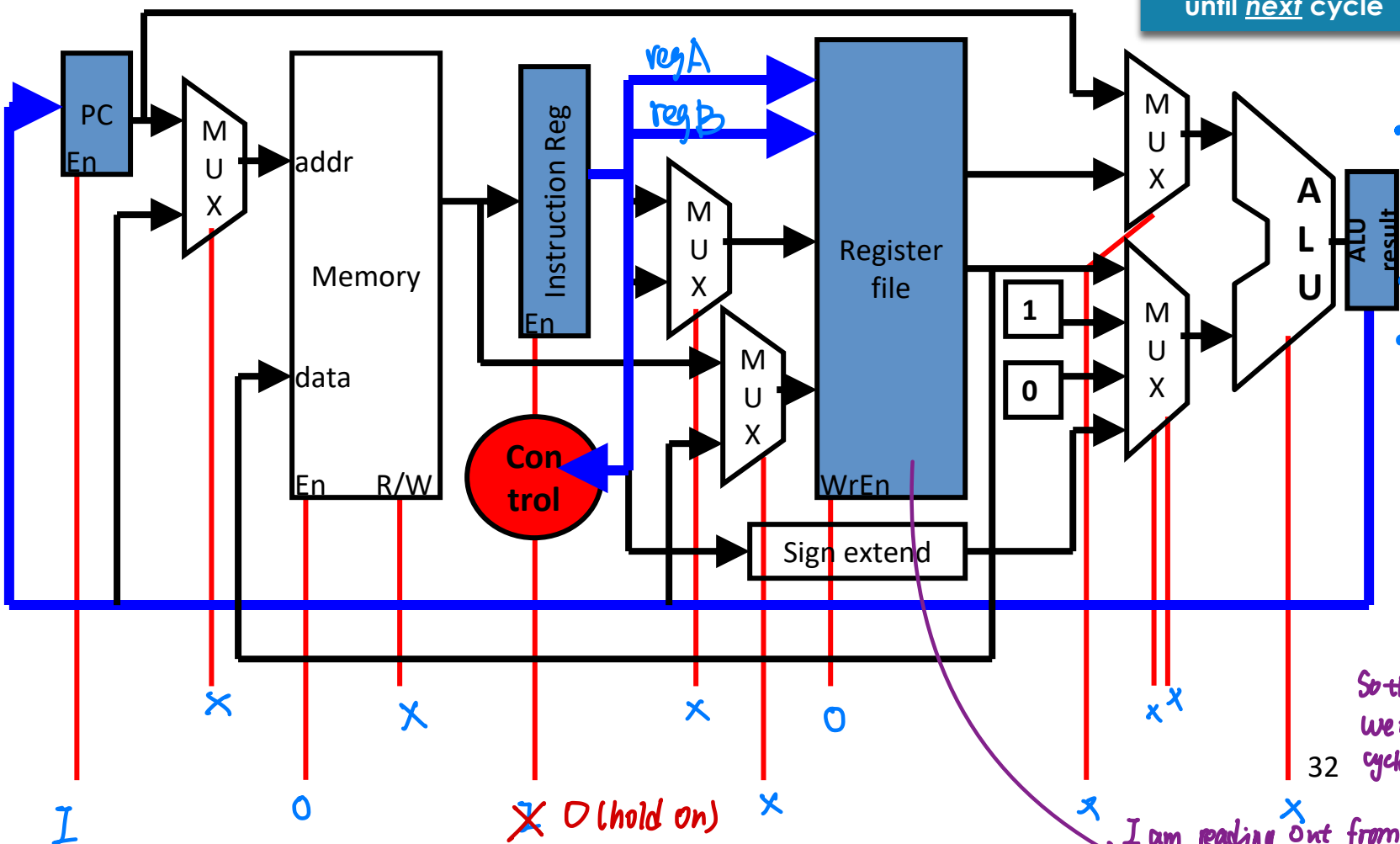


State 1: output function

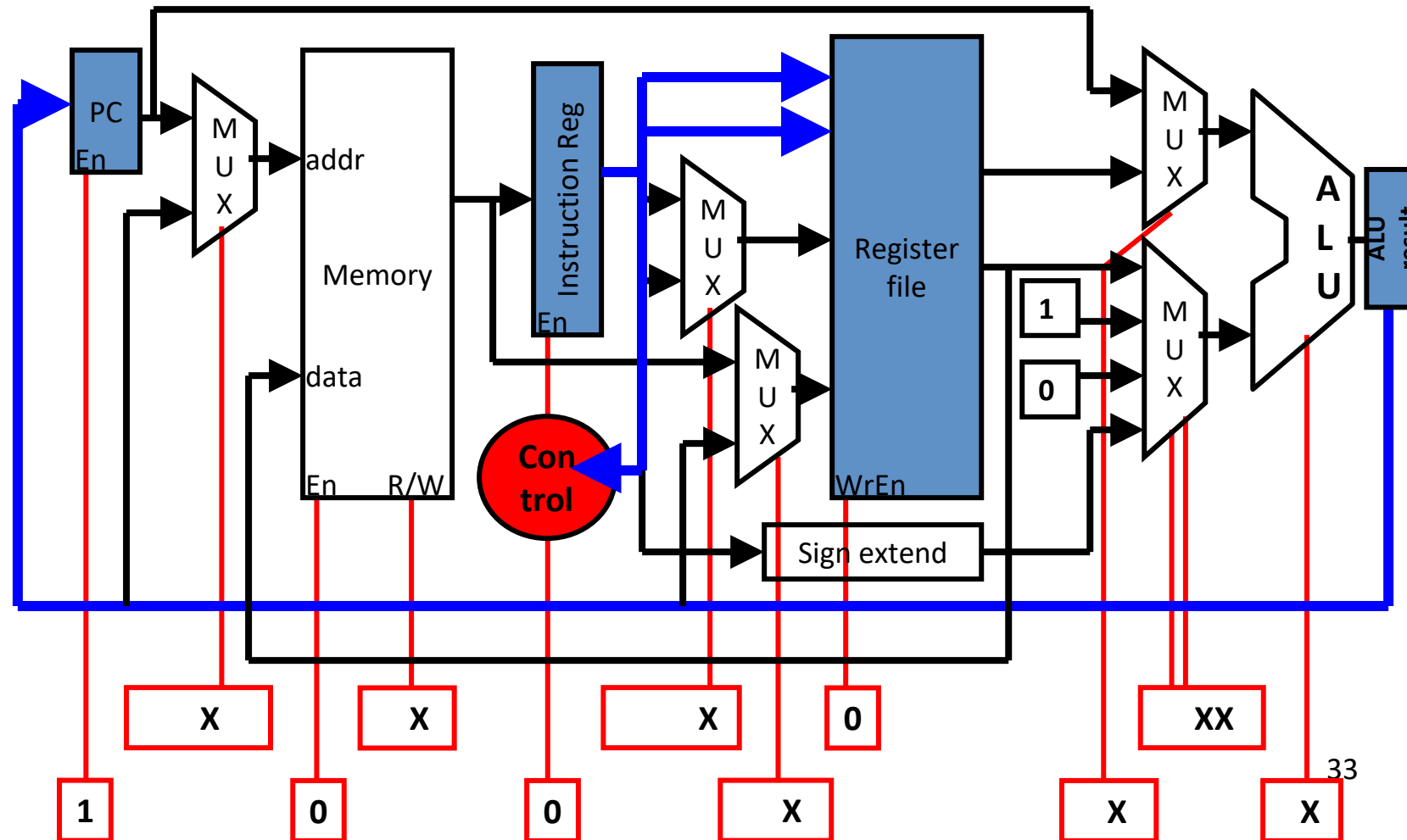Update PC; read registers (regA and regB);
use opcode to determine next state



Building the Control ROM

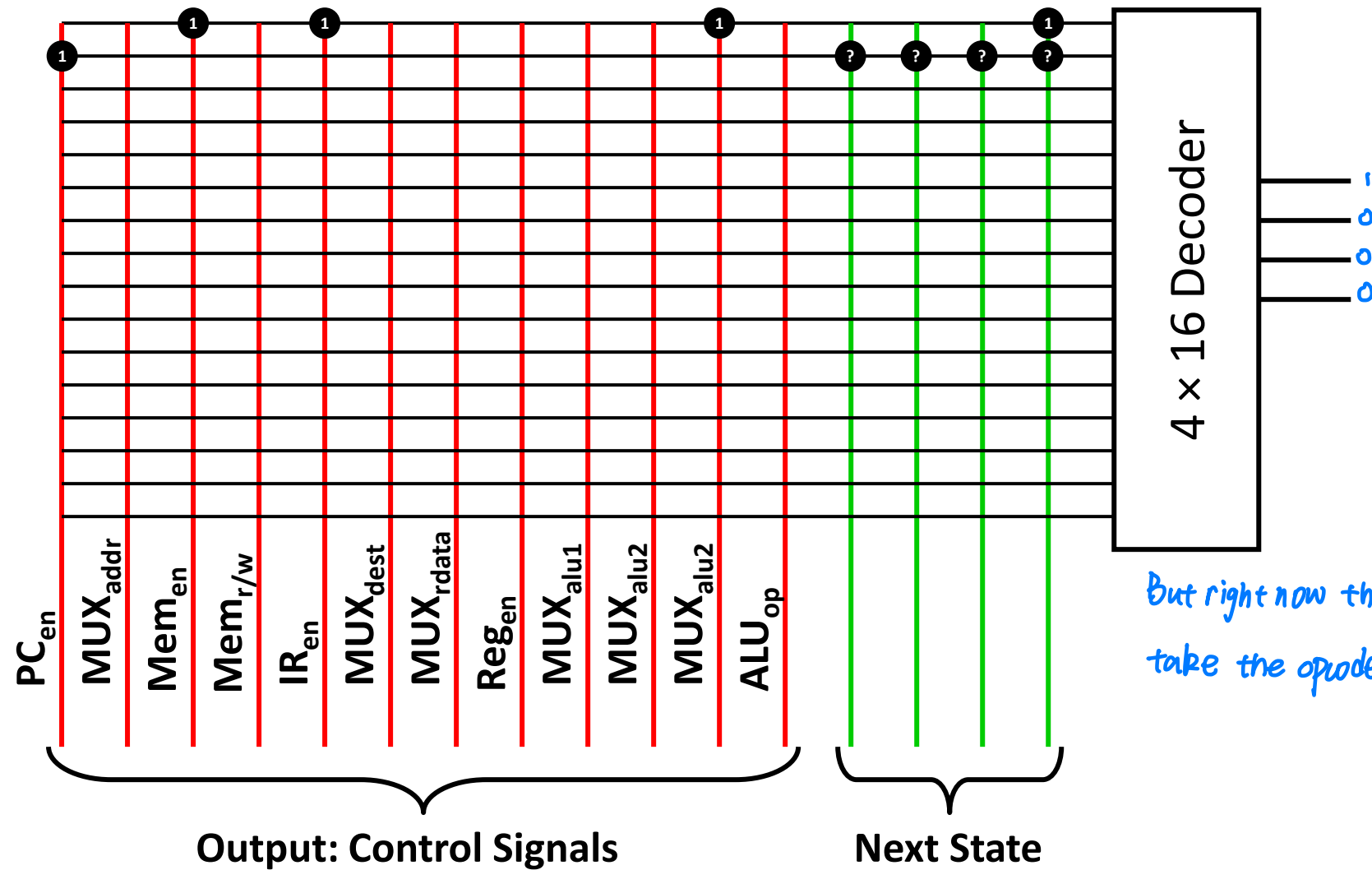How do we set
next state??
Let's come
back to that...




Next time

- Finish up multi-cycle processors
- Introduce pipelining


Extra Slides

State 2: Add cycle 3

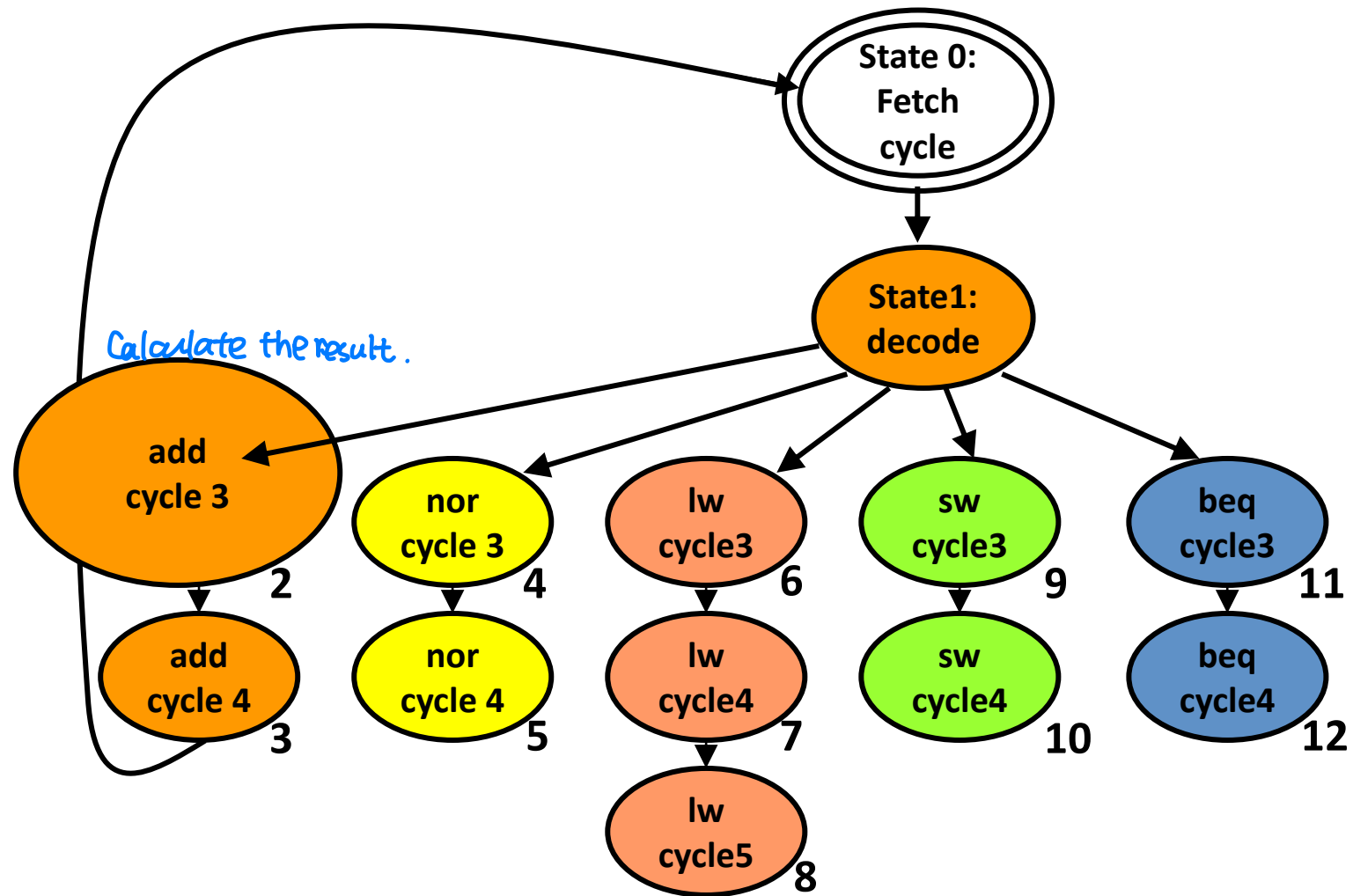


State 2: Add Cycle 3 Operation

Send control signals to MUX to select values of regA and regB and control signal to ALU to add

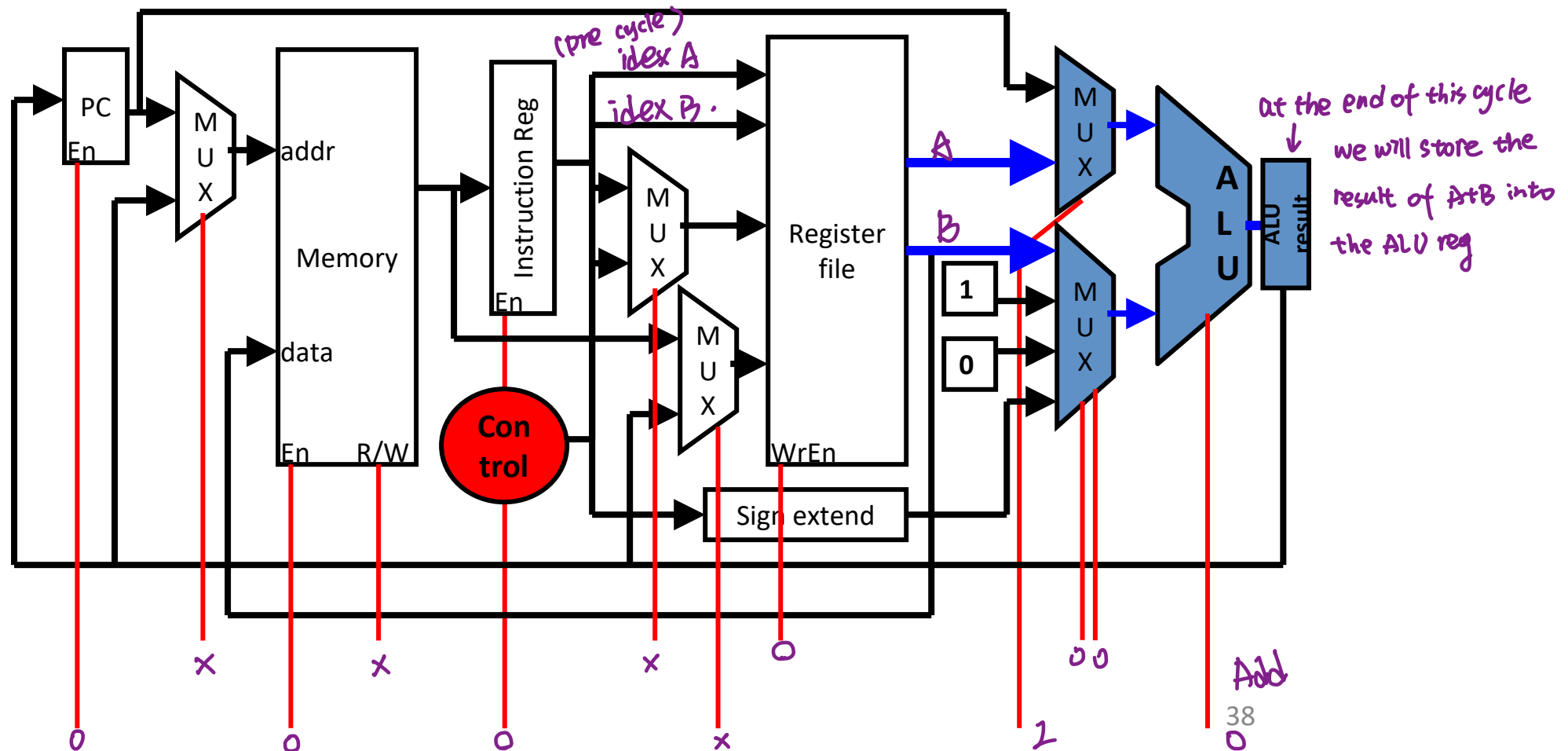


State 2: Add Cycle 3 Operation

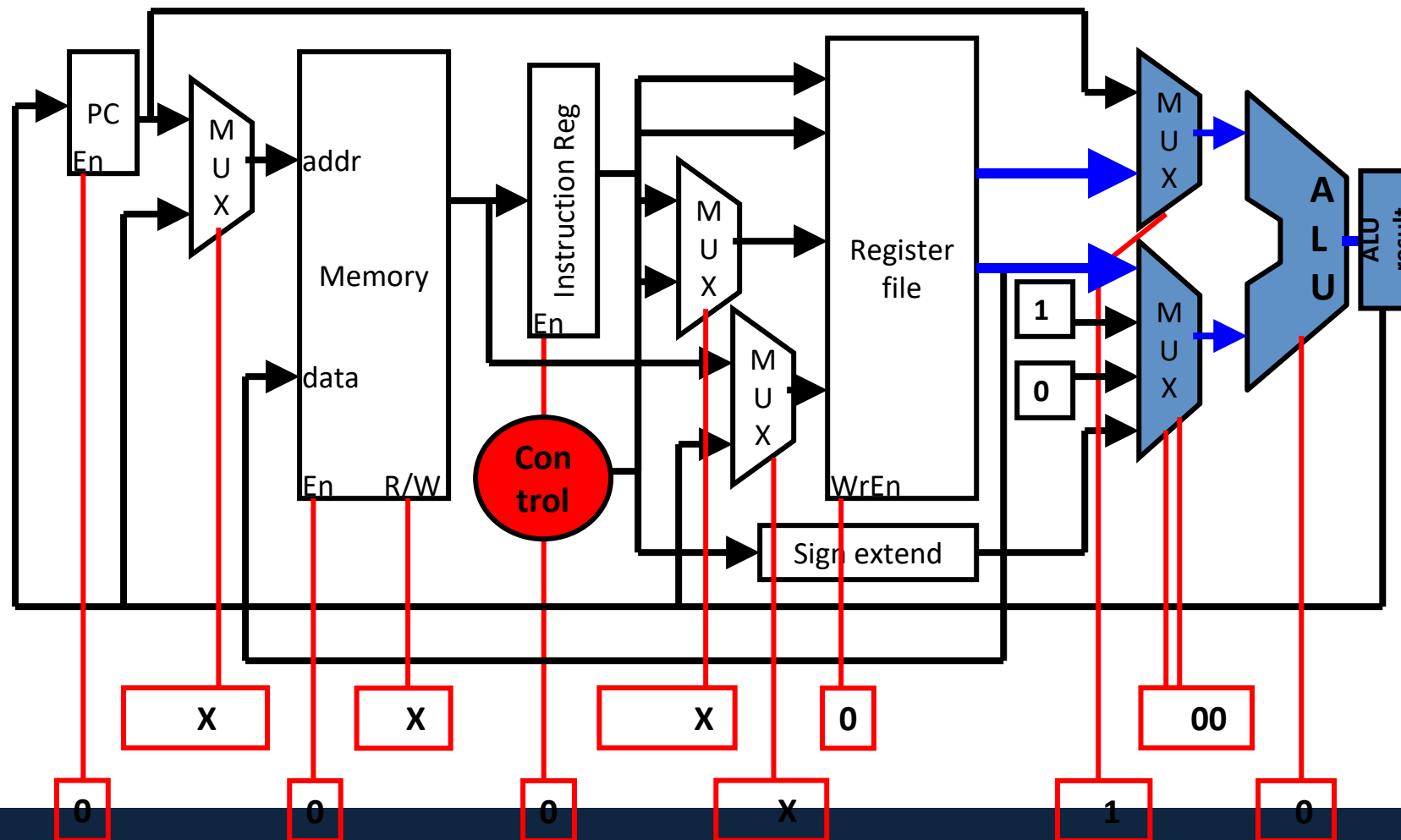
Send control signals to MUX to select values of regA and regB and control signal to ALU to add



Building the Control Rom

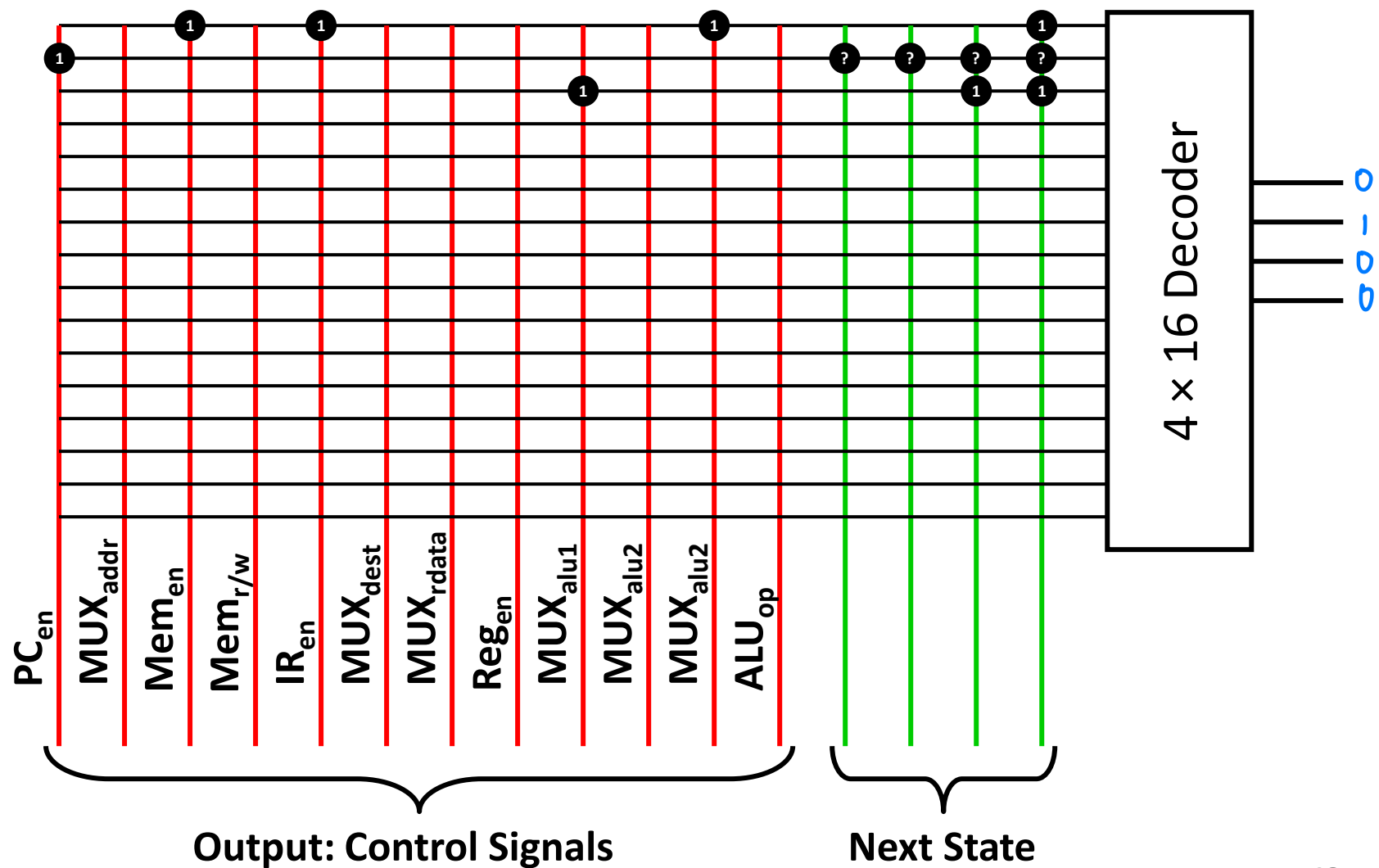


State 3: Add cycle 4

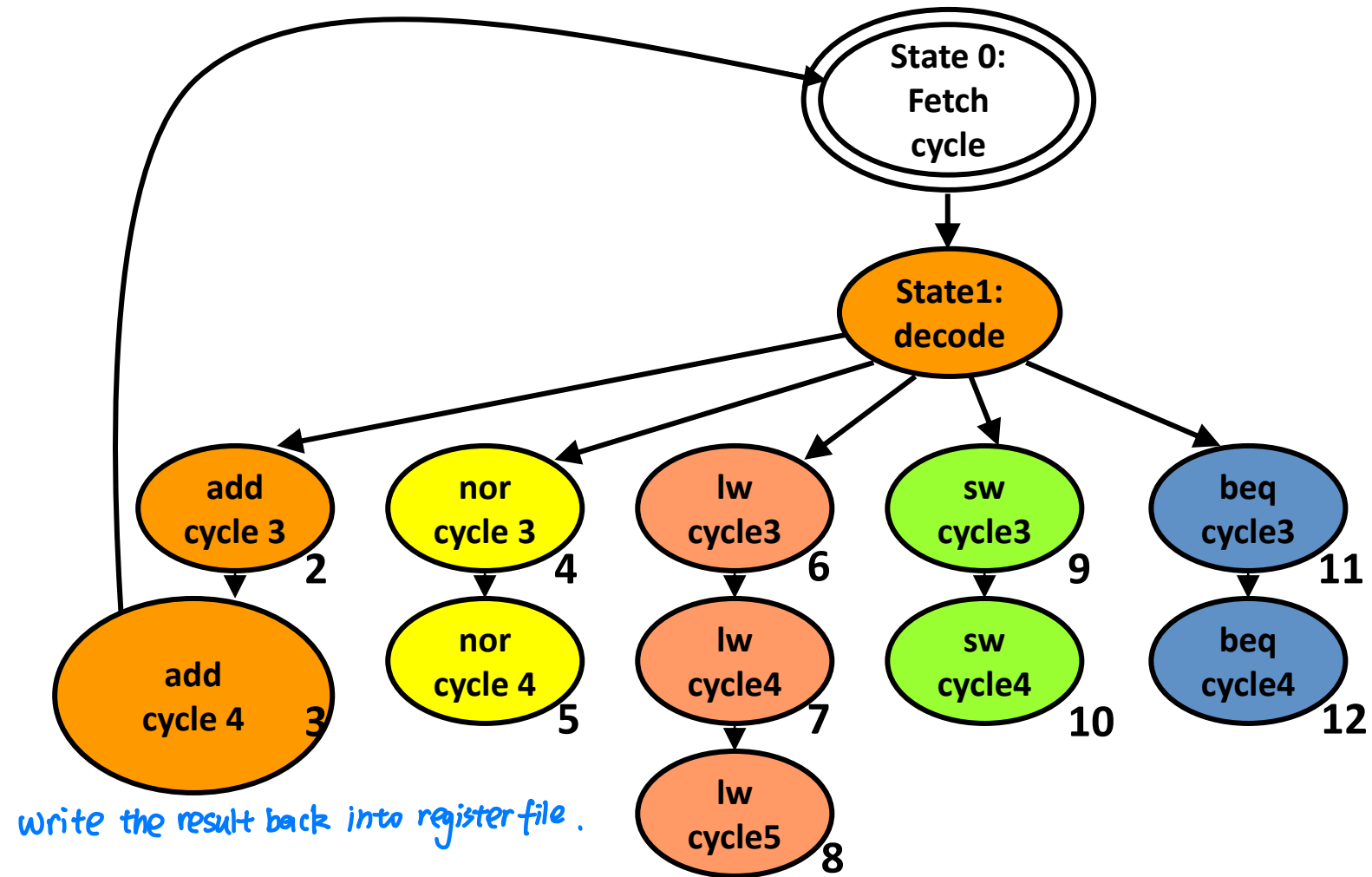


Add Cycle 4 (State 3) Operation

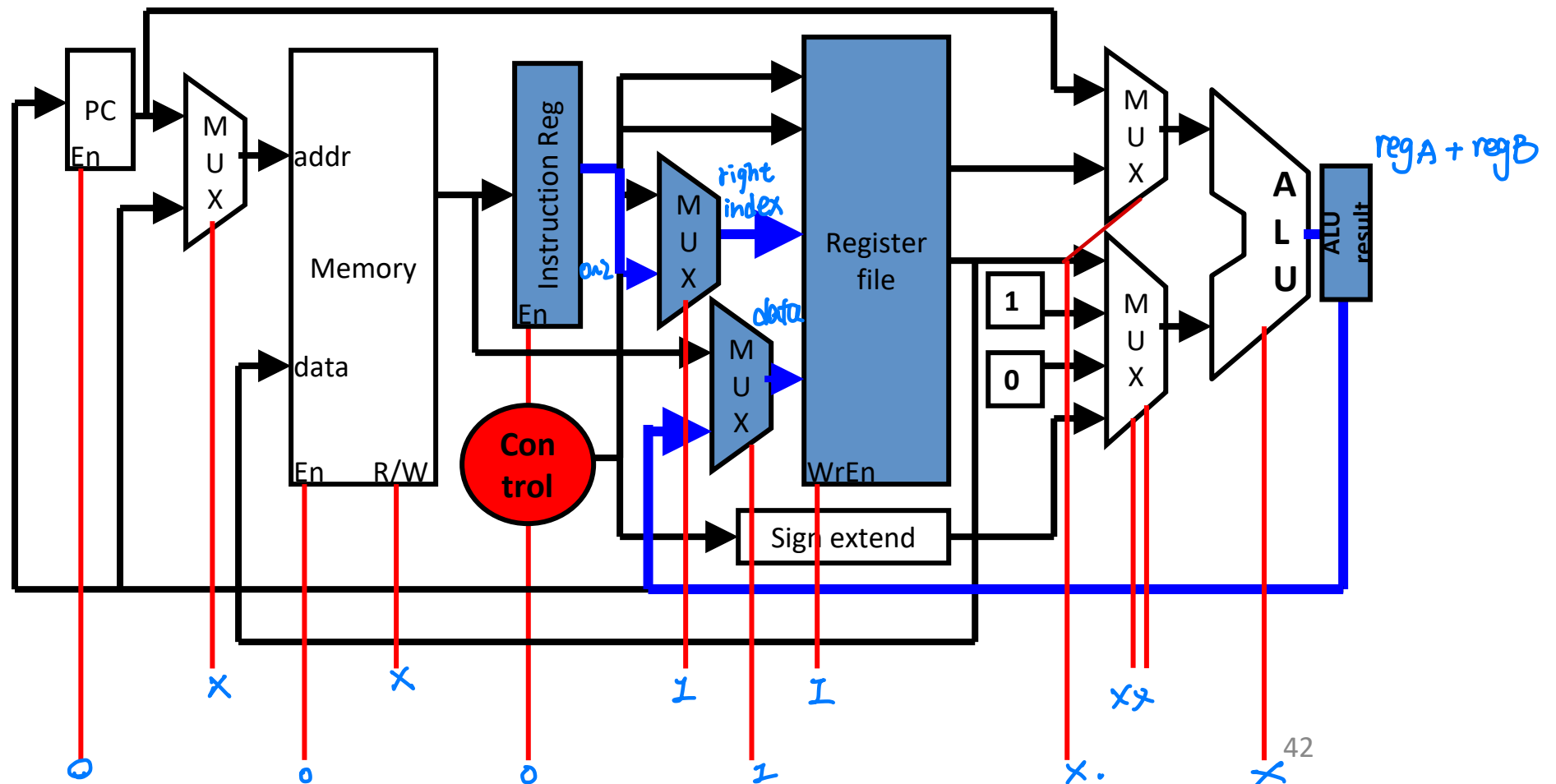Send control signal to address MUX to select dest and to data MUX to select ALU output, then send write enable to register file.




Add Cycle 4 (State 3) Operation

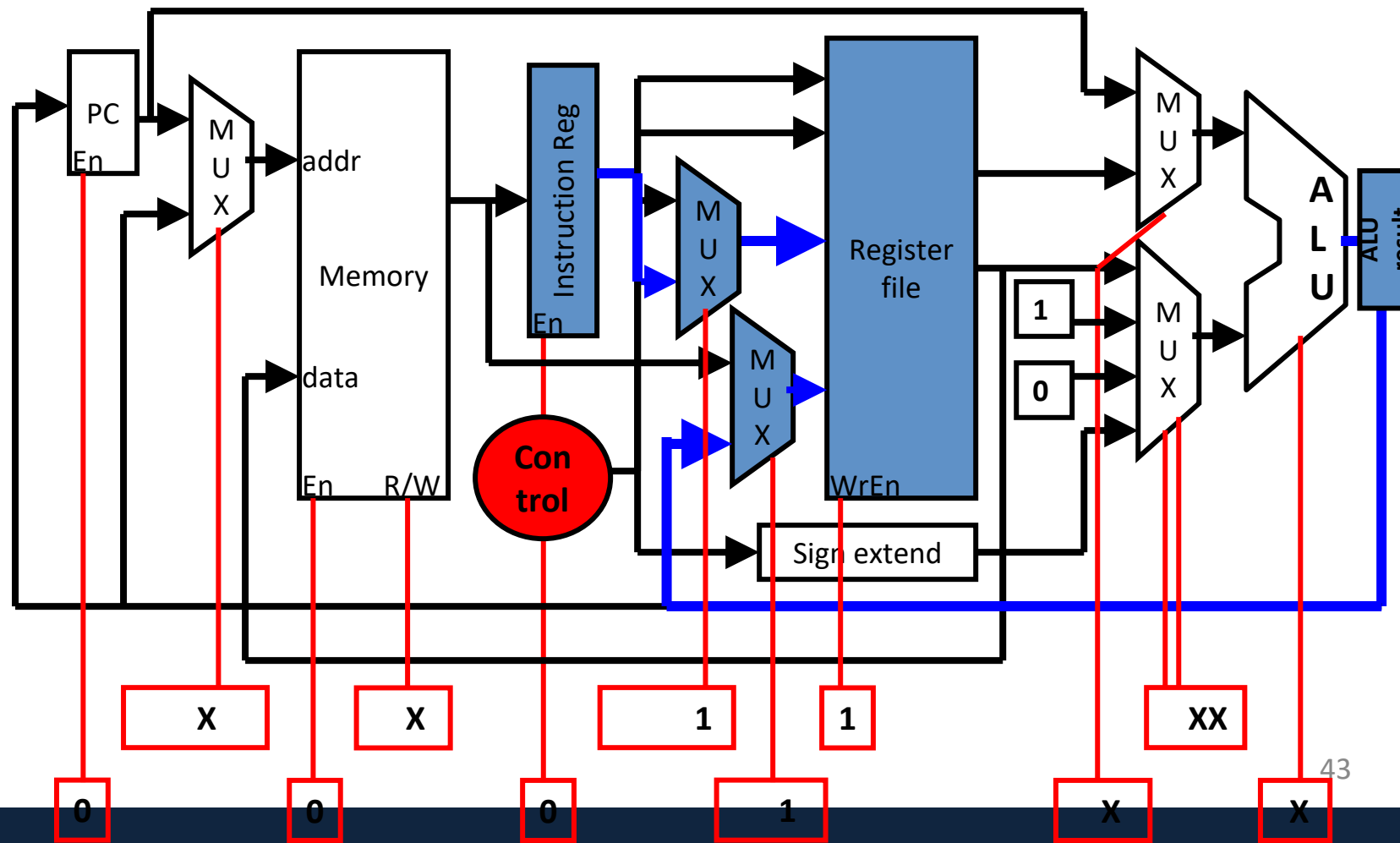
Send control signal to address MUX to select dest and to data MUX to select ALU output, then send write enable to register file.



Building the Control Rom

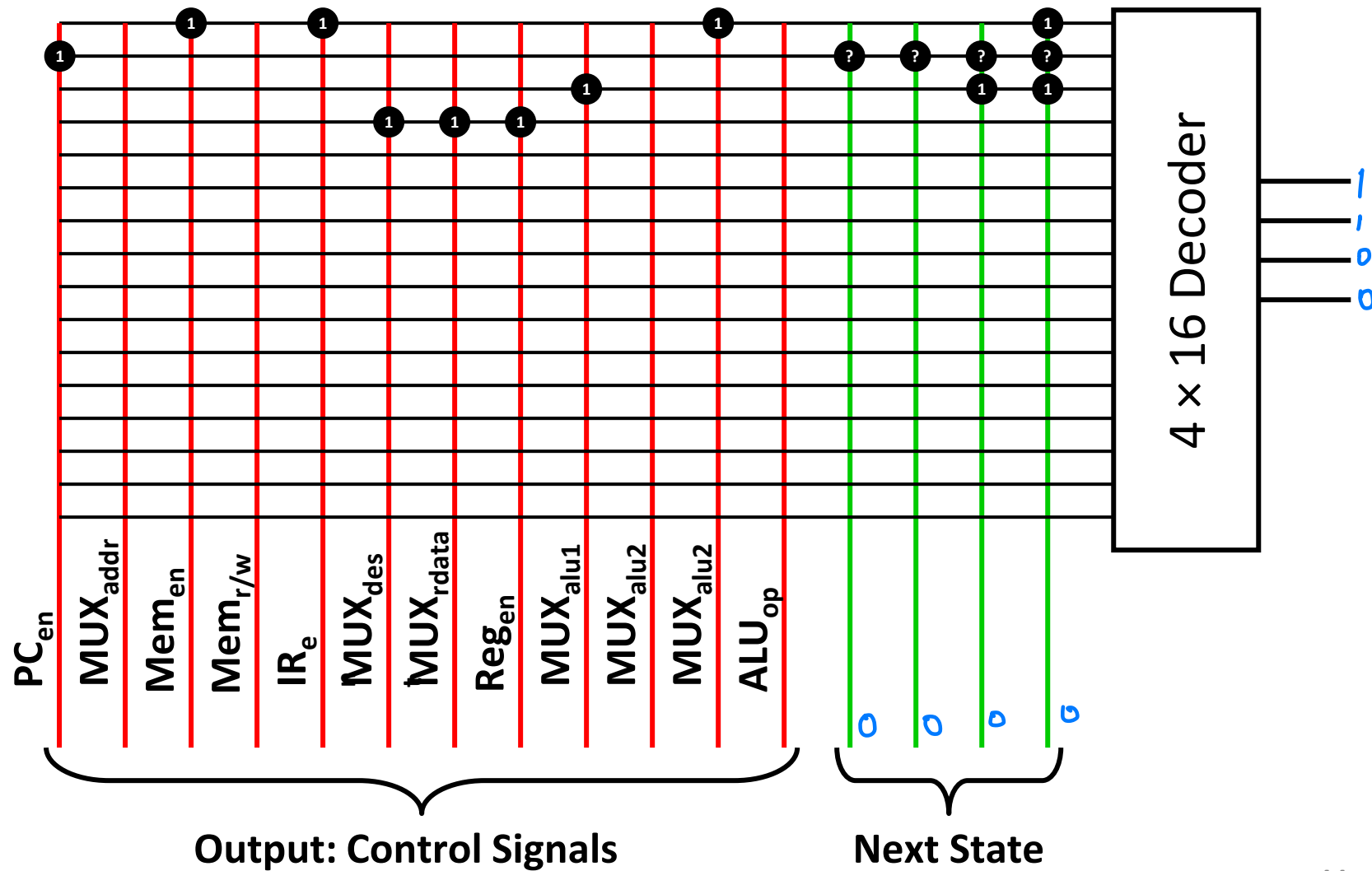


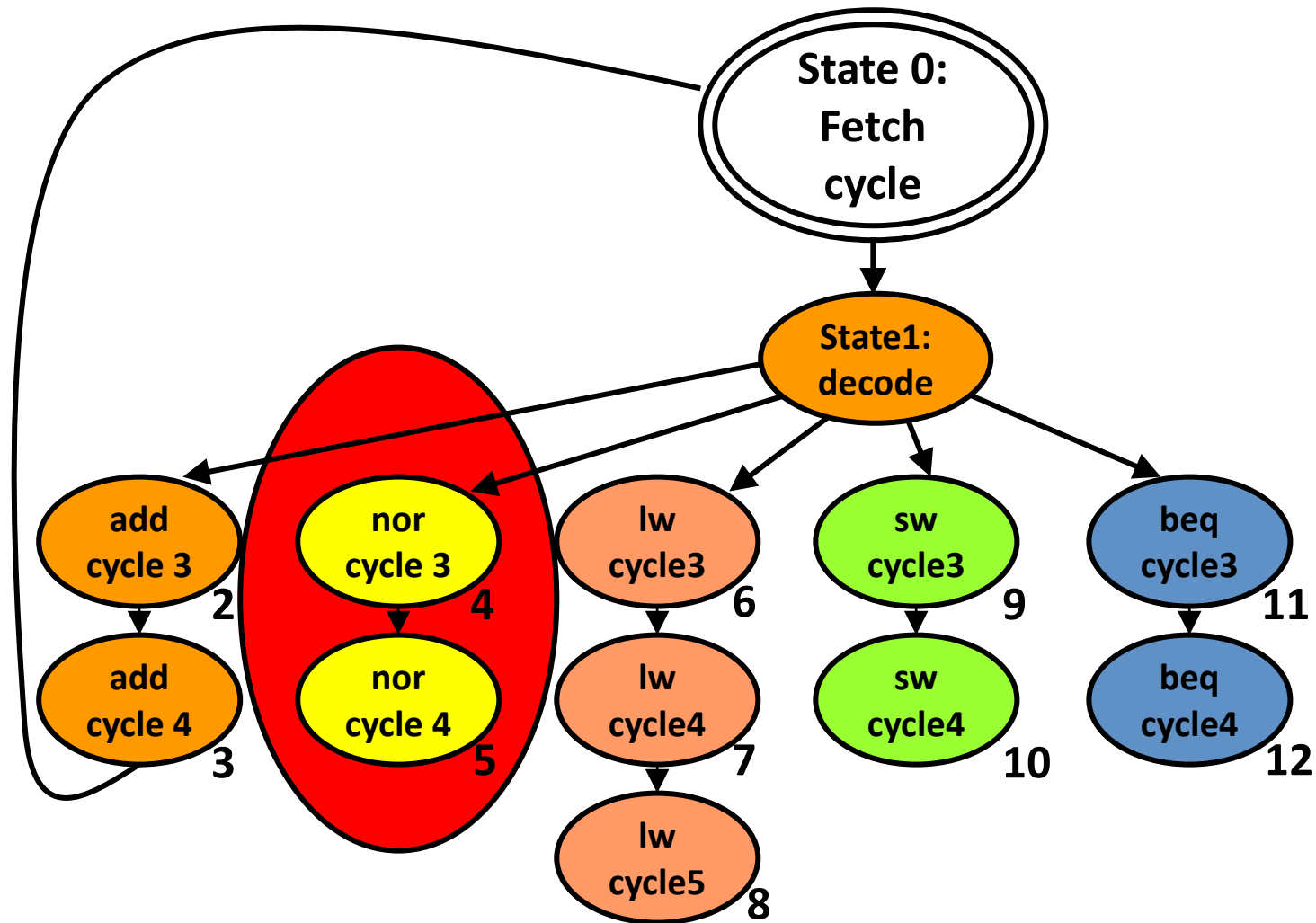Return to State 0: Fetch cycle to execute the next instruction



Control Rom for nor (4 and 5)

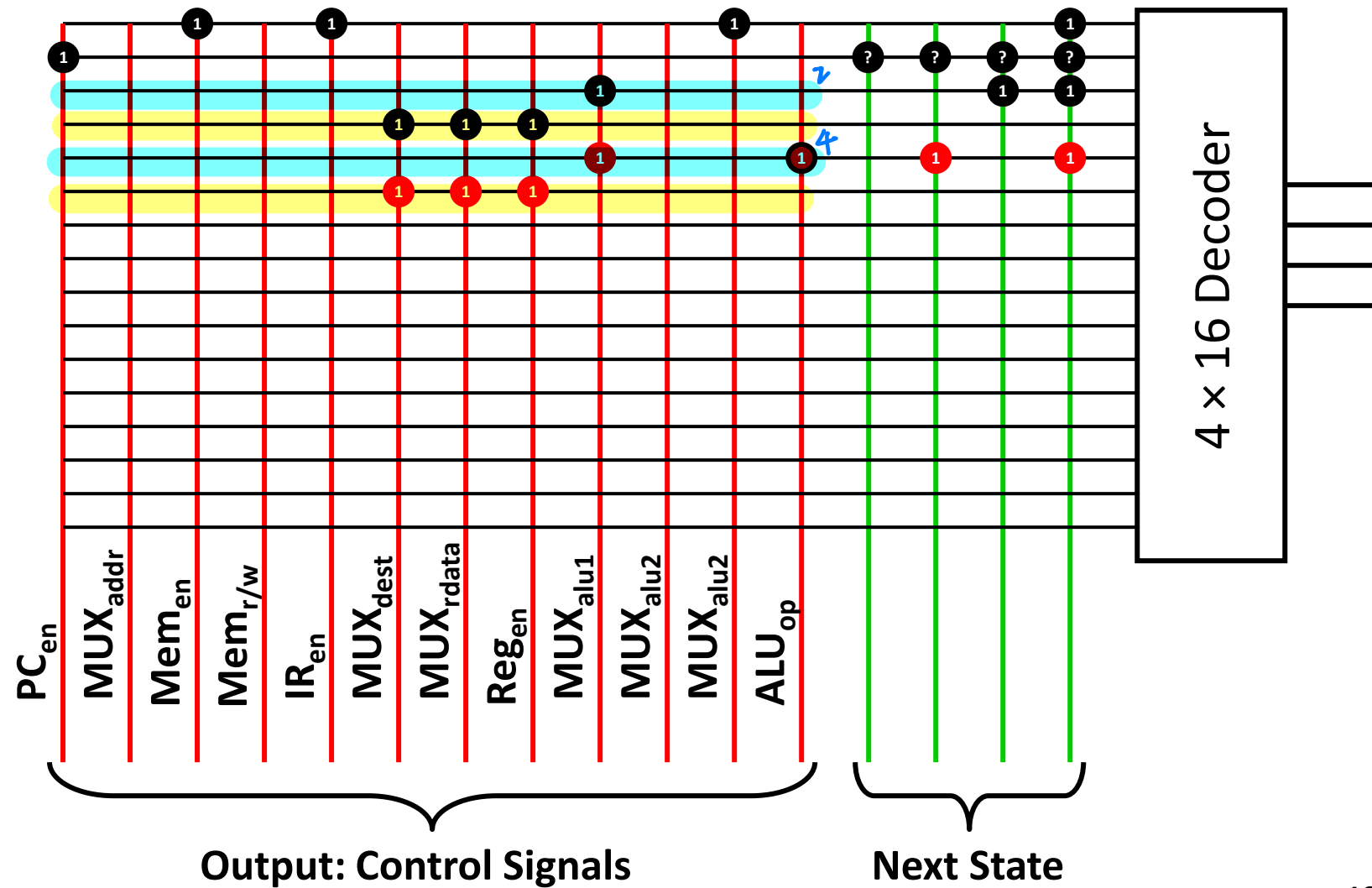
Same output as
add except
 ALU_{op} and Next
State




Agenda

- Short-comings of single-cycle
- Multi-cycle overview
- Fetching instructions
- Decoding instructions
- ADD/NOR execution
- **Choosing which state to transition to**
- LW/SW execution
- BEQ execution
- Performance


What about the transition from state 1?

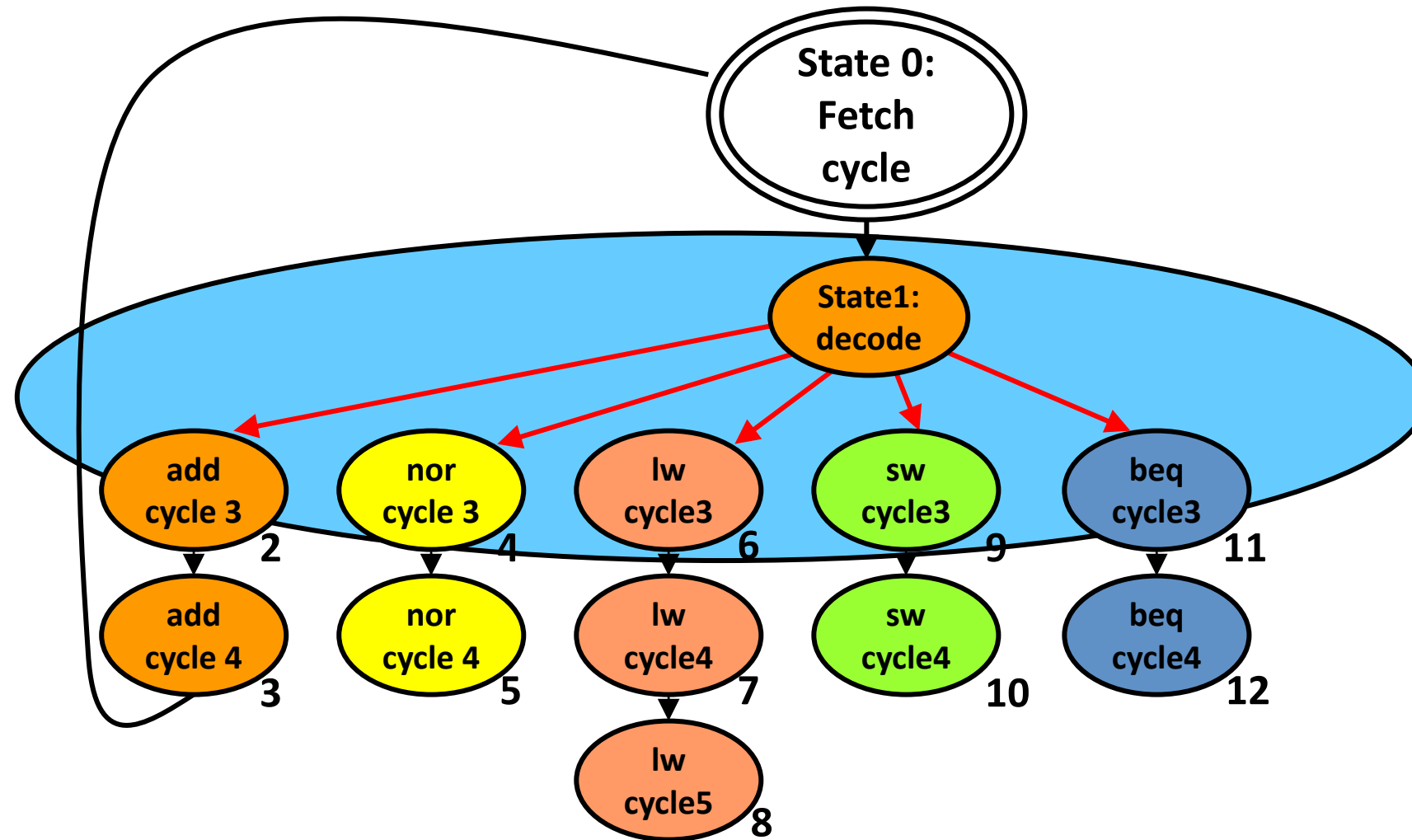


Complete transition function circuit

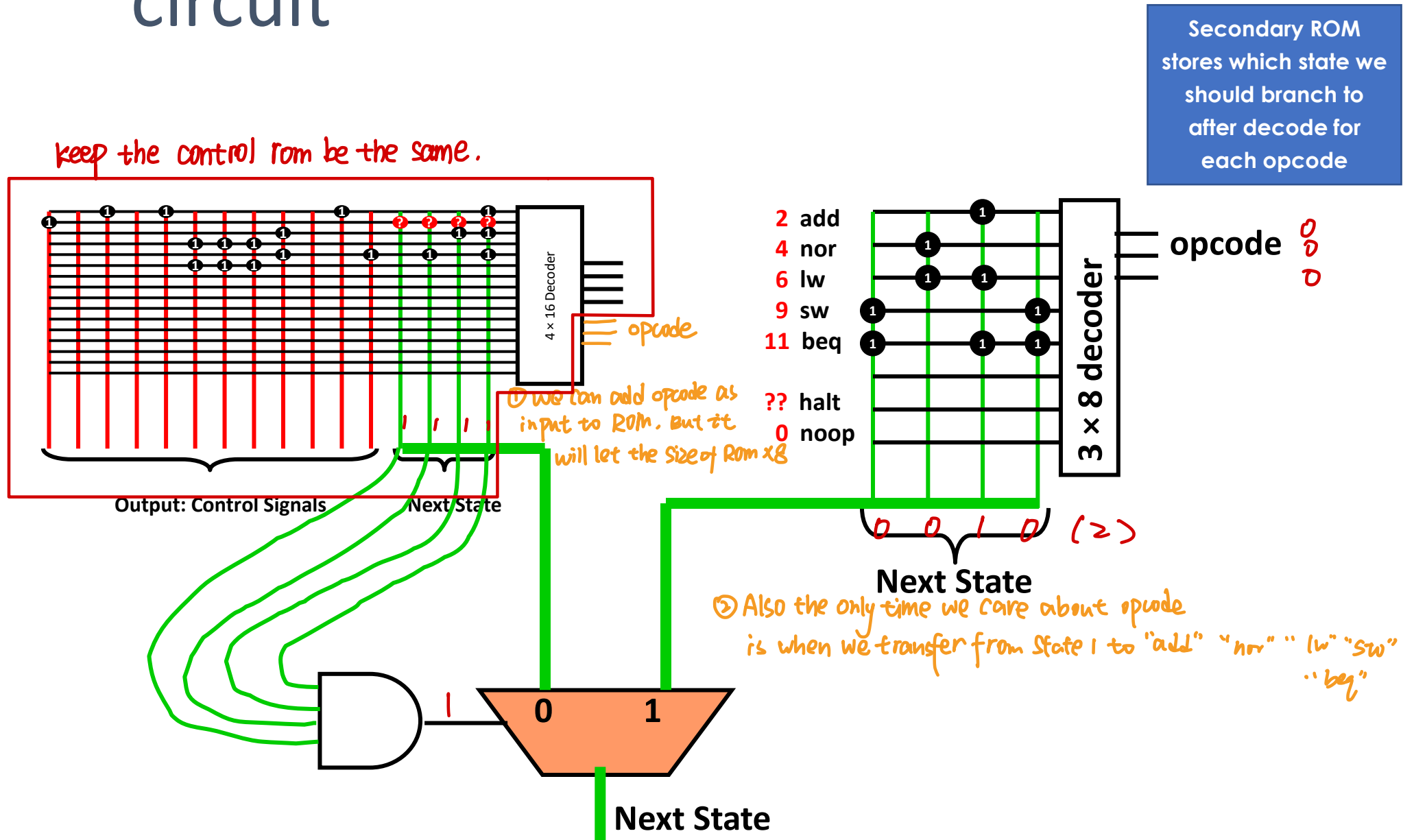

Complete transition function circuit

 

Control Rom (use of 1111 state)

 

Control Rom (use of 1111 state)

