

```

module MusicalChairs(clk, en, qtr);
    input clk;
    input en;
    output qtr;
    2 bits vector
    reg [1:0] Q; } we define the input and output of flip-flop
    reg [1:0] D; } as register
    // Corresponding inputs
    // Initial state
    initial Q = 2'b00;
    initialize the vector we defined for
    // Output logic the flip flops
    assign qtr = Q[1] && Q[0];
    // Version 1: Describe next-state logic
    //
    // FF D inputs (Combinational)
    assign D[1] = en && (Q[1] ^ Q[0]) || ~en && Q[1];
    assign D[0] = en ^ Q[0];
    // Next-State Equations
    always @(posedge clk)
    begin
        Q[1] <= D[1];
        Q[0] <= D[0];
    end

```

↓ assignment to the next state "=<" is sequential assignment.
 ↓ means repeat forever

These two assignment happens concurrently.

what we say here is } the equation we got
 we will do it repeatedly.

```

module Testbench();
    reg clk; define clock as register
    reg en;
    wire qtr;


    MusicalChairs MC(clk,en, qtr);
    // clk 10ns clock period
    always #50 clk = ~clk;

    // in
    initial
    begin
        clk = 1;
        en = 0;
        #75;
        en = 1;
        #500
        en = 0;
        #125;
    end

```

Q : How the state change

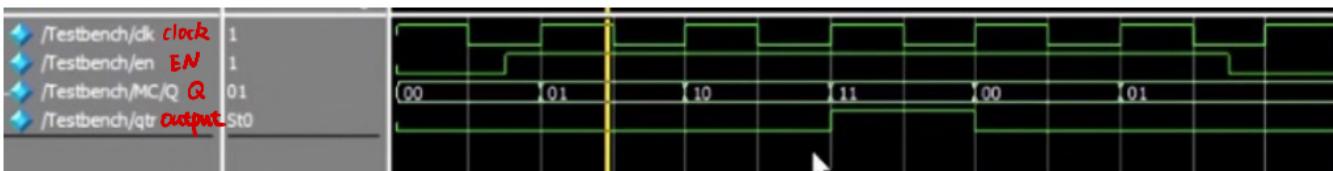A : change on a positive edge of the clock



```
// Version 2: Describe state transitions
// -----
// State Update (DFF Characteristic Equation)
always @ (posedge clk)
    Q <= D;

// Assign state labels
parameter ZERO  = 2'b00;
parameter ONE   = 2'b01;
parameter TWO   = 2'b10;
parameter THREE = 2'b11;

// State Transitions

always @ (en, Q)
begin
    I
    case (Q)
        ZERO: if (en)
            D = ONE;
        else
            D = ZERO;
        ONE:  if (en)
            D = TWO;
        else
            D = ONE;
        TWO:  if (en)
            D = THREE;
        else
            D = TWO;
        THREE: if (en)
            D = ZERO;
        else
            D = THREE;
    endcase
end
// 
endmodule
```





UM EECS 270 F22

Introduction to Logic Design

11. Design of Sequential Circuits

Sequential Circuit Design



- Goal: Design a sequential circuit that satisfies the requirements of the given problem description (spec.)
- Follow sequential circuit analysis steps in reverse!
(more or less)

- 1) (optional) Construct state diagram *"Art of design"*
- 2) Construct state/output table
- 3) Create state assignments
- 4) Create transition/output table *"Turn the crank"*
- 5) Choose FF type
- 6) Construct **excitation/output table**
 - Similar to transition/output table
- 7) Find excitation and output logic equations

Sequential Design Example

- Problem description: design a Moore sequential circuit with one input IN and one output OUT, such that OUT is one iff IN is 1 for three consecutive clock cycles
- State table:

S	IN		OUT
	0	1	
zero1s	zero1s	one1	0
one1	zero1s	two1s	0
two1s	zero1s	three1s	0
three1s	zero1s	three1s	1

S^+

- State Assignments

- What is the minimum number of state variables needed to encode four states?

2

- In general, if we have n states, what is the minimum number of state variables needed to encode those states?

$\lceil \log_2 n \rceil$

State name	Q_1	Q_0
zero1s	0	0
one1	0	1
two1s	1	0
three1s	1	1

These state assignments may seem rather arbitrary – that's because they are! We will soon see the impact that state assignments have on our final circuit...



- Transition/output table

State/Output Table:

S	IN		OUT
	0	1	
zero1s	zero1s	one1	0
one1	zero1s	two1s	0
two1s	zero1s	three1s	0
three1s	zero1s	three1s	1

Symbolic

State name	State Assignments	
	Q_1	Q_0
zero1s	0	0
one1	0	1
two1s	1	0
three1s	1	1

Transition/Output Table:

IN		OUT
Q_1	Q_0	
0	0	00 01
0	1	00 10
1	0	00 11
1	1	00 11

$Q_1^+ Q_0^+$

- Choose FF type:

- Using D flip-flops will simplify things (as we'll see below...)
easiest, because $Q^+ = D$

- Excitation table

- Shows *FF input values required to create next state values* for every current state/input combination
- If we're designing with D FFs, entries in excitation/output table are the same as those in transition/output table!

- Because of D FF characteristic equation: $Q^+ = D$

		IN		OUT
Q_1	Q_0	0	1	
0	0	00	01	0
0	1	00	10	0
1	0	00	11	0
1	1	00	11	1

$D_1 = Q_1^+ = \text{function of } (Q_1, Q_0, \text{IN})$

$D_0 = Q_0^+ = \text{function of } (Q_1, Q_0, \text{IN})$

- Excitation Logic

By looking at D_1 : we find when " $IN=0$ ", $D_1=0$

② 当 "IN=1" 时
Only when $Q_1 = Q_0 = D$ 时, $D_1 = 0$.

Excitation/Output Table:

		IN	OUT
Q_1	Q_0	0 1	
0	0	00	01
0	1	00	10
1	0	00	11
1	1	00	11
		D_1	D_0



$$D_1 = IN' \cdot 0 + IN \cdot (Q_1' \cdot Q_0')'$$

$$= IN \cdot (Q_1 + Q_0)$$



$$D_0 = IN' \cdot 0 + IN \cdot (Q_1' \cdot Q_0)'$$

$$= IN \cdot (Q_1 + Q_0')$$



- Output Logic

$$OUT = Q_1 \cdot Q_0$$

- Circuit:


Excitation Equations:

$$D_1 = IN \cdot (Q_1 + Q_0)$$

$$D_0 = IN \cdot (Q_1 + Q'_0)$$

Output Equation:

$$OUT = Q_1 \cdot Q_0$$

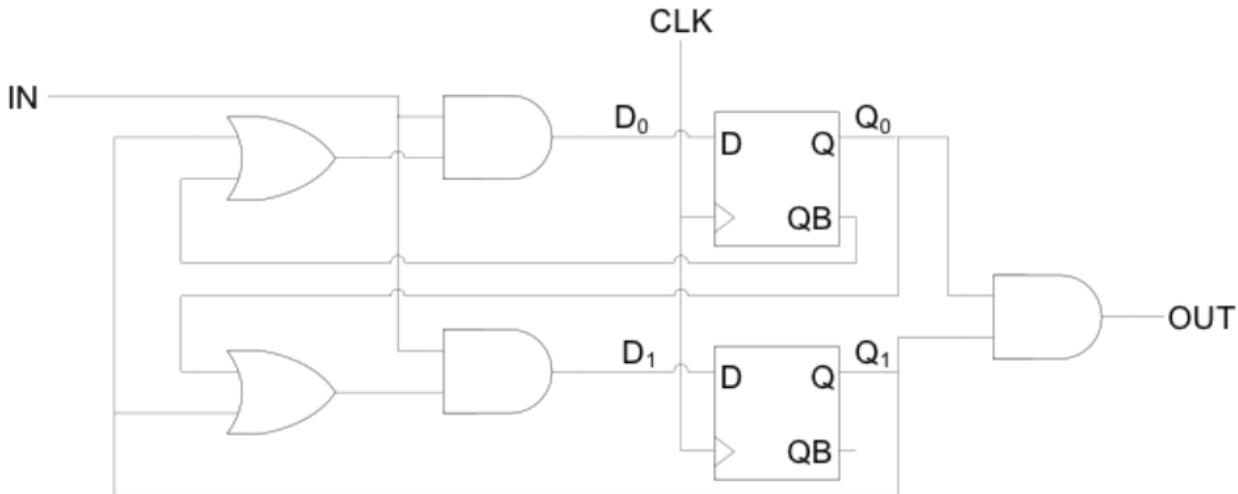


In Class Exercise



- Design a state/output table for the following problem specification:

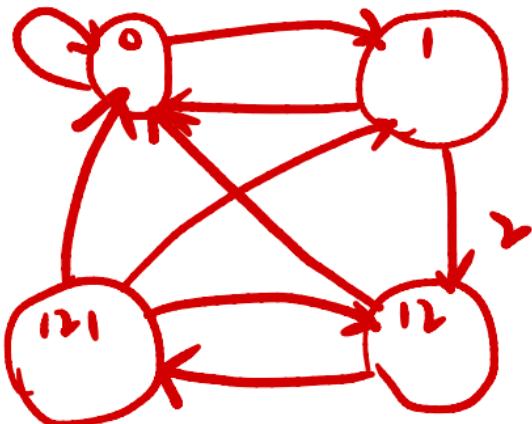Combination lock: Two inputs, X and Y, encode a binary number between 0 and 3 (X is MSB, i.e., $XY = 10 \rightarrow 2$). A single output signal UNLOCK should be set to 1 iff the sequence 1, 2, 1 occurs on the inputs in three consecutive clock cycles



Schlage BE365CAM619 Be365 Camelot Keypad Deadbolt, Satin Nickel

You purchased this item on March 3, 2019.

Style: Camelot Keypad | Color Name: Satin Nickel | Product Packaging: Standard Packaging | View this order

Try, "Alexa, reorder schlage keyless lock"



Roll over image to zoom in

Schlage BE365CAM619 Be365 Camelot Keypad Deadbolt, Satin Nickel

by **Schlage Lock Company**
5.203 customer reviews | **1000+ answered questions**

Amazon's Choice for "schlage keyless lock"

Price: **\$91.99** **prime**

Style: **Camelot Keypad**

Camelot Keypad **Camelot Keypad + Handleset** **Plymouth Keypad**

Color Name: **Satin Nickel**

Product Packaging: **Standard Packaging**

Standard Packaging **Ecommerce Packaging**

Setup options: **Get expert setup** [Details](#)

Without expert setup **Expert setup** **+\$108.17 per unit**

v What's included

- Create and delete access codes for trusted friends and family (up to 19)
- Installs in minutes - no wiring needed; Door thickness range: 1-5/8 inches to 2 inches thick (41mm-51mm) standard; Thick door kit available
- Guaranteed to fit on standard doors. Backset of universal latches and deadbolts fits 2 to 0.375 inch or 2 to 0.75 inch backsets
- Silicone-coated keypad prevents numbers from wearing off
- Pairs with our most popular trim styles to coordinate the look throughout your home
- See more product details

Buy New **\$91.99**
prime

FREE Delivery by Tuesday
if you order within 7 hrs 49 mins.
Details

In Stock.

Qty: **1**

Add to Cart **Buy Now**

Ships from and sold by Amazon.com. Gift-wrap available.

Item arrives in packaging that reveals what's inside. To hide it, choose Ship in Amazon packaging at checkout.

Add a Protection Plan:

4-Year Protection for **\$12.99**

3-Year Protection for **\$7.99**

Deliver to Karem - Ann Arbor 48103

Buy Used



In Class Exercise

- Design a state/output table for the following problem specification:

Combination lock: Two inputs, X and Y, encode a binary number between 0 and 3 (X is MSB, i.e., $XY = 10 \rightarrow 2$). A single output signal UNLOCK should be set to 1 iff the sequence 1, 2, 1 occurs on the inputs in three consecutive clock cycles

		XY				UNLOCK
S		00	01	10	11	
<i>got nothing</i>	A	A	B	A	A	0
<i>got "1"</i>	B	A	B	C	A	0
<i>got "1,2"</i>	C	A	D	A	A	0
<i>got "1,2,1"</i>	D	A	B	C	A	1

$\overline{S^+}$

FSM Transition List Design: 50s Vending Machine



- Inputs
 - **d**: asserted when user inserts dime
 - **n**: asserted when user inserts nickel
 - **c**: asserted when user presses candy button
 - **s**: asserted when user presses soda button
- Outputs
 - **dc**: dispenses candy when asserted
 - **ds**: dispenses soda when asserted
 - **cr**: 4-bit unsigned number, represents the user's credit
- Specifications *dns c has 16 combinations, but you can not press two options at the same time.*
 - All inputs are one-hot *can not press two options at the same time.*
 - Candy costs 10 cents, soda costs 15 cents
 - Money need only be counted up to 15 cents

Vending Machine State Diagram and Transition List

Not all of the inputs are indicated on the arrows

all transitions out of the state are mutually exclusive

is the implement
of n.ord. (n+d)

n·d


means:

I'm staying in that state. [look it as consistency condition for transitions to make the machine on circuit deterministic.]

By definition

"d and n" must be 0, because they are "one-hot".

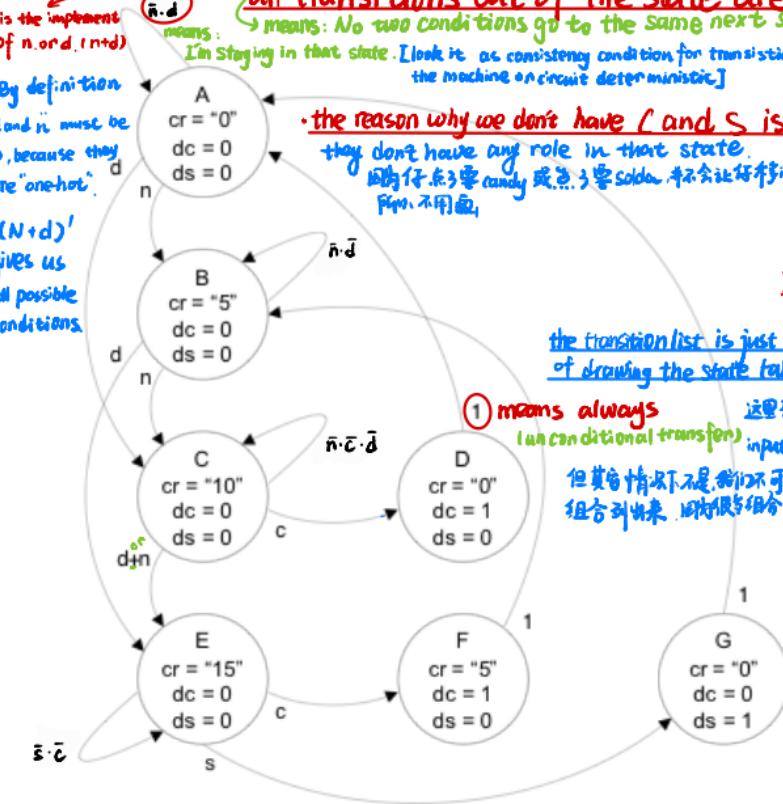$(N+d)$
gives us
all possible
conditions.



Output Table

	Q ₂ Q ₁ Q ₀	cr	dc	ds
A	0 0 0	"0"	0	0
B	0 0 1	"5"	0	0
C	0 1 0	"10"	0	0
D	0 1 1	"0"	1	0
E	1 0 0	"15"	0	0
F	1 0 1	"5"	1	0
G	1 1 0	"0"	0	1

Each row in the List is an arrow in the diagram.

Transition List

S	Q ₂ Q ₁ Q ₀	Transition Expression	S'	Q ₂ 'Q ₁ 'Q ₀ '
A	0 0 0	n	B	0 0 1
A	0 0 0	d	C	0 1 0
A	0 0 0	n·d	A	0 0 0
B	0 0 1	n	C	0 1 0
B	0 0 1	d	E	1 0 0
B	0 0 1	n·d	B	0 0 1
C	0 1 0	n+d	E	1 0 0
C	0 1 0	c	D	0 1 1
C	0 1 0	n·d·c	C	0 1 0
D	0 1 1	1	A	0 0 0
E	1 0 0	c	F	1 0 1
E	1 0 0	s	G	1 1 0
E	1 0 0	s·c	E	1 0 0
F	1 0 1	1	B	0 0 1
G	1 1 0	1	A	0 0 0

不理解
对一些输入是
1位输入但是
symbolic. 12为
这里我们说一
位输入没有用binary的方
式表示. 而是使用312

Transition List

S	$Q_2 Q_1 Q_0$	Transition Expression	S^*	$Q_2^* Q_1^* Q_0^*$
A	0 0 0	n	B	0 0 1
A	0 0 0	d	C	0 1 0
A	0 0 0	$n-d$	A	0 0 0
B	0 0 1	n	C	0 1 0
B	0 0 1	d	E	① 0 0
B	0 0 1	$\bar{n}-\bar{d}$	B	0 0 1
C	0 1 0	$n+d$	E	① 0 0
C	0 1 0	c	D	0 1 1
C	0 1 0	$\bar{n}-\bar{d}-\bar{c}$	C	0 1 0
D	0 1 1	1	A	0 0 0
E	1 0 0	c	F	① 0 1
E	1 0 0	s	G	① 1 0
E	1 0 0	$\bar{s}-\bar{c}$	E	① 0 0
F	1 0 1	1	B	0 0 1
G	1 1 0	1	A	0 0 0

Output Table

$Q_2 Q_1 Q_0$	cr	dc	ds
A 0 0 0	"0"	0	0
B 0 0 1	"5"	0	0
C 0 1 0	"10"	0	0
D 0 1 1	"0"	①	0
E 1 0 0	"15"	0	0
F 1 0 1	"5"	①	0
G 1 1 0	"0"	0	①

搞清楚 D_2, D_1, D_0 与 什么有关

input + State Variable
 n,d,s,c $Q_0 Q_1 Q_2$

$$D_2 = Q_2^+ = \bar{Q}_2 \bar{Q}_1 Q_0 d + \bar{Q}_2 Q_1 \bar{Q}_0 (n+d) + Q_2 \bar{Q}_1 \bar{Q}_0 c + Q_2 \bar{Q}_1 \bar{Q}_0 s + Q_2 \bar{Q}_1 \bar{Q}_0 sc$$

$$D_1 = Q_1^+ = \bar{Q}_2 \bar{Q}_1 \bar{Q}_0 d + \bar{Q}_2 \bar{Q}_1 Q_0 n + \bar{Q}_2 Q_1 \bar{Q}_0 c + \bar{Q}_2 Q_1 \bar{Q}_0 ndc + Q_2 \bar{Q}_1 \bar{Q}_0 s$$

$$D_0 = Q_0^+ = \bar{Q}_2 \bar{Q}_1 \bar{Q}_0 n + \bar{Q}_2 \bar{Q}_1 Q_0 \bar{nd} + \bar{Q}_2 Q_1 \bar{Q}_0 c + Q_2 \bar{Q}_1 \bar{Q}_0 c + Q_2 \bar{Q}_1 Q_0$$

excitation equation

$$dc = Q_2 Q_1 Q_0 + Q_2 Q_1 \bar{Q}_0$$

$$ds = Q_2 Q_1 \bar{Q}_0$$

output equation

...

Transition List

S	$Q_2 Q_1 Q_0$	Transition Expression	S^*	$Q_2^+ Q_1^+ Q_0^+$
A	0 0 0	n	B	0 0 1
A	0 0 0	d	C	0 1 0
A	0 0 0	$\bar{n} \cdot \bar{d}$	A	0 0 0
B	0 0 1	n	C	0 1 0
B	0 0 1	$n \cdot d$	B	0 0 1
C	0 1 0	c	D	0 1 1
C	0 1 0	$\bar{n} \cdot \bar{d} \cdot \bar{c}$	C	0 1 0
D	0 1 1	1	A	0 0 0
E	1 0 0	c	F	1 0 1
E	1 0 0	s	G	1 1 0
E	1 0 0	$\bar{s} \cdot \bar{c}$	E	1 0 0
F	1 0 1	1	B	0 0 1
G	1 1 0	1	A	0 0 0

Output Table

$Q_2 Q_1 Q_0$	cr	dc	ds
A 0 0 0	"0"	0	0
B 0 0 1	"5"	0	0
C 0 1 0	"10"	0	0
D 0 1 1	"0"	1	0
E 1 0 0	"15"	0	0
F 1 0 1	"5"	1	0
G 1 1 0	"0"	0	1

$$D_2 = Q_2^+ = \bar{Q}_2 \bar{Q}_1 Q_0 d + \bar{Q}_2 Q_1 \bar{Q}_0 (n+d) \\ + Q_2 \bar{Q}_1 \bar{Q}_0 c + Q_2 \bar{Q}_1 \bar{Q}_0 s + Q_2 \bar{Q}_1 \bar{Q}_0 sc$$


$$D_1 = Q_1^+ = \bar{Q}_2 \bar{Q}_1 \bar{Q}_0 d + \bar{Q}_2 \bar{Q}_1 Q_0 n + \bar{Q}_2 Q_1 \bar{Q}_0 c \\ + \bar{Q}_2 Q_1 \bar{Q}_0 ndc + Q_2 \bar{Q}_1 \bar{Q}_0 s$$

$$D_0 = Q_0^+ = \bar{Q}_2 \bar{Q}_1 \bar{Q}_0 n + \bar{Q}_2 \bar{Q}_1 Q_0 \bar{nd} + \bar{Q}_2 Q_1 \bar{Q}_0 c \\ + Q_2 \bar{Q}_1 \bar{Q}_0 c + Q_2 \bar{Q}_1 Q_0$$



$$dc = \bar{Q}_2 Q_1 Q_0 + Q_2 \bar{Q}_1 Q_0$$

$$ds = Q_2 Q_1 \bar{Q}_0$$

...

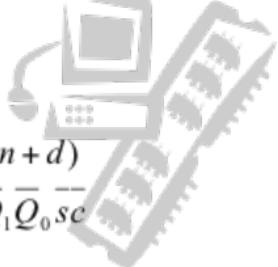

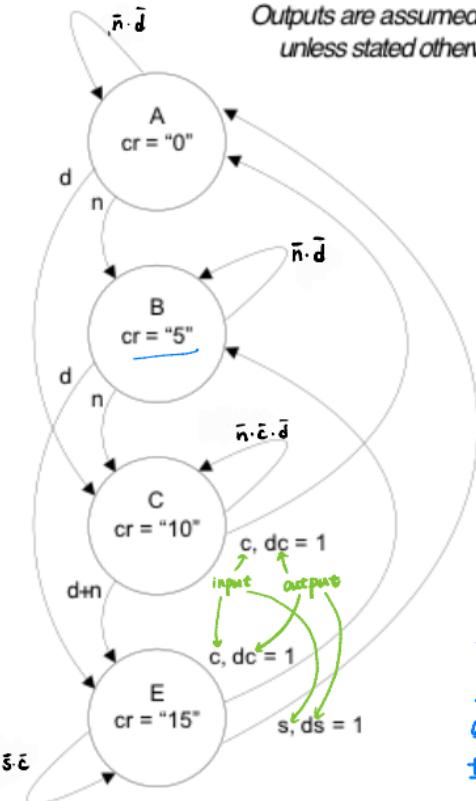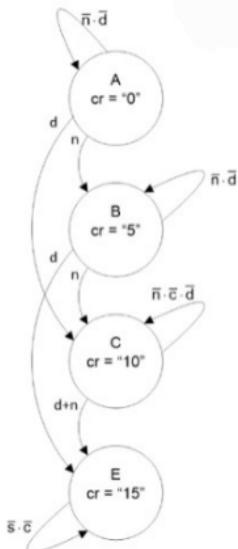50s Vending Machine: Mealy Implementation



The Mealy implementation uses fewer states, and therefore fewer FFs!

Q: What is the difference between state table and transition table.

A: State table is in terms of symbolic names of states (but not binary) —> once you make a state assignment, the state table becomes a transition table.