



UM EECS 270 F22

Introduction to Logic Design

10. Analysis of Sequential Circuits

Sequential Circuits



- Modeled as **Finite** State Machines
- Timing behavior:
 - Synchronous (clocked)
 - Asynchronous



Our Focus: **Synchronous** Sequential Circuits

不考虑时间, 使 functionality correct


Timing: How fast is this thing

- Sequential Circuit Components:

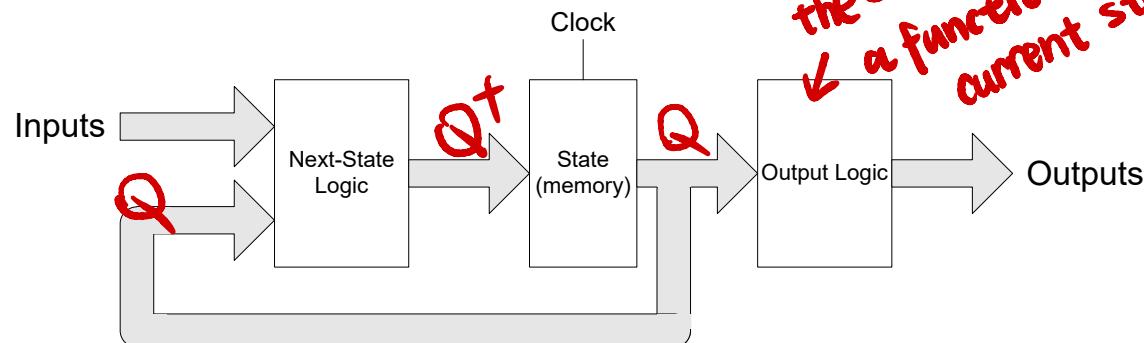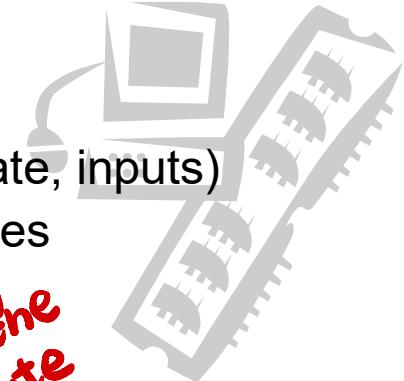- **Next state logic (combinational)**: $\text{next state} = f(\text{current state}, \text{inputs})$
- **Memory (sequential)**: stores state in terms of state variables
- **Output logic (combinational)**:
 - Moore Output: $\text{output} = g(\text{current state})$



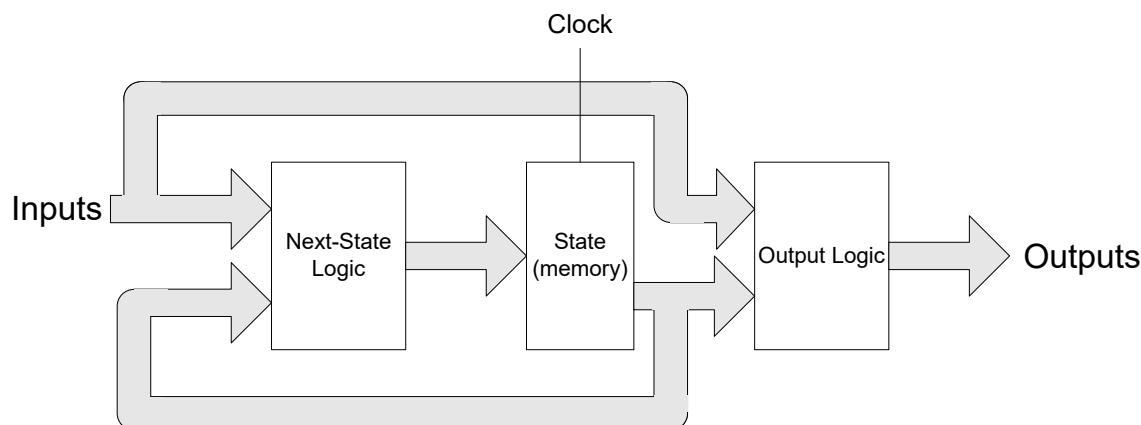
- Mealy Output: $\text{output} = g(\text{current state}, \text{inputs})$




Sequential Circuit Analysis



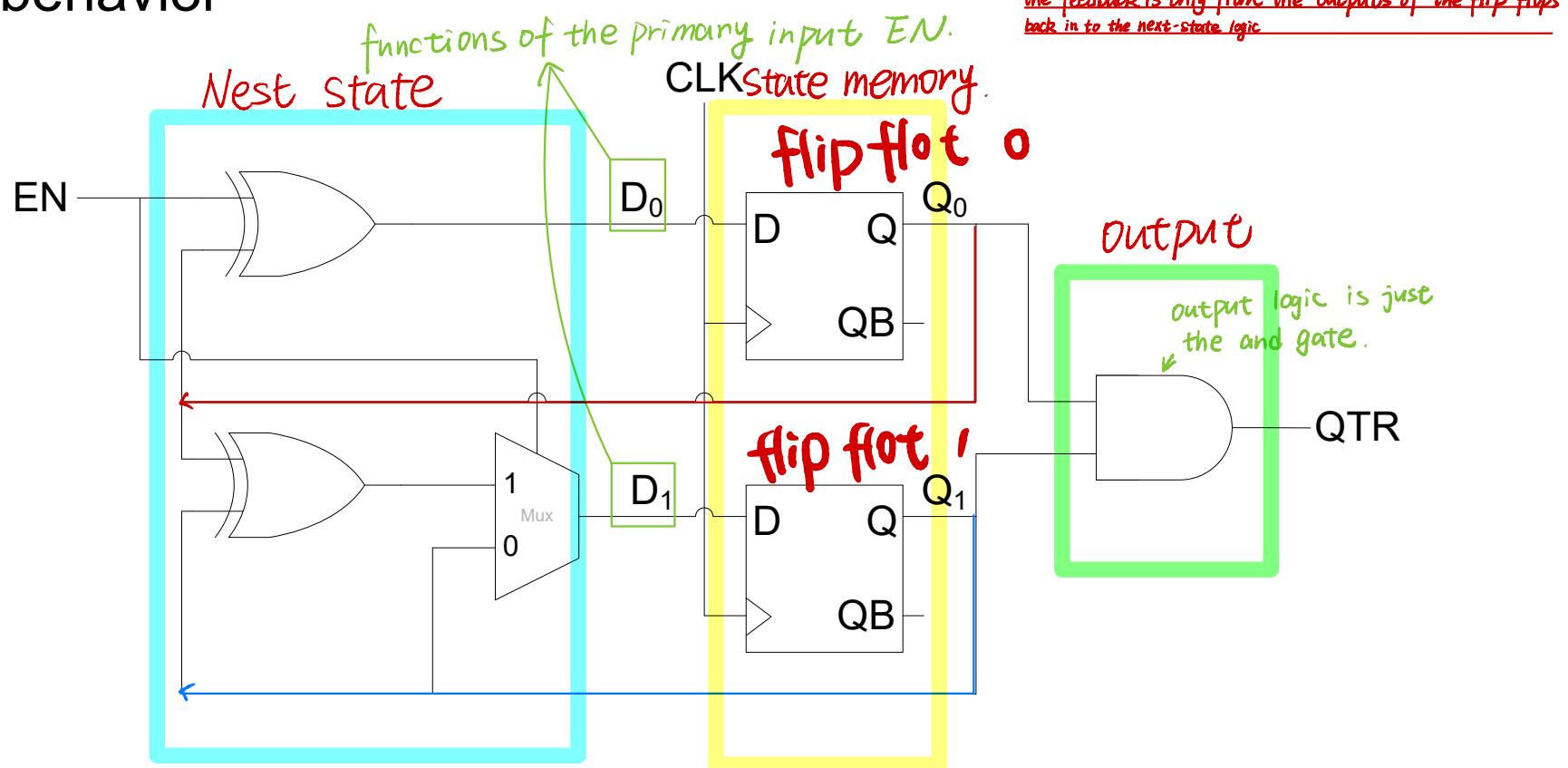
- Goal: Given a sequential circuit, describe the circuit's behavior



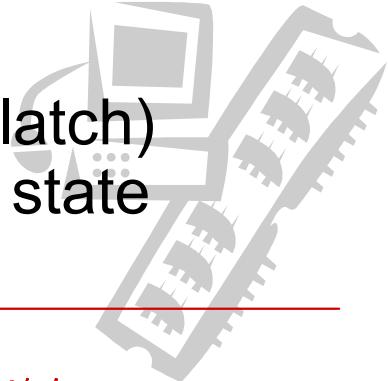- **Excitation equations** describe memory (FF or latch) input signals as a function of inputs and current state (i.e., state variables)



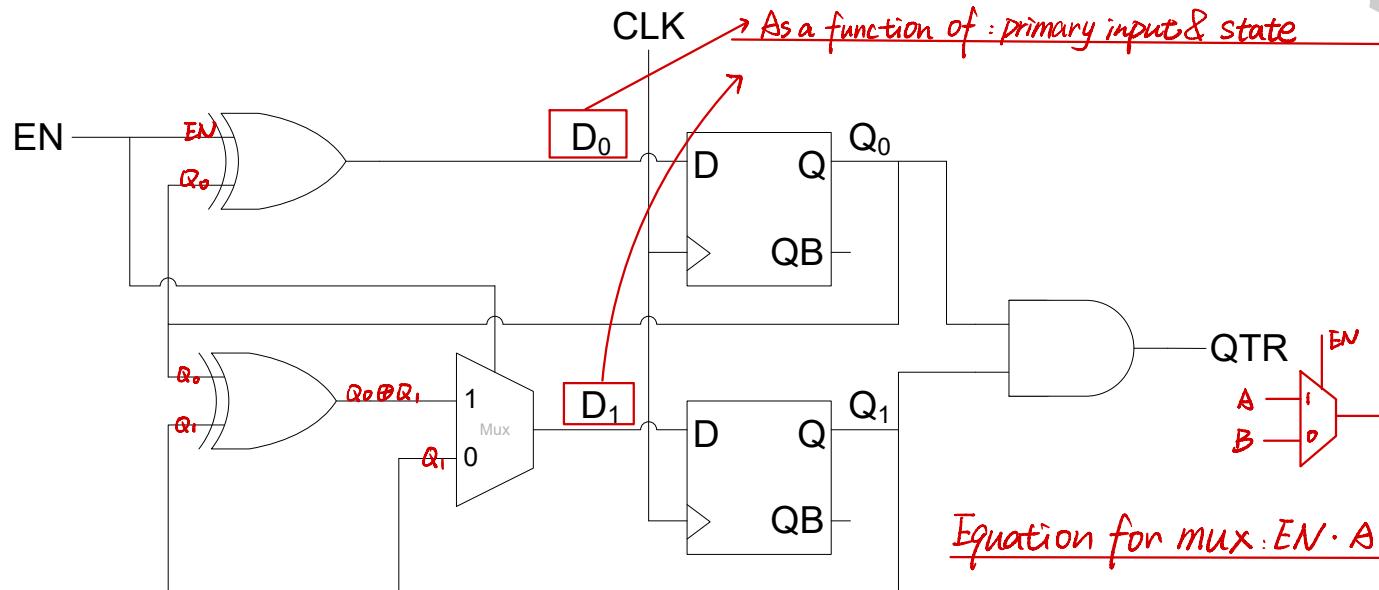excitation logic equations : excite the flip flops.



Equation for mux : $EN \cdot A + \bar{EN} \cdot B$


Excitation Equations: they excite the flip flop.

$$D_0 = EN \oplus Q_0$$

$$D_1 = EN \cdot (Q_0 \oplus Q_1) + \bar{EN} \cdot Q_1$$

- **Transition equations** describe the next state as a function of inputs and current state

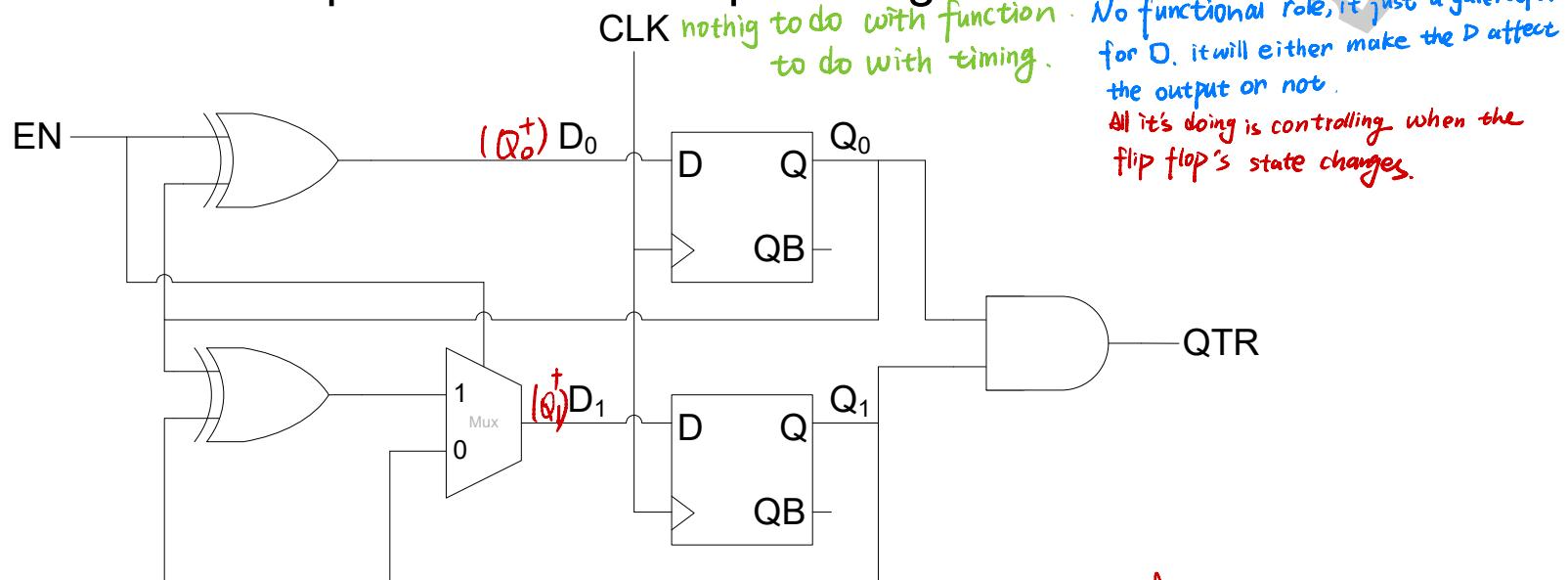- Generated by substituting the excitation equations into the characteristic equation for the sequential gates



D FF Characteristic Eqn:
特征方程

$$Q^+ = D$$



Next state f (IN, PS)
Transition Equations:

$$Q_0^+ = D_0 = EN \oplus Q_0$$

$$Q_1^+ = D_1 = EN \cdot (Q_0 \oplus Q_1) + \overline{EN} \cdot Q_1$$

This step is trivial when using D FFs!

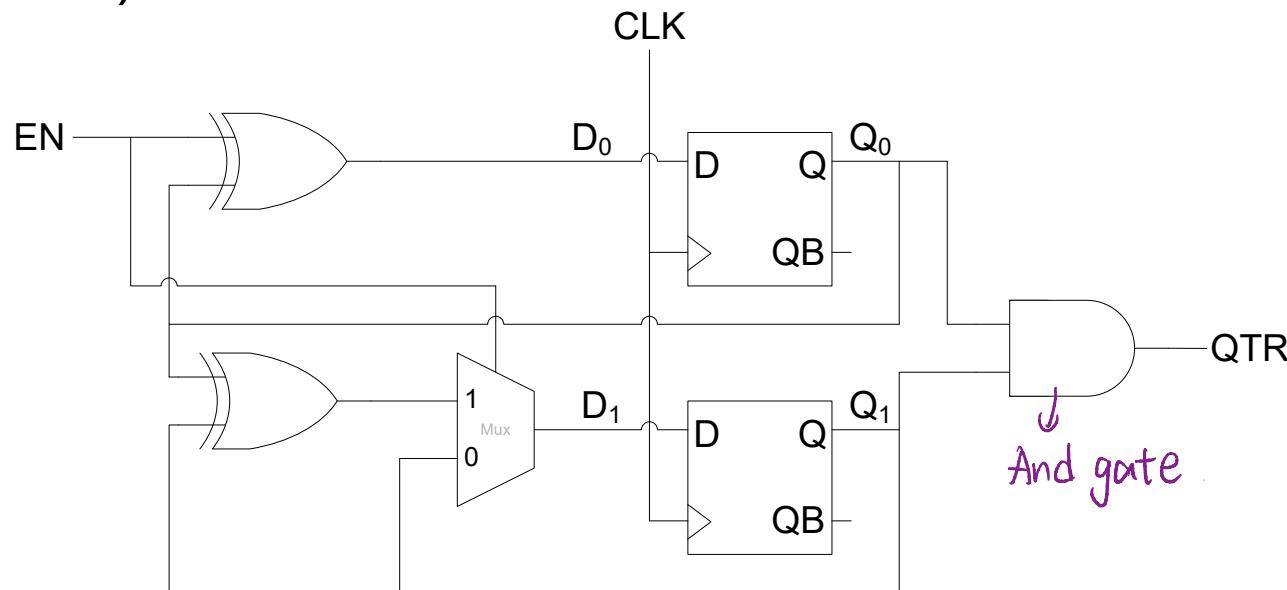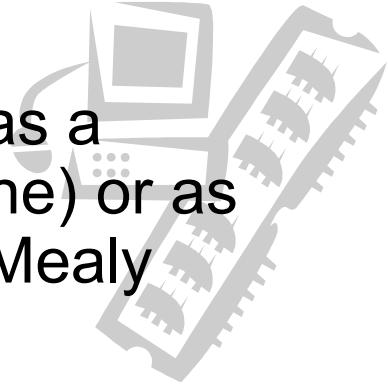
- **Output equations** describe the output signals as a function of the current state (for a Moore machine) or as a function of the current state and inputs (for a Mealy machine)



Output Equation:

$$QTR = Q_0 \cdot Q_1$$

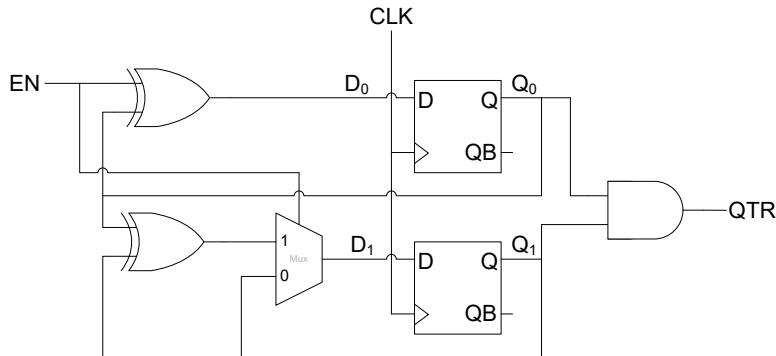- The transition/output table shows the next state and output for every current state/input combination
 - Entries of the table are obtained from the transition equations and the output equations



Transition Equations:

we have three
input: EN, Q_0 , Q_1

$$Q_0^+ = D_0 = EN \oplus Q_0$$

$$Q_1^+ = D_1 = EN \cdot (Q_0 \oplus Q_1) + \overline{EN} \cdot Q_1$$

Output Equation:

$$QTR = Q_0 \cdot Q_1$$

针对于一个 sequential circuit.

对应一个 input 和目前有的 current states, Q .
(因为 flip flop 不另一个, 所以 Q_2 也不另一个).

Q 会 transit 成 Q^+ . 也就是一个组合 bits 的多少
取决于 Q 的多少 (也就是 flip flops 的多少).

于是我们就通过 Q^+ 的 bits 的多少推导出有几种可能的 Q^+ .

Transition 就是从 $Q \rightarrow Q^+$ 的过程, 所以左侧是 current state Q .
 Q^+ 取决于 input 和 Q , 由 transition equation 来描述具体的 logic combination 的逻辑. 而 output P 取决于 current state.

名字的由来是因为

中间是 transition 的结果, 左侧是 output 的结果.

Transition/Output Table: 中间是 transition 的结果, 左侧是 output 的结果.

A possible current state		input	output
Q_1	Q_0	EN	QTR
0	0	00	0
0	1	01	0
1	0	10	0
1	1	11	1

Q_1^+ Q_0^+

next state

transition function 如何计算.

- **State labels** are a one-to-one mapping from state encodings to state names



- 并且左侧的 current state Q_i 也可以被集中起来表示

Q_1	Q_0	State name
0	0	A
0	1	B
1	0	C
1	1	D

• 给每个 state 编号 (Binary number)

• state 一共有 4 个.

一个是 current state, 另一个是 next state.

- 所以图表中间显现的不再是每个 flip flop 的 output 怎么变, 而是简化成 state 怎么变.

- The **state/output table** has the same format as the transition table, but state names are substituted in for state encodings

Transition/Output Table:

Q_1	Q_0	EN	QTR
0	0	00	01
0	1	01	10
1	0	10	11
1	1	11	00

we just change from bits to labels.

State Assignments

Q_1	Q_0	State name
0	0	A
0	1	B
1	0	C
1	1	D

State value (4)
State/Output Table:

S	EN	QTR
A	0	A
B	0	B
C	0	C
D	1	D


所以 Transition / output table 和 State / output table 相比就是去掉所有单独出现的 Q_0 , Q_1 , Q_0^+ , Q_1^+ , 而是按照 current 和 Next

- A **state diagram** is a graphical representation of the information in the state/output table
- **Nodes** (or vertices) represent states
 - Moore machines: output values are written in state node
- **Arcs** (or edges) represent state transitions
 - Labeled with a transition expression
 - when an arc's transition expression evaluates to 1 for a given input combination, that arc is followed to the next state
 - Mealy machines: output values (or expressions) are written on arcs


State/Output Table:

S	EN	QTR	
S	0	1	QTR
A	A	B	0
B	B	C	0
C	C	D	0
D	D	A	1

S^+

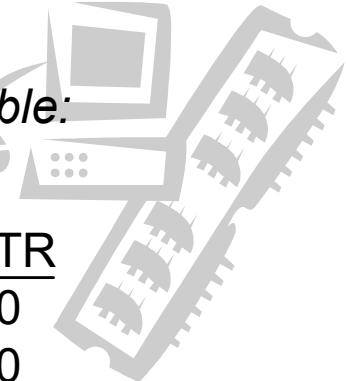

State Diagram:

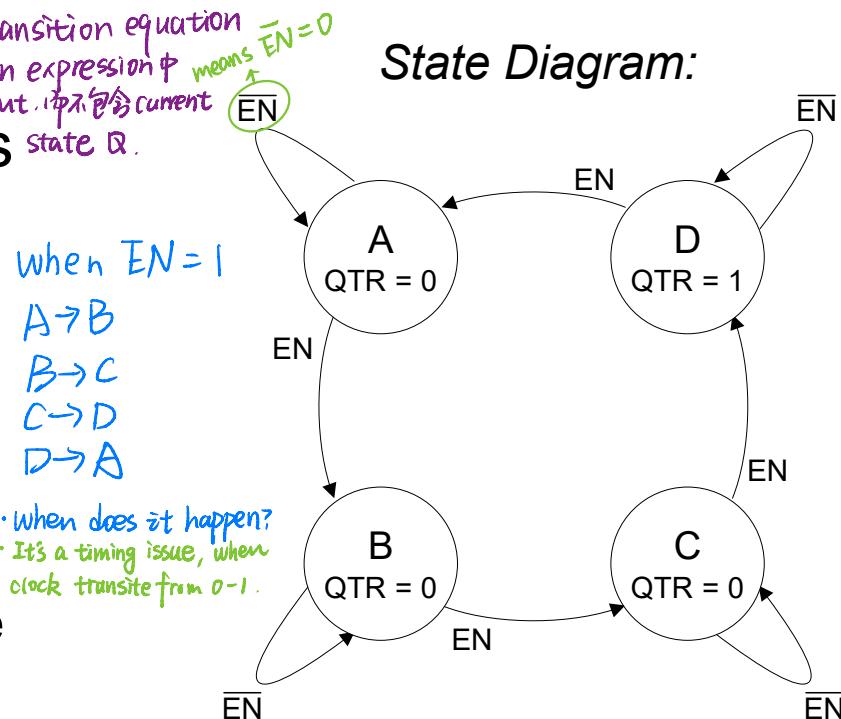



Sequential Circuit Analysis Recap

- 1) Find the circuit's excitation equations $D = (\text{input \& current state})$
- 2) Using the excitation and characteristic equations, write the circuit's transition equations $Q^+ \text{ 与 } D \text{ 之间的关系.}$
- 3) Write the circuit's output equations
- 4) From the transition and output equations, create the circuit's transition/output table
- 5) Create state labels
- 6) Using the transition table and state labels, create the state table $\text{state/output table}$.
- 7) (optional) Draw the circuit's state diagram.