

UNIVERSITY OF MICHIGAN

EECS 270: Intro to Logic Design

Midterm Exam 2

Prof. Kareem A Sakallah

Monday March 30, 2020

6:00-8:00 p.m.

A - K: 1013 DOW || L - R: 1014 DOW || S - Z: 1005 DOW

Name: _____

UMID: _____

Honor Pledge:

"I have neither given nor received aid on this exam, nor have I concealed any violation of the Honor Code."

Signature: _____


Instructions:

- | | |
|--|------------------|
| • The exam is closed book except for two 8.5"x11" sheets of notes.
No electronics of any kind may be used. | 1. _____/20 |
| | 2. _____/20 |
| | 3. _____/20 |
| • Print your name and student ID number and sign the honor
pledge. | 4. _____/10 |
| | 5. _____/20 |
| | 6. _____/10 |
| • The exam consists of 6 problems with the point distribution
indicated here. Please keep this in mind as you work through
the exam. Use your time wisely. | Total: _____/100 |
| • There are 13 sheets in this exam. Make sure that you have all
13 sheets and notify an instructor if you do not. | |

1 [Weird Latches—20 points]

 a. [7 points]

[6 Points] Complete the function table for this proposed latch.




X	Y	Q^+	QB^+	Function
0	0			
0	1			
1	0			
1	1			

[0.5 Points] Is this a valid latch? _____

[0.5 Points] If not valid, why not? _____

 b. [7 points]

[6 Points] Complete the function table for this proposed latch.




X	Y	Q^+	QB^+	Function
0	0			
0	1			
1	0			
1	1			

[0.5 Points] Is this a valid latch? _____

[0.5 Points] If not valid, why not? _____

Continued on next page


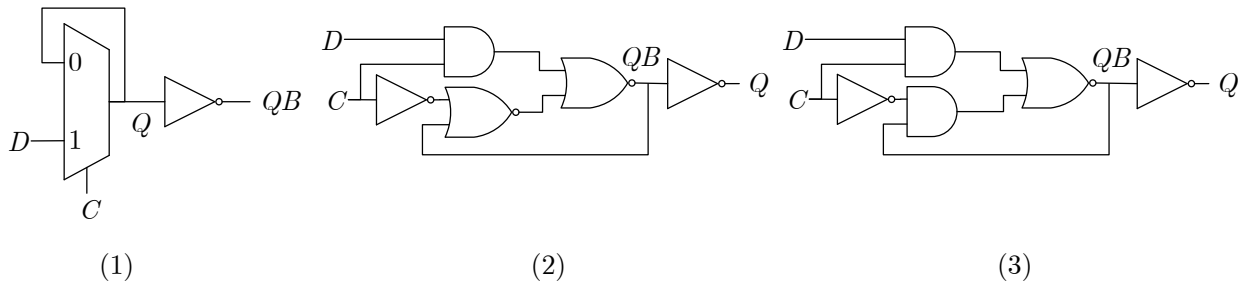
- c. **[6 points]** Circuits 1, 2, and 3 below are proposed as possible implementations of a D latch. Which of the following statements is true?



- (a) Only one of the circuits is a D latch.
- (b) Only circuits 1 and 2 are D latches.
- (c) Only circuits 2 and 3 are D latches.
- (d) Only circuits 1 and 3 are D latches.
- (e) All three circuits are D latches.

2 [Timing Analysis–20 points]

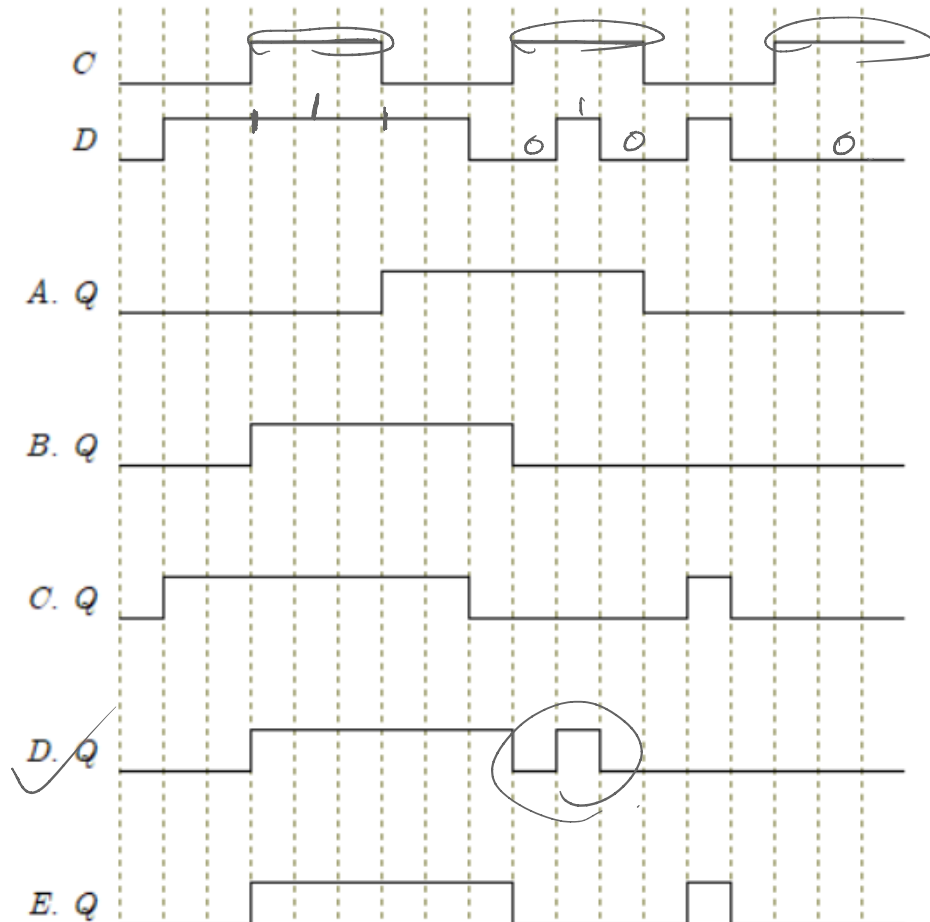 
- a. [4 points] Consider the positive level-sensitive D latch shown below along with the given waveforms for its C and D inputs. Which of the following choices is the correct response at the output Q ? You may ignore propagation delays.



Continued on next page

B


 
- b. [4 points] Consider the back-to-back negative edge-triggered flip-flop and positive level-sensitive latch shown here as a *single flip-flop*. Let $C \uparrow$ and $C \downarrow$ denote, respectively, the rising and falling edges of the clock input C . Let S and H denote the setup and hold constraints. Which of the following statements is true?




- (a) S and H must be checked against $C \uparrow$; Q changes shortly after $C \uparrow$.
 (b) S and H must be checked against $C \downarrow$; Q changes shortly after $C \uparrow$.
 (c) S and H must be checked against $C \downarrow$; Q changes shortly after $C \downarrow$.
 (d) S and H must be checked against $C \uparrow$; Q changes shortly after $C \downarrow$.
 (e) S must be checked against $C \uparrow$, and H against $C \downarrow$; Q changes shortly after $C \downarrow$.

Continued on next page

- c. **[12 points]** Annotate the waveforms for D_1 , J_0 , and K_0 in the following sequential circuit with their early a and late A arrival times and calculate the maximum frequency that allows this circuit to operate without timing violations. *Note that waveform transitions in the timing diagram are not meant to be exact, just representative.*

 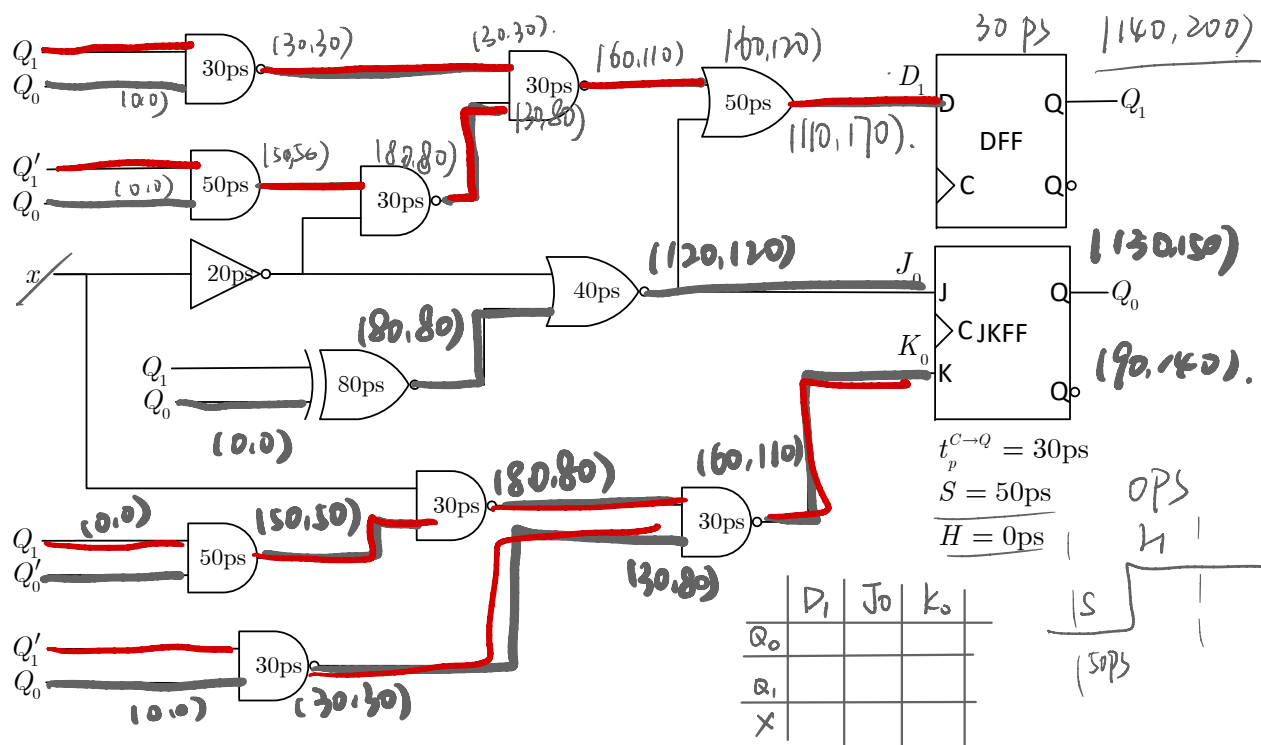
$$A = 140$$
$$A = 200$$
 
$$A = 150$$
$$A = \begin{pmatrix} 1 & 0 \\ 0 & 1 \end{pmatrix}$$

$$A = (90)$$
$$A = (140.)$$

$$f_{max} = 700 + 50 = 750 \text{ ns}$$

$$f_{\max} = \frac{1}{4 \times 10^{-4} \text{ s}} = 4 \text{ GHz}$$

3 [Two-level Minimization—20 points]

- a. **[6 points]** Which of the following K-maps is for a function that has no essential prime implicants in a minimal SOP expression for the function?

A.

		<i>cd</i>			
		00	01	11	10
00					
01					
11	<i>ab</i>	1			1
10		1			1

B.

		<i>cd</i>			
		00	01	11	10
00			1	1	
01				1	
11	<i>ab</i>		1	1	
10			1		

C.

		<i>cd</i>			
		00	01	11	10
00				1	
01					
11	<i>ab</i>		1	1	1
10		1		1	

D.

		<i>cd</i>			
		00	01	11	10
00				1	
01					
11	<i>ab</i>	1	1		1
10		1		1	

E.

		<i>cd</i>			
		00	01	11	10
00			1	1	
01				1	
11	<i>ab</i>		1	1	
10		1	1		

Answer: _____

- b. **[6 points]** Find minimal SOP and POS solutions for the function $f(w, x, y, z)$ whose K-map is shown below.

		yz			
		00	01	11	10
wx	00	1	1	0	X
	01	0	1	0	0
	11	0	X	X	X
	10	1	X	0	0

$f^{\text{SOP}}(w, x, y, z) =$ _____

$f^{\text{POS}}(w, x, y, z) =$ _____

- c. **[8 points]** Consider the function $g(a, b, c, d)$ whose K-map is shown below.

		cd			
		00	01	11	10
ab	00	1	1	1	1
	01	1	0	1	1
	11	1	1	1	1
	10	1	1	1	0


[4 Points] How many prime implicants does g have? _____

[2 Points] How many essential prime implicants does g have? _____


[2 Points] The number of literals in the minimal POS solution for g is: _____

4 [Sequential Circuit Analysis–10 points]

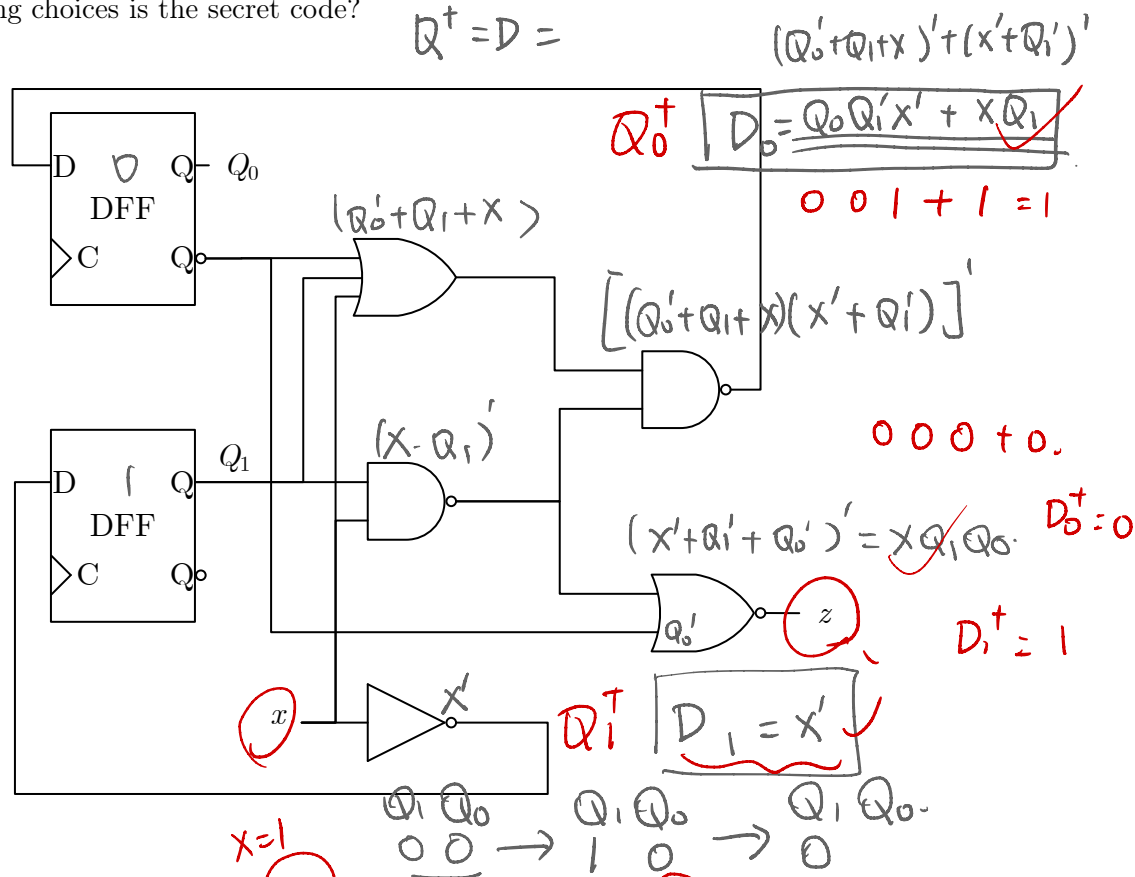- a. **[2 points]** The following sequential circuit sets its output z to 1 when the appropriate secret code is entered on its input line x . Your job is to figure out what that secret code is! Assuming that the circuit is reset to state $Q_1Q_0 = 00$ before application of any input, which of the following choices is the secret code?



 - (a) 0101
(b) 1010
(c) 1101
(d) 0110
(e) 0100



$$Q_1 = 0 \quad Q_0 = 1$$

$$Q_0^+ = Q_1' Q_0 X' + X Q_1$$

$$Q_0^T = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix}$$

$$Q_b^T = [$$

Continued on next page


Page 9

$Q_1^+ = 1$ $Q_2^+ = 0 \cdot 1 \cdot 1 + 0 \cdot 0 = 0$

b. [8 points] Given the state assignment

Q_1Q_0	State Label
00	A
01	B
10	C
11	D

 derive the state table for the following synchronous sequential circuit.



Present State	$x = 0$	$x = 1$
A		
B		
C		
D		
Next State		

5 [Sequential Synthesis—20 points]

Complete the design of the sequential circuit which is described by the following transition and output table:

$Q_1 Q_0$	$x = 0$	$x = 1$	z
00	01	11	0
01	00	10	1
11	01	00	1
10	11	01	0

$x=0$ $x=1$
 $0 \rightarrow 1$ $0 \rightarrow 1$
 $1 \rightarrow 0$ $1 \rightarrow 0$
 $1 \rightarrow 1$ $1 \rightarrow 0$
 $0 \rightarrow 1$ $0 \rightarrow 1$

[12 Points] Using a D flip-flop for Q_1 and a JK flip-flops for Q_0 , complete the following K-maps and derive minimal SOP solutions for D_1 , J_0 , K_0 , and z .

x

	0	1
00	0	1
01	0	1
11	0	0
10	1	0

$Q_1 Q_0$

x

	0	1
00	1	1
01	X	X
11	X	X
10	1	1

x

	0	1
00	X	X
01	1	1
11	0	1
10	X	X

$Q_1 Q_0$

$$D_1 \Rightarrow Q_1^+$$

$$J_0$$

$$Q_0^+$$

$$K_0$$

$$z$$

[2 Points] $D_1^{\text{SOP}}(x, Q_1, Q_0) = Q_1 Q_0' X' + X Q_1'$

[2 Points] $J_0^{\text{SOP}}(x, Q_1, Q_0) = 1$

[2 Points] $K_0^{\text{SOP}}(x, Q_1, Q_0) = X + Q_1'$


[2 Points] $z^{\text{SOP}}(x, Q_1, Q_0) = Q_0$

6 [Lab Experience—10 points]

You are given the task of implementing a piecewise linear function in hardware for fast computation. It consists of 4 continuous functions. You start simple by limiting the input ranges as follows:

$$\begin{aligned} y &= 3x & x &= 0 - 3 \\ y &= 2x + 3 & x &= 4 - 6 \\ y &= x + 9 & x &= 7 - 9 \\ y &= 18 & x &= 10 - 31 \end{aligned}$$

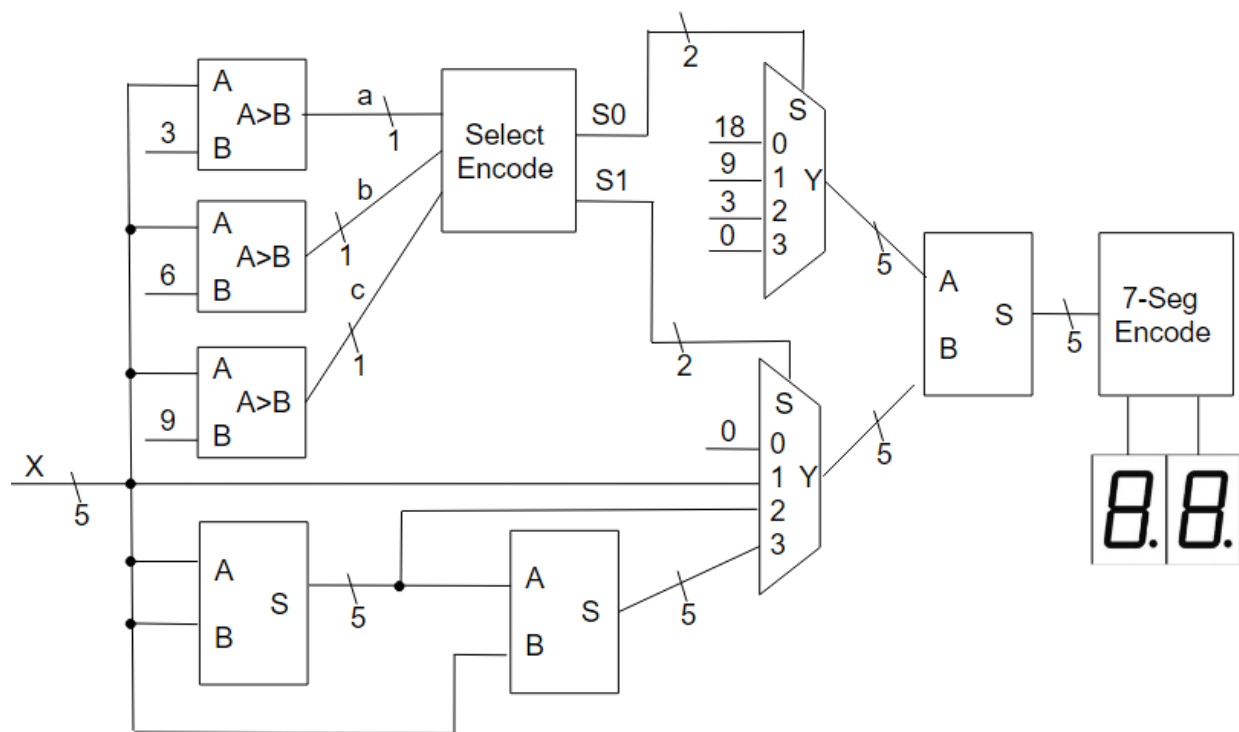The FPGA and tools you are using will only synthesize adders, multiplexers, comparators and various combinational logic. Given these restrictions you come up with the following design that uses 5-bit comparators, 5-bit adders, 5-bit multiplexers and various logic. You can assume input x is limited to the unsigned integers 0 to 31.



Complete the following Verilog that implements this design. You will need to complete some declarations, connections between modules, the 5-bit 4 to 1 multiplexer and the select encode module. You can assume the 5-bit adder, 5-bit comparator and 7-segment encoder are provided. Point values are listed on each line for a **total of 10 points**.

```

module pwf(x, y10, y1);

input [4:0] x; //argument x
output [5:0] y10, y1; //7seg display

_____ a,b,c; (1 point)
_____ s0, s1; (1 point)
_____ sum2x, sum3x, y0, y1, y; (1 point)

five_bit_comparator c0(_____); (0.5 point)
five_bit_comparator c1(_____); (0.5 point)
five_bit_comparator c2(_____); (0.5 point)
select_encode e0(a, b, c, s0, s1);

five_bit_adder a0(_____); (0.5 point)
five_bit_adder a1(_____); (0.5 point)
five_bit_4to1mux m0(0, 3, 9, 18, y0);
five_bit_4to1mux m1(0, x, sum2x, sum3x, y1);
five_bit_adder a2(y0, y1, y);
seven_seg_encoder el(y, y1, y10); //
endmodule

_____ (a,b, c, s0, s1); (0.5 point)
input a, b, c;
output [1:0] s0, s1;

assign s0[0] = _____; (0.5 point)
assign s0[1] = _____; (0.5 point)
assign s1[0] = _____; (0.5 point)
assign s1[1] = _____; (0.5 point)
endmodule

_____ (a0, a1, a2, a3, sel, y); (0.5 point)
input [4:0] a0, a1, a2, a3;
input [1:0] sel;
output [4:0] y;

_____ = (sel == 0) ? a0: (0.5 point)
              (sel == 1) ? _____: (0.5 point)
              (sel == 2) ? _____: (0.5 point)
endmodule

```