



# UM EECS 270 F22

## Introduction to Logic Design

### 12. Two-Level Logic Minimization

# Logic Synthesis: From Specs to Circuits

- Implementation Styles
  - Random
  - Regular
- Optimization Criteria
  - Area (roughly number of transistors)
  - Delay (roughly number of gates on longest circuit path)
  - Testability assembly line to test them 但是 gate 的 delay 和 width 相关，input 的数量。所以用 delay 来 approximate Area 相对比较简单。
  - Power consumption when the circuit is operating, especially go to higher frequency when the number of inputs becomes really large, these algorithms become unscaleable.
- 2-Level Synthesis
  - Classical (Exact)
  - Heuristic (Non-Exact)
- Multilevel Synthesis means: gates circuits that have multiple levels of logic between inputs and output or between inputs and flip flops that store memory (state)


# Not just one way to synthesize Logic Expressions $\leftrightarrow$ Circuits

logic expressions and circuits have a one-to-one correspondence.

SOP

$$f = stv + stwx + styz + uv + uwx + uyz$$

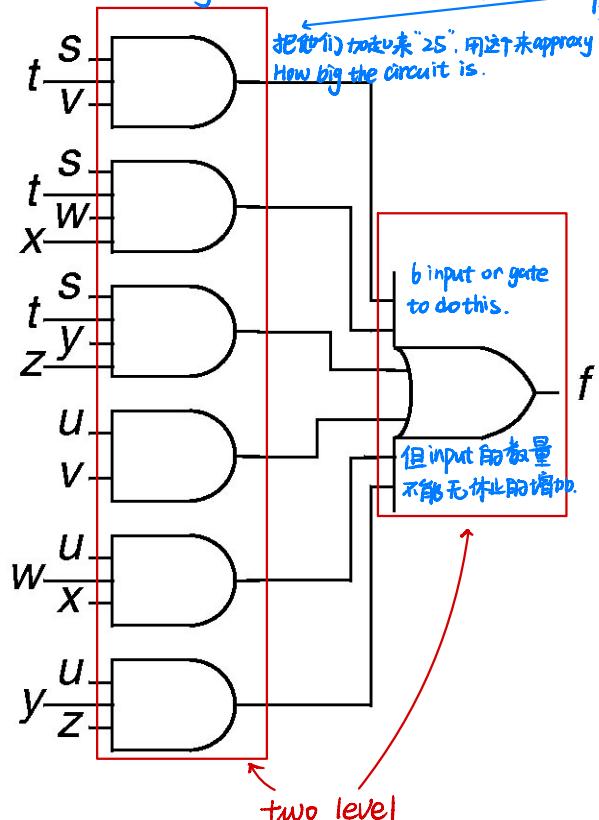
what is the size of: count how many literals are in the expression; 对于 and gate 有 1 个. 对于 or gate 有 6 个.  
the circuit?



it's not POS, because there exist product in sum. 不是 SOP 也不是 POS



$$f = (st + u)(wx + yz + v)$$

我们通过 factorization 得到这.

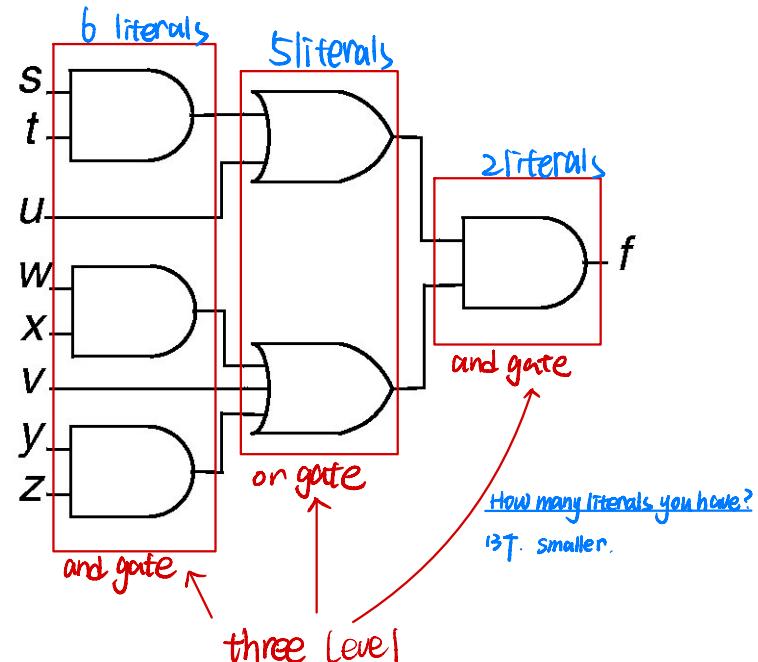




- Smaller circuit.
  - it could also be faster. (因为 gate 的 max input 是 3)
- 优先级由左向右更 preferable

# 2-Level Circuits

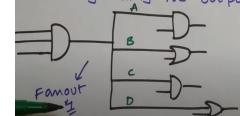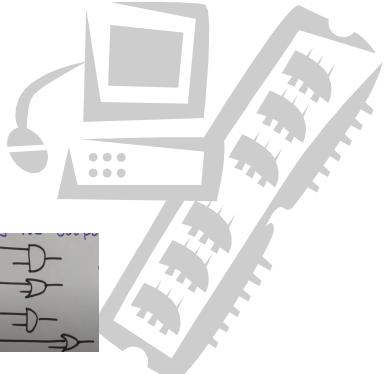

- Assumptions:
  - Inputs are available in both true and complemented forms  
(reasonable assumption: FF outputs are available in both phases)
  - Gates have no fan-in or fan-out restrictions  
(unreasonable assumption: typically FI < 4, FO < 6)
- Correspond to SOP or POS forms of a switching function:
  - SOP  $\Leftrightarrow$  AND/OR (NAND/NAND) *they are the same*
  - POS  $\Leftrightarrow$  OR/AND (NOR/NOR)
- # of 1st level AND (OR) gates = # of nontrivial product (sum) terms
- Fan-in of 2nd level OR (AND) gate = total # of product (sum) terms
- Usually implemented using regular structures:
  - Read-Only Memories (ROMs)
  - Programmable Logic Arrays (PLAs)

# AND/OR $\leftrightarrow$ NAND/NAND

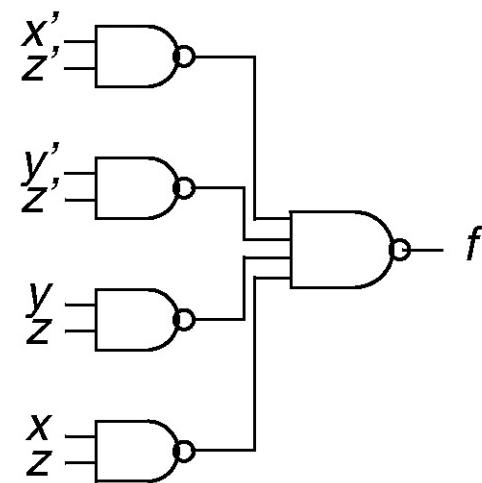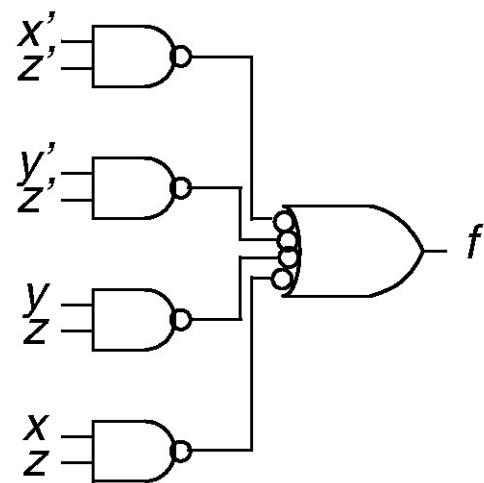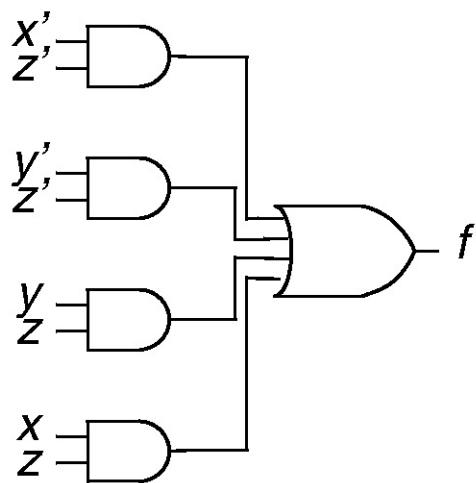

→  
Involution


→  
De Morgan's

# Terminology Review



- **Literal:** A variable or its complement
  - Ex:  $X, Y, \bar{B}$   
*that's a trivial product  
it doesn't need a gate.*
- **Product Term:** A single literal or a product of two or more literals
  - Ex:  $XY, \bar{A}\bar{B}C, \bar{W}X\bar{Y}Z$
- **Sum of Products:** A sum of product terms
- **Minterm:** A product term where every variable of the function appears once as a literal (i.e., in complemented or uncomplemented form)
- **Canonical Sum:** A sum of minterms. Every function has a unique canonical sum (up to associativity of OR)

# Canonical Sum Representations

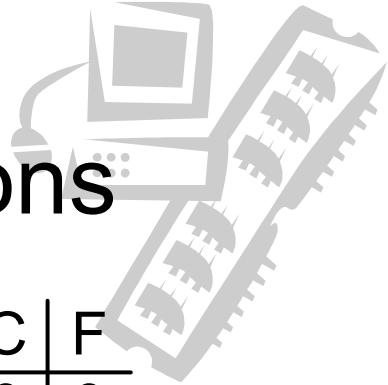

- Canonical sum uniquely defines a function, but can be long. A **minterm list** is a list of the row numbers of minterms included in the canonical sum.
  - Also known as the on-set  
*These are the roads in the truth table for the function value must be one*
- Three canonical ways of representing functions
  - truth table
  - canonical sum
  - minterm list

Row #	A	B	C	F
0	0	0	0	0
1	0	0	1	0
2	0	1	0	1
3	0	1	1	0
4	1	0	0	0
5	1	0	1	0
6	1	1	0	1
7	1	1	1	1

$$F = \sum_{A,B,C} (2,6,7)$$



# Canonical Product Representation

- **Sum Term:** A single literal or a sum of two or more literals
- **Product of Sums:** A product of sum terms
- **Maxterm:** A sum term where every variable in the function appears once as a literal
- **Canonical Product:** A product of maxterms
- **Maxterm List:** A list of the truth table row numbers of the maxterms of a function
  - Also known as the off-set

*Maxterm corresponding to 0*

Row #	A	B	C	F	Maxterms
0	0	0	0	0	A+B+C
1	0	0	1	1	A+B+ $\bar{C}$
2	0	1	0	1	A+ $\bar{B}$ +C
3	0	1	1	1	A+ $\bar{B}$ + $\bar{C}$
4	1	0	0	1	$\bar{A}$ +B+C
5	1	0	1	0	$\bar{A}$ +B+ $\bar{C}$
6	1	1	0	1	$\bar{A}$ + $\bar{B}$ +C
7	1	1	1	0	$\bar{A}$ + $\bar{B}$ + $\bar{C}$

$$F = (A + B + C)(\bar{A} + B + \bar{C})(\bar{A} + \bar{B} + C)$$

$$F = \Pi_{A,B,C}(0,5,7)$$

minterm : on-set  
maxterm : off-set

don't cares : offset

Think about how can we minimize

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Minterms

$\bar{A}\bar{B}\bar{C}$

$\bar{A}\bar{B}C$

$\bar{A}B\bar{C}$

$\bar{A}BC$


$A\bar{B}\bar{C}$

$A\bar{B}C$

$AB\bar{C}$

$ABC$

Circuit:

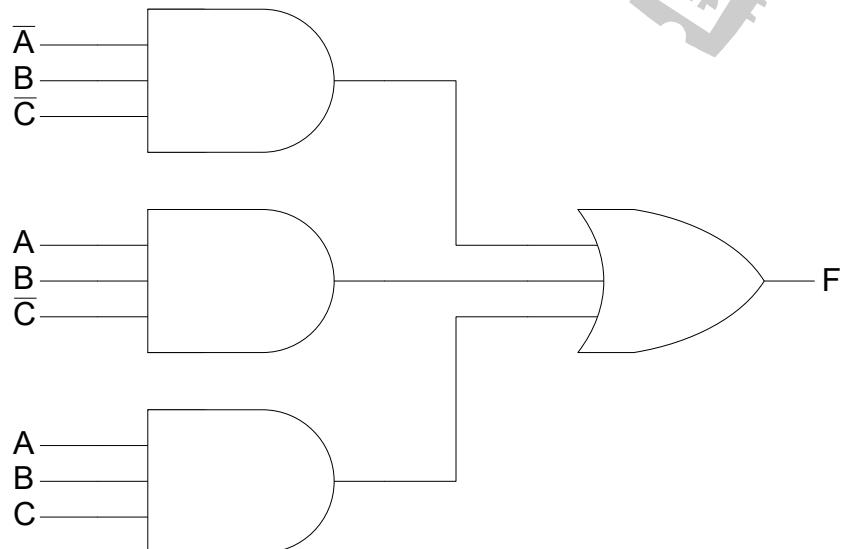

能做什么，让这个变简单吗？(见下页)

Canonical Sum:

$$F = \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} + ABC$$

Cost of implementation: **3 3-input ANDs (9 literals) + 1 3-input OR**

- Canonical sum is *not* (in general) the least-cost way to implement a function
- How to get smaller circuits?
  - One way: Switching algebra theorems!

Q: 挑出 16x3 來 minimize expression 呢？

We look for patterns where things are adjacent.

$$F = \overline{A}\overline{B}\overline{C} + A\overline{B}\overline{C} + ABC$$

Q: terms adjacent 什麼意思？


they agree on everything except one variable.

variable that is complement in one but not in other can be removed.

logical adjacency

$$= (\overline{A}\overline{B}\overline{C} + A\overline{B}\overline{C}) + (A\overline{B}\overline{C} + ABC) \quad \text{Idempotency}$$
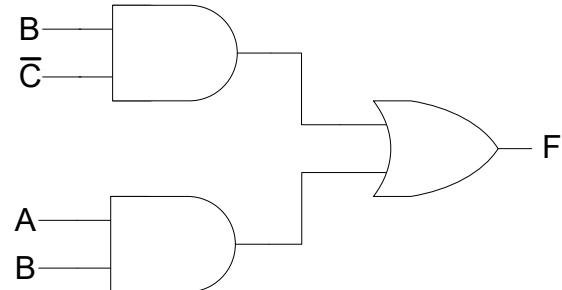
$$= B\overline{C} + AB \quad \text{Combining}$$




Cost: 2 2-input ANDs (4 literals) + 1 2-input OR!

Applying theorems directly becomes more difficult as canonical sums get bigger...

$$\overline{ABCD} + \overline{ABC}\overline{D} + \overline{ABC}\overline{D} + \overline{AB}\overline{C}\overline{D} + \overline{AB}\overline{C}\overline{D} + \overline{ABC}\overline{D} + \overline{ABC}\overline{D} + \overline{ABC}\overline{D} + \overline{ABC}\overline{D} + ABC\overline{D}$$

do the algebra graphically

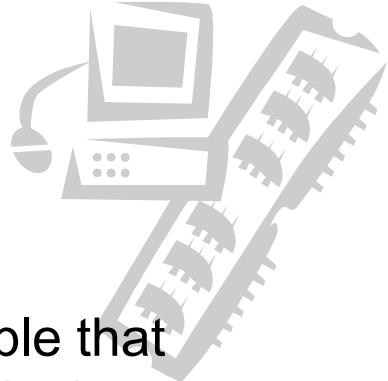- Another (perhaps easier) way: **Karnaugh maps**




# Karnaugh Maps

- Karnaugh map (K-map) is a 2D representation of truth table that present a graphical way to find the minimal SOP (or POS) of a function
  - Each cell represents a minterm
  - Cells with a common edge are logically adjacent (i.e., they will combine)
  - K-map is actually a doughnut: outside edges connect


this called normal counting sequence

	A	B	C	F
0	0	0	0	$m_0$
1	0	0	1	$m_1$
2	0	1	0	$m_2$
3	0	1	1	$m_3$
4	1	0	0	$m_4$
5	1	0	1	$m_5$
6	1	1	0	$m_6$
7	1	1	1	$m_7$

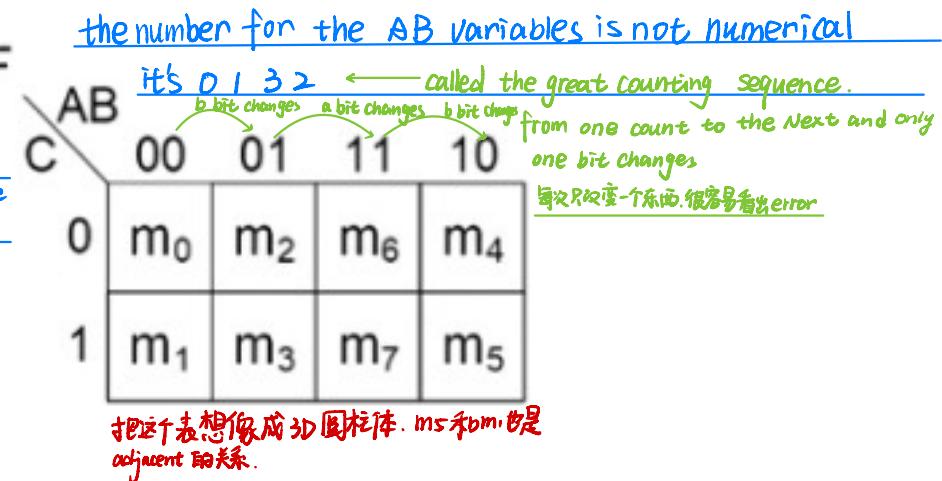idea:  
 • 左侧的每一个 square  
 对应左侧的每一行  
 • 右侧相邻的两个 square  
 是 adjacent 的关系




We'll omit 0s for clarity

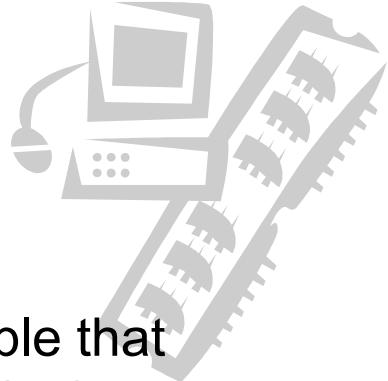

# Karnaugh Maps


- Karnaugh map (K-map) is a 2D representation of truth table that present a graphical way to find the minimal SOP (or POS) of a function
  - Each cell represents a minterm
  - Cells with a common edge are logically adjacent (i.e., they will combine)
  - K-map is actually a doughnut: outside edges connect

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

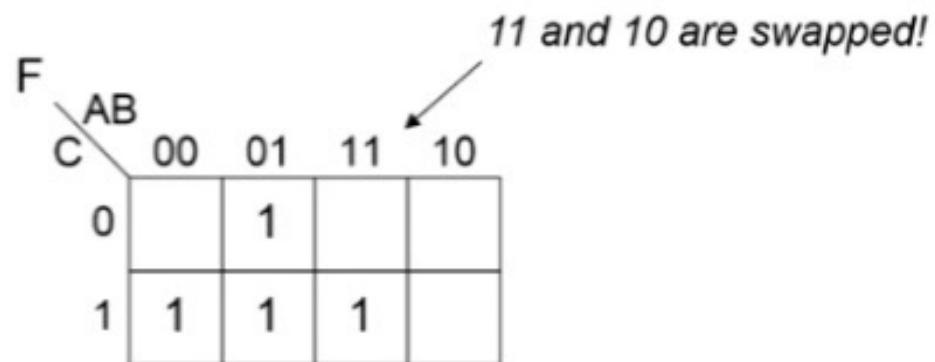

We'll omit 0s for clarity

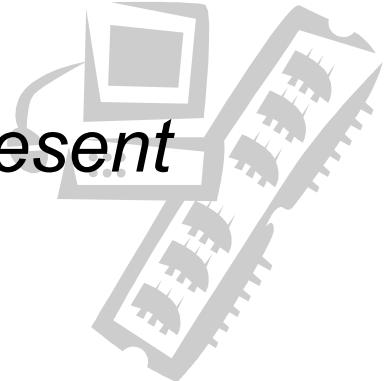
- Key K-map property: adjacent cells represent minterms that will combine!



看每个 minterm 的 binary 表达式。

如果超过一个 bit 不同，则就不是 adjacent

$$F = \sum_{X,Y,Z} (1,2,4,5)$$

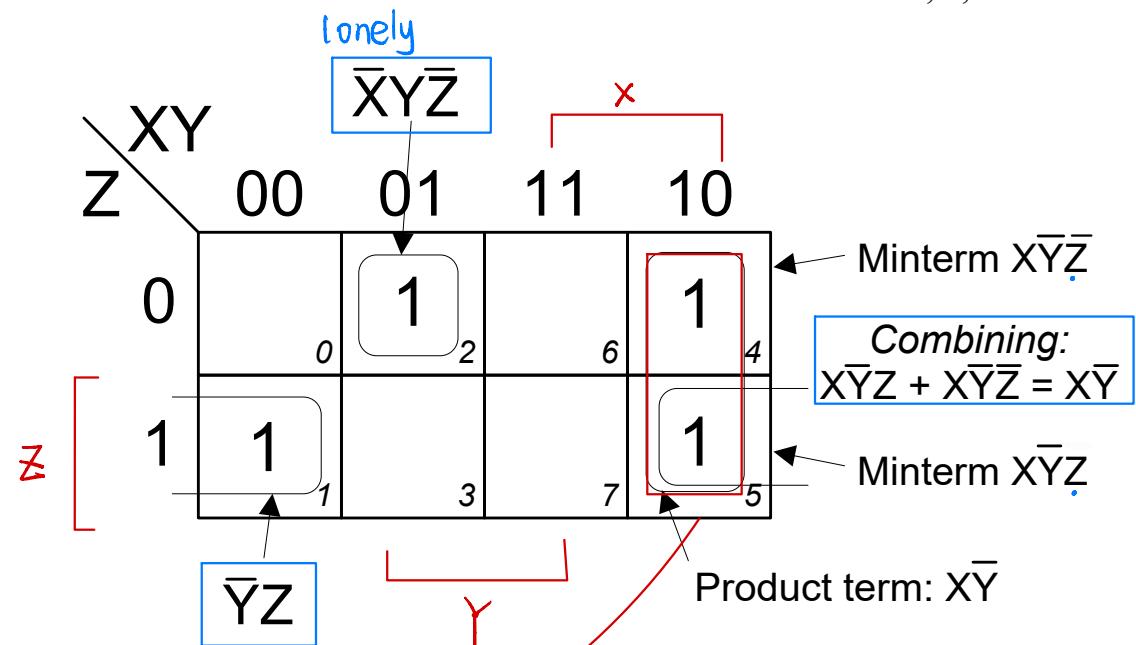

Reading product term:  
 X is 1 in both minterms: X  
 Y is 0 in both minterms:  $\bar{Y}$   
 Z is 1 in one minterm and 0 in the other: Z does not appear in product term

look at the right-most column what we can say?  
 x is true, y is not true  $\rightarrow x\bar{y}$   
 we doing set algebra

Minimal SOP:

$$F = X\bar{Y} + \bar{Y}Z + X\bar{Y}\bar{Z}$$

the cost is:  
 $2+2+3+1\times 3 = 10$

# Four Variable K-map



$$F = \sum_{W,X,Y,Z} (0,1,2,3,4,5,7,14,15)$$

F	WX	YZ	00	01	11	10
			$m_0$	$m_4$	$m_{12}$	$m_8$
			$m_1$	$m_5$	$m_{13}$	$m_9$
			$m_3$	$m_7$	$m_{15}$	$m_{11}$
			$m_2$	$m_6$	$m_{14}$	$m_{10}$

F	WX	YZ	00	01	11	10
			1 0	1 4		8
			1 1	1 5		9
			1 3	1 7	1 15	11
			1 2		1 14	10

*How do we find the product terms to include in the minimal SOP?*

- K-map “rules”

- Only circle adjacent cells (remember edges are adjacent!)

	AB	00	01	11	10
C	0		1		
	1		1		

	AB	00	01	11	10
C	0	1			
	1		1		

- Only circle groups that are powers of 2 (1, 2, 4, 8, ...)

	AB	00	01	11	10
C	0	1	1		
	1	1	1		


*It's not you can't circle it. But remember we're circling group of minterms that can be implemented as "an and gate"*

	AB	00	01	11	10
C	0	1	1		
	1		1		

- Only circle 1-cells

	AB	00	01	11	10
C	0	1			1
	1				1

	AB	00	01	11	10
C	0	1	1		
	1				

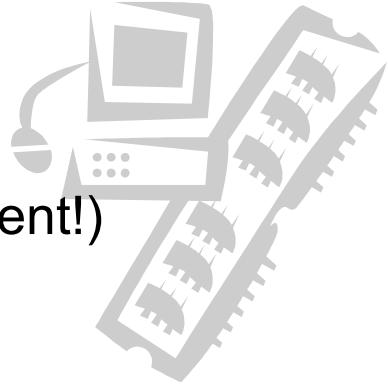

# Covering



○ = input combinations for which  $g$  outputs 1


○ = input combinations for which  $f$  outputs 1

We can also say:  $g$  implies  $f$   $g \rightarrow f$   
因为  $g$  是对的时候,  $f$  一定是对的

**$f$  covers  $g$**   
 $f=1$  whenever  $g=1$

$$f \geq g$$

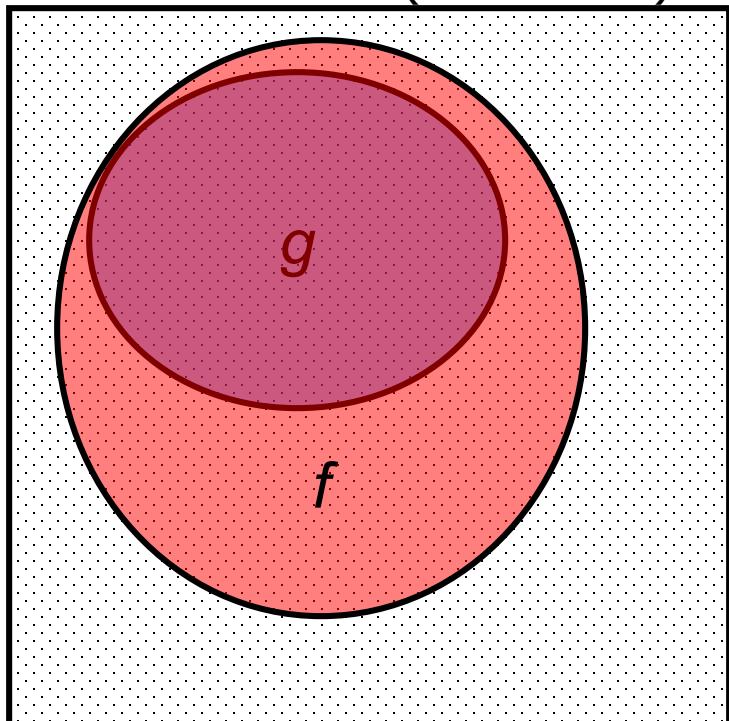Space of all  $2^n$  input combinations (minterms)




# Implicants



- = input combinations for which  $g$  outputs 1
- = input combinations for which  $f$  outputs 1
- = input combinations for which  $h$  outputs 1

If  $g$  is a product term &  $g \leq f$ ,  
Then  $g$  is an **implicant** of  $f$ .

我们专门给他一个名字。

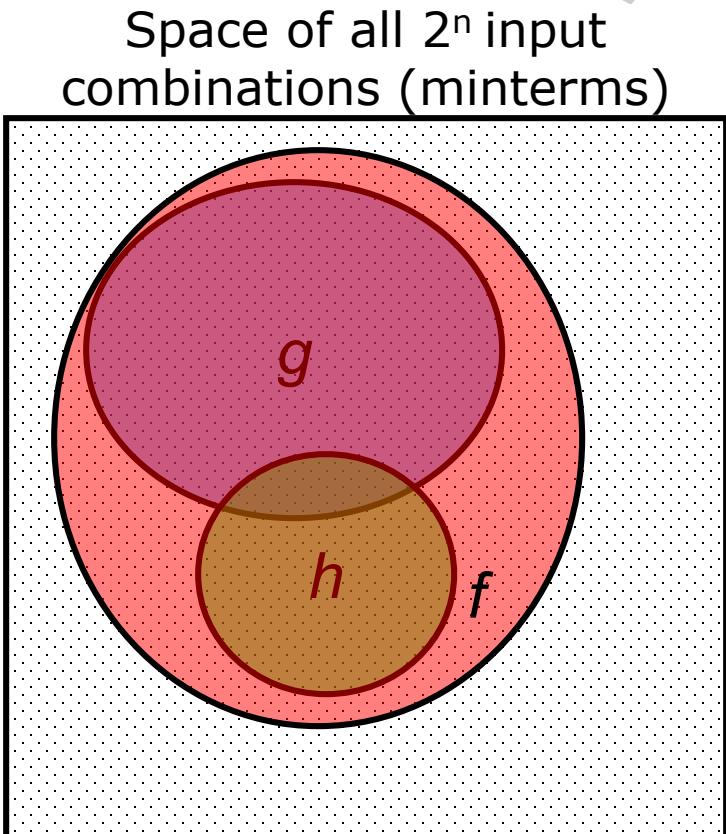


The key to minimization is finding the best implicants or the smallest and gates


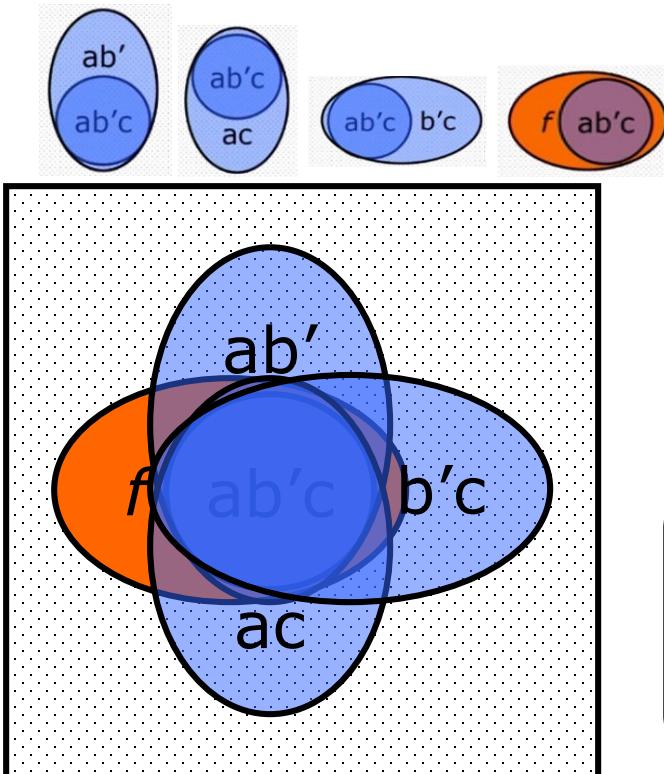
# Prime Implicants

- Removing a literal from any product term (any implicant) makes it cover twice as many minterms.
  - Removing a literal “grows” the term
  - ex. 3 variables:



ab'c covers 1 minterm  
ab'  
ac  
b'c } each cover 2 minterms

ab'c is an implicant of  $f$ .

Any way of removing a literal makes  $ab'c$  no longer imply  $f$ .  
So  $ab'c$  is a **prime implicant** of  $f$ .

**Implicant:** Any product term that implies a function F (i.e., if, for some input combination, product term  $P = 1$ , then  $F = 1$  for the same input combination)

YZ \ WX	00	01	11	10
00				
01	1	1		
11	1	1	1	
10			1	1



**Prime Implicant:** An implicant such that if one literal is removed, the resulting product term no longer implies F

YZ \ WX	00	01	11	10
00				
01	1	1		
11	1	1	1	
10			1	1

**Essential Prime Implicant:** A prime implicant that covers a minterm that is not covered by any other prime implicants

by idempotency I can cover one minterm several times, but I don't have to.


YZ \ WX	00	01	11	10
00				
01	1	1		
11	1	1	1	
10			1	1

对于这个落单的，我们有两种方式来cover 它。



*Theorem: The minimal SOP of a function is a sum of prime implicants*

## K-map minimization procedure:

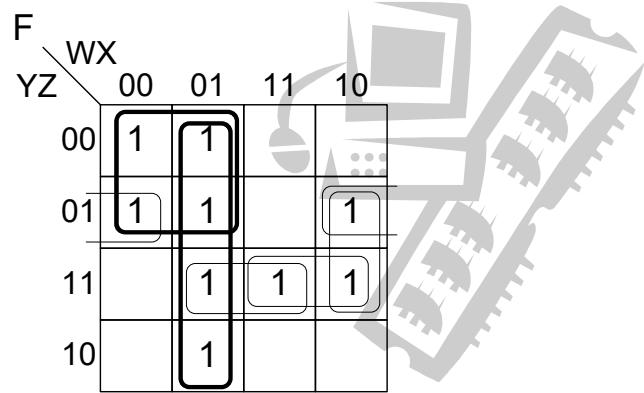- 1) Find all prime implicants (PIs)
  - 2) Determine which PIs are essential prime implicants (EPIs) and include those in the minimal SOP. *Remove all EPIs and the 1-cells they cover*
  - 3) Remove all PIs that are **eclipsed (dominated)**
    - Prime implicant X **eclipses** prime implicant Y if X covers at least all of the 1-cells that Y covers
  - 4) Find secondary EPIs, include secondary-EPIs in minimal SOP, and remove 1-cells they cover. If there are any 1-cells remaining, goto step 3
- Note: If, at any stage, there are no remaining EPIs, all remaining combinations of PIs must be considered for the minimal SOP



$$F = \overline{W}Y + \overline{W}X$$

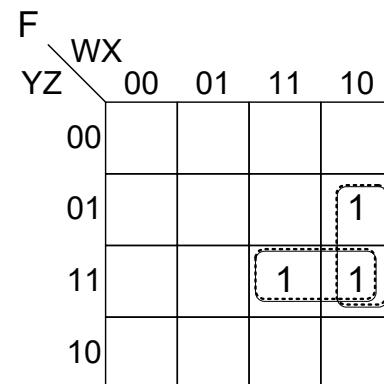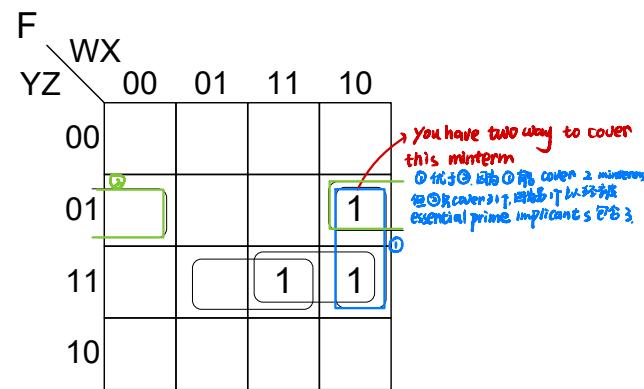

$$F = \overline{W}Y + \overline{W}X + WYZ + W'XZ$$

$\text{cost} = 2 + 2 + 3 + 3 + 4 \times 1 = 14$


19
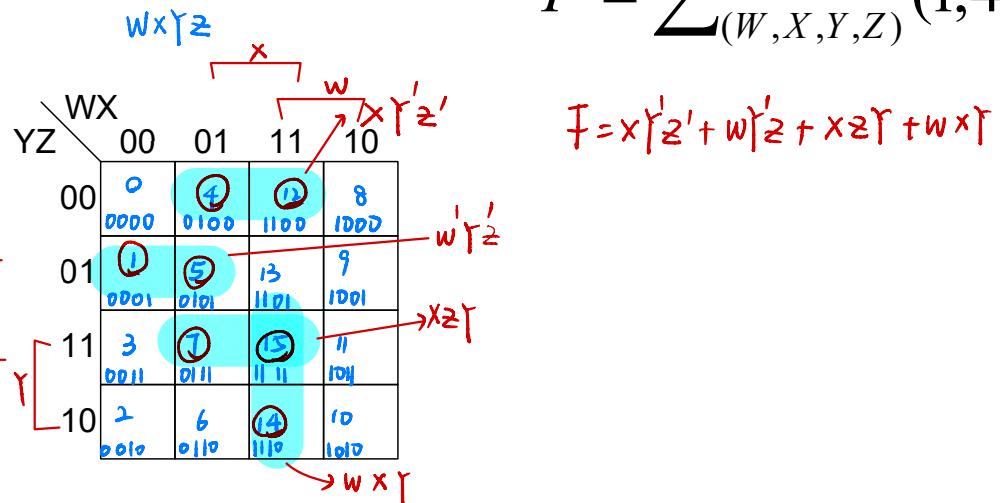
# In Class Exercise



Find the minimal SOP for the following function:

$$F = \sum_{(W,X,Y,Z)} (1,4,5,7,12,14,15)$$



$$f = xz' + w'z + xz' + wx'$$

# In Class Exercise



Find the minimal SOP for the following function:

$$F = \sum_{(W,X,Y,Z)} (1,4,5,7,12,14,15)$$

YZ \ WX	00	01	11	10
00		1	1	
01	1	1		
11		1	1	
10			1	

YZ \ WX	00	01	11	10
00		1	1	
01				
11		1	1	
10			1	

YZ \ WX	00	01	11	10
00		1	1	
01				
11		1	1	
10			1	

YZ \ WX	00	01	11	10
00				
01				
11				
10				1

$$F = \overline{W}\overline{Y}Z$$

$$F = \overline{W}\overline{Y}Z + X\overline{Y}\overline{Z} + XYZ$$

$$F = \overline{W}\overline{Y}Z + X\overline{Y}\overline{Z} + XYZ + WXY$$

or

$$F = \overline{W}\overline{Y}Z + X\overline{Y}\overline{Z} + XYZ + WX\overline{Z}$$

*The minimal SOP may not always be unique!*


# Using K-maps to find minimal POS

根据“1”的分布位置，有时 minterm 如，有时 Maxterm 如。

- 1) Find minimal SOP for  $\bar{F}$  将其找 maxterm, 不要 ↴
- 2) Use DeMorgan's to get minimal POS for F

$$F = \sum_{W,X,Y,Z} (1,3,4,6,9,11,12)$$

		WX	YZ	00	01	11	10
		00		1	1		
		01	1				1
		11	1				1
		10		1			

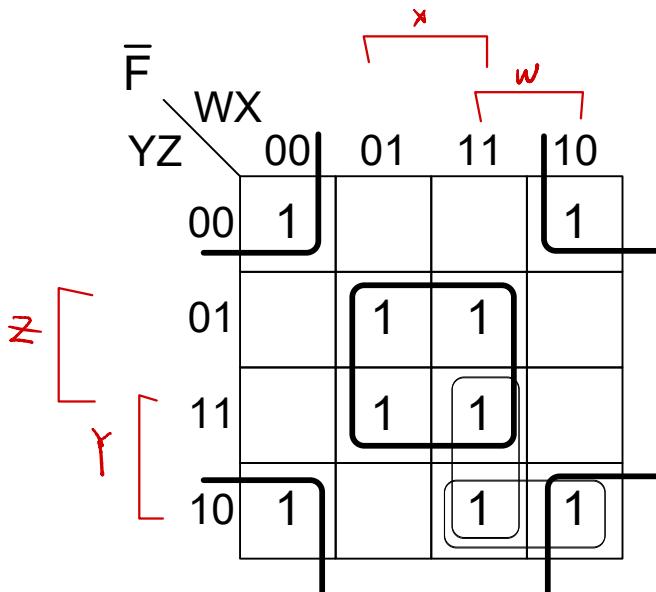

$$\bar{F} = \bar{X}\bar{Z} + XZ + WY\bar{Z}$$

$$F = (X + Z)(\bar{X} + \bar{Z})(\bar{W} + \bar{Y} + Z)$$

count cost: 2+2+3+3  
= 10

# Don't Care Outputs



- Sometimes when designing a function, some input combinations may never occur
- Design Example - *Encoder*: Converts 3-bit one-hot code to equivalent binary code

$i_2$	$i_1$	$i_0$	$O_1$	$O_0$
0	0	0	0	0
0	0	1	0	1
0	1	0	1	0
1	0	0	1	1
<i>others</i>			0	0
			(d)	(d)

How to assign unused input combinations?

$i_2$	$i_1$	$i_0$	$O_1$	$O_0$
0	0	0	1	1
0	0	1		
0	1	0		
1	0	0		

6 literals

$i_2$	$i_1$	$i_0$	$O_1$	$O_0$
0	0	0		
0	0	1	1	
0	1	0		
1	0	0		

6 literals

$i_2$	$i_1$	$i_0$	$O_1$	$O_0$
0	0	0	1	d
0	0	1	d	d
0	1	0	d	d
1	0	0	d	d

2 literals

$i_2$	$i_1$	$i_0$	$O_1$	$O_0$
0	0	0		d
0	0	1	d	d
0	1	0	d	d
1	0	0	1	d

2 literals


*Don't cares allow us to easily assign 1 or 0 to unused input combinations in order to minimize implementation cost!*

- When finding minimal SOP with don't cares:

- Use  $d$  cells to make PIs as large as possible
- No prime implicant should include only  $d$ 's
- Only 1-cells should be considered when finding minimal covering set of PIs


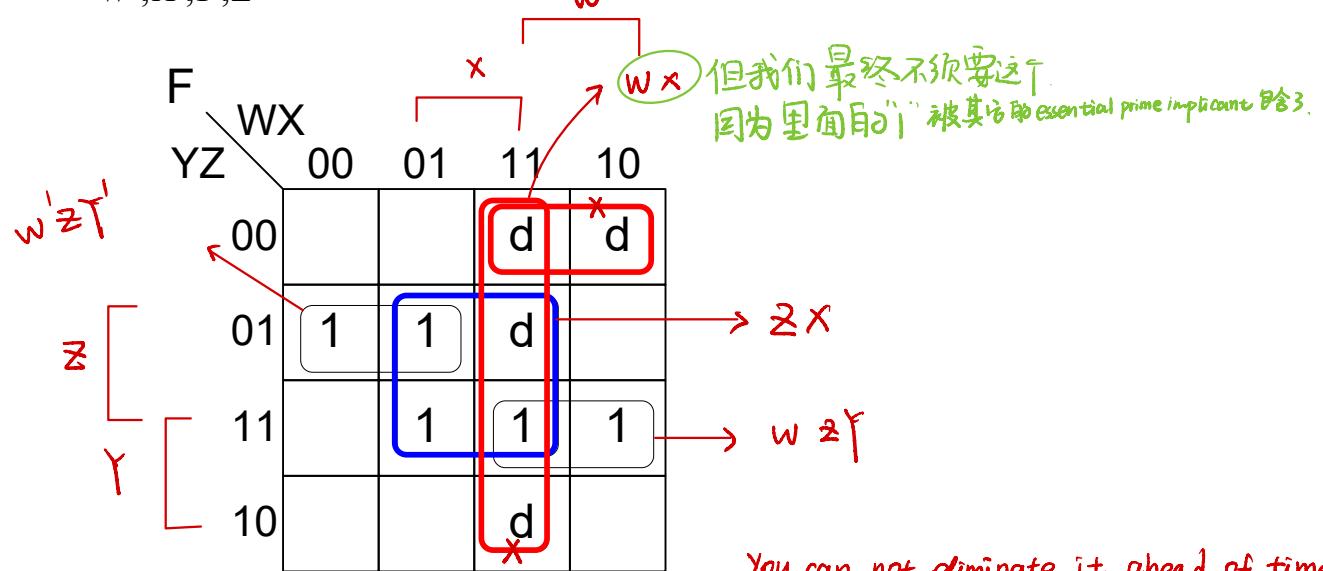
$$F = \sum_{W,X,Y,Z} (1,5,7,11,15) + d(8,12,13,14)$$



You can not eliminate it ahead of time.

Because you have to actually identify all the prime


$$F = XZ + \overline{W}\overline{Y}Z + WYZ + \cancel{WX}$$

implicants before you start minimization


So the minimal solution must be a subset of prime implicants

Most of time. Some are essential prime implicant.  
the rests are covered by them
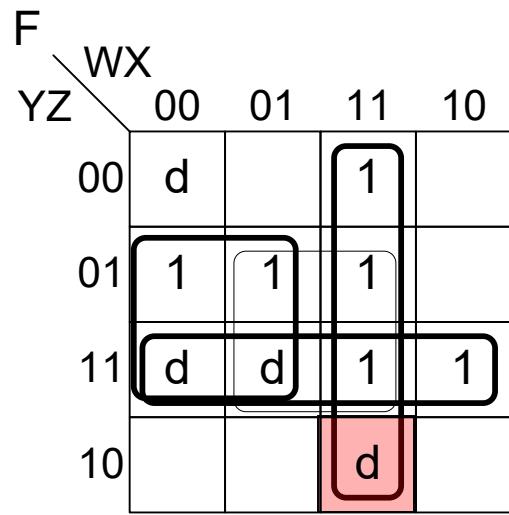
# Minimal SOP vs. Minimal POS w/ Don't Cares



$$F_{SOP} = WX + YZ + \overline{W}Z$$

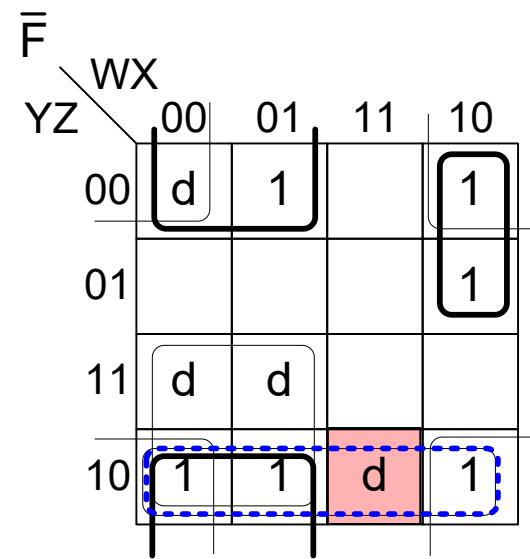


$$\begin{aligned}\bar{F} &= \overline{W}\overline{Z} + Y\overline{Z} + W\overline{X}\overline{Y} \\ F_{POS} &= (W + Z)(\overline{Y} + Z)(\overline{W} + X + Y)\end{aligned}$$

- $F_{SOP}$  has a smaller literal cost than  $F_{POS}$
- $WXYZ = 1110$ :  $F_{SOP}(1,1,1,0) = 1$ ,  $F_{POS}(1,1,1,0) = 0 \rightarrow F_{SOP} \neq F_{POS}!!!$
- When don't cares are involved, in general the minimal SOP for a function is *not equal* to the minimal POS for the function
  - But that's ok! We don't care about the input combinations where they differ...
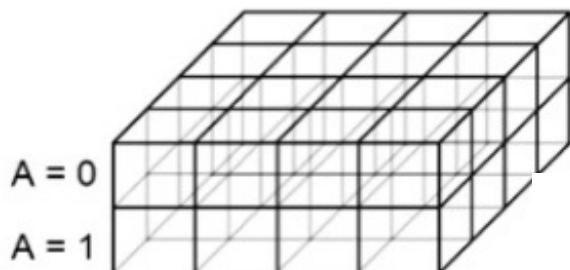
# 5 Variable K-Maps



- Every cell is adjacent to 5 other cells



		F	BC	DE	00	01	11	10
					$m_0$	$m_4$	$m_{12}$	$m_8$
					$m_1$	$m_5$	$m_{13}$	$m_9$
					$m_3$	$m_7$	$m_{15}$	$m_{11}$
					$m_2$	$m_6$	$m_{14}$	$m_{10}$

UM EECS 270

Keep life simple by splitting on the MSB!

		F	BC	DE	00	01	11	10
					$m_{16}$	$m_{20}$	$m_{28}$	$m_{24}$
					$m_{17}$	$m_{21}$	$m_{29}$	$m_{25}$
					$m_{19}$	$m_{23}$	$m_{31}$	$m_{27}$
					$m_{18}$	$m_{22}$	$m_{30}$	$m_{26}$

A = 1

Q: How many prime implicants are possibly there for a function?

A: the square in the space =  $2^n$ ,  
is an "and" of up to n literals

the prime implication is a product term  
对于每个位置有三种情况:  
complement  
uncomplement  
missing

$$F = \sum_{A,B,C,D,E} (1, 3, 15, 17, 19, 29, 31)$$



F	BC	DE	00	01	11	10
00			0	4	12	8
01	1		1	5	13	9
11	1		3	7	15	11
10			2	6	14	10


$$A = 0$$

F	BC	DE	00	01	11	10
00			16	20	28	24
01	1		17	21	29	25
11	1		19	23	31	27
10			18	22	30	26

$$A = 1$$

$$F = \overline{B}\overline{C}E + BCDE + ABCE$$
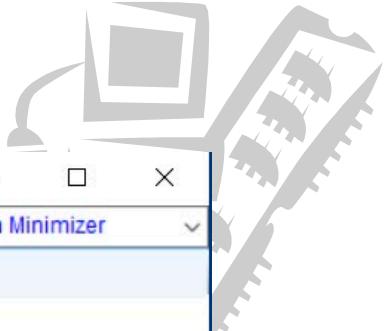
$$F = \sum_{A,B,C,D,E} (1,3,15,17,19,29,31)$$



ss BEQ

File Edit Zoom Examples Options Help Boolean Minimizer

Input Window  $\Rightarrow \neg\Rightarrow \neg\Rightarrow \neg\Rightarrow \neg\Rightarrow \neg\Rightarrow \neg\Rightarrow$

A	B	C	D	E	F
0	0	0	0	1	1
0	0	0	1	1	1
0	1	1	1	1	1
1	0	0	0	1	1
1	0	0	1	1	1
1	1	1	0	1	1
1	1	1	1	1	1;

Output Data  $\Rightarrow \neg\Rightarrow \neg\Rightarrow$  Search

```
10/3/2021
MINIMIZE TRUTH-TABLE

(1) * 25 unspecified truth table rows

      F = not B and not C and E or A and B and C and E or B and C and D and E;

.i 5
.o 1
.ilb A B C D E
.ob F
.p 3
-00-1 1
111-1 1
-1111 1
.e
```

Output Options

- Comment Lines
- Input Eqn / TT
- Truth Table - Full
- Minimize
- Invert & Minimize
- Align Minterms
- PLA Truth Table
- Sort Terms
- Logic Design

0 Operator Format